

Capacitance of a PN Junction

Objective:

Investigate the AC characteristics of the PN junction diode, and find the zero-bias junction capacitance C_{j0} .

Theory - AC Analysis

The abrupt PN junction looks like a pair of parallel plates of area A , separation W , and permittivity ϵ . This capacitance is given by,

$$C = \frac{A\epsilon}{W} \quad (1)$$

However, the width of the depletion (junction) region of a PN junction is not constant. W varies with the dc voltage across the junction as

$$W(V) = (V_0 - V)^{1/2} \left(\frac{2\epsilon_r \epsilon_0}{q} \right)^{1/2} \left(\frac{N_a + N_d}{N_a N_d} \right)^{1/2} \quad (2)$$

where V_0 is the built-in potential of the device (a constant). The junction capacitance then becomes:

$$C_j(V) = A \left(\frac{q\epsilon_r \epsilon_0}{2} \frac{N_a N_d}{N_a + N_d} \right)^{1/2} \frac{1}{|V_0 - V|^{1/2}} \quad (3)$$

where V is the dc applied voltage. The junction may be forward biased ($V > 0$) or reverse biased ($V < 0$) but Eq. (3) is the total capacitance only for reverse bias. If we square equation 3 and rewrite it, we have,

$$\frac{1}{C_j^2} = K(V_0 - V) \quad (4)$$

where $K = [(N_a + N_d)/(N_a * N_d)] * 2 / (q * \epsilon_r * \epsilon_0 * A^2)$. A plot of $1/C_j^2$ vs. V as measured should be a straight line for the ideal abrupt PN junction.

In this laboratory we will design an experiment to measure the capacitance of a PN junction as a function of the dc bias voltage V across the device. The constraints put upon this design are that the dc voltage should be varied from -20 V to +0.0 V. Some factors should be

kept in mind:

- 1) Typical junction capacitances are very small (about 100 pF), so we must make sure that we can measure these small capacitances
- 2) High frequencies must be used (you will have to justify this in your report)
- 3) Circuit leads (wires) may add stray capacitance to our measurements

An example of such a design is now presented, but a different design for achieving this task is also welcomed. The circuit chosen appears in Figure 1. **The diode is replaced with a parallel combination of a resistor and a capacitor for analysis (but not for measurements).** The ac and dc equivalent circuits are shown in Figure 2.

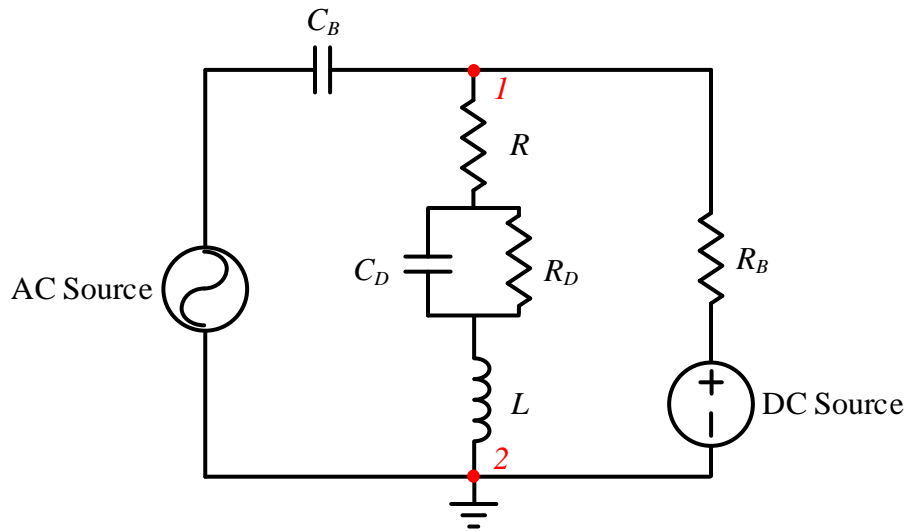


Figure 1. Experimental set-up with the diode replaced with its RC diode model

Ignoring the small R_D , If we calculate the total impedance of the RLC combination from point (1) to point (2) in Figure 1, taking into account both the real and imaginary parts, we get,

$$Z_{eq} = R + \frac{1}{j\omega C_D} + j\omega L \quad (5)$$

Rearranging and combining the real and imaginary terms,

$$Z_{eq} = R + j\left(\omega L - \frac{1}{\omega C_D}\right) \quad (6)$$

From this we can clearly see that resonance will occur for,

$$C_D = \frac{1}{(2\pi f)^2 L} \quad (7)$$

This is derived from the fact that the magnitude of a complex number has a minimum value when its imaginary component is equal to zero. Since the value of the inductance L is fixed, the only variable is frequency which is a convenient controlling parameter.

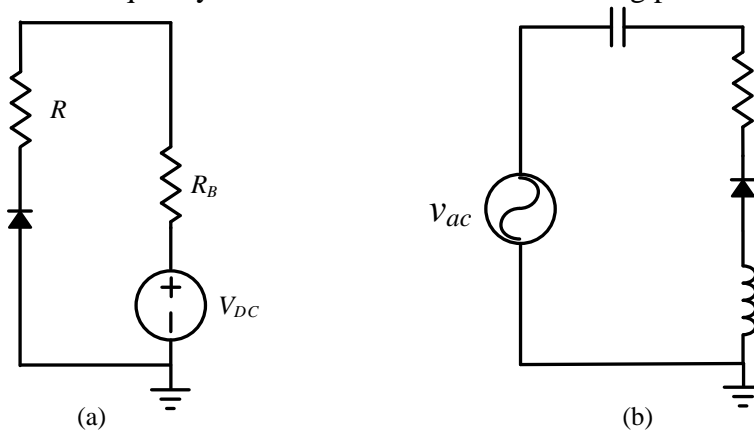


Figure 2. (a) DC equivalent circuit; (b) AC equivalent circuit.

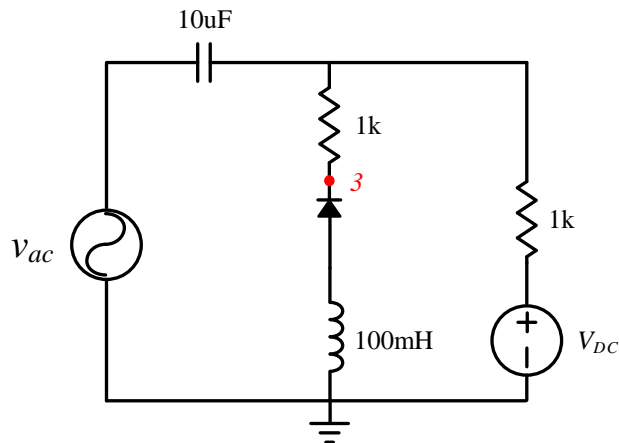


Figure 3. Circuit for capacitance measurement

PreLab - AC Analysis

Before performing the following experiments, decide on

- 1) Format for table of resonance data (voltage drop, frequency, capacitance, etc.). Be sure to note the voltage across L and diode.
- 2) Method for determining C_{j0} , the junction capacitance at zero dc bias.

Procedure - AC Analysis

1. Using an estimate of 1 pF for the diode capacitance C_j , calculate the expected resonant

frequency ($\omega^2 = 1/LC$). Use this value to choose a starting point for the frequency of your AC source.

2. Set up the circuit in Fig. 3.
3. Obtain desired voltage drop across the diode V_d by adjusting the DC power supply from 20 V to ~0.0 V in 5V steps.
4. For each V_d , observe v_{out} (the voltage of point (3) to the ground). Vary the frequency of the AC source until the LCR circuit reaches resonance (as indicated by a minimum p-p v_{out}). Record the resonant frequency f at this V_d . Tabulate these values and plot results for C_j vs. V_d and $1/C_j^2$ vs. V_d .
5. **In simulation, the frequency response can be observed by the AC sweep function in Multisim. While in experiments, the Bode analyzer in Elvis II can be used.**

Reference

- [1] Drexel University, ECE-E302, Electronic Devices.