

ShanghaiTech University
School of Information Science and Technology

EE112 Lab Experiments

**Experiment 3: Single Stage Common-Emitter(CE) & Common-
Source(CS) Amplifier**

Contents

1	Lab	1
1.1	Attenuation Network	1
1.2	Single Stage CE BJT Amplifier	1
1.3	Single Stage CS MOS Amplifier	3

1 Lab

Please remember to bring USB storage to save oscilloscope captures. Make sure you have desired measurement results displayed on the picture you saved.

1.1 Attenuation Network

Measured Attenuation Ratio: _____

1.2 Single Stage CE BJT Amplifier

Table 1: Component Values

Component Values	Measurement	Simulation(Refer to Prelab)
R_{b1}		
R_{b2}		
R_c		
R_e		

Table 2: Device Operating Points

Operating Points	Measurement	Simulation(Refer to Prelab)
V_{be}		
V_{ce}		
I_b		
I_c		

Table 3: Performance

Performance	Measurement	Simulation(Refer to Prelab)
Middle Band Gain(A_{mid})		
Low Cutoff Frequency(f_L)		
High Cutoff Frequency(f_H)		
Output Swing(SW)		
Total Power Consumption(P_{total})		

Attach the Bode plot of voltage gain (in dB) with frequency from 100Hz to 100kHz (in log scale). Mark A_{mid} , f_L and f_H on the curve.

Attach output waveform with $V_{source}=1V$ at middle band frequency. Record the magnitude (pk-pk) and frequency of the function generator aside.

Attach output waveform when output is swing limited. Record the magnitude (pk-pk) and frequency of the function generator aside.

1.3 Single Stage CS MOS Amplifier

Table 4: Component Values

Component Values	Measurement	Simulation(Refer to Prelab)
R_{g1}		
R_{g2}		
R_d		
R_s		

Table 5: Device Operating Points

Operating Points	Measurement	Simulation(Refer to Prelab)
V_{gs}		
V_{ds}		
I_d		

Table 6: Performance

Performance	Measurement	Simulation(Refer to Prelab)
Middle Band Gain(A_{mid})		
Low Cutoff Frequency(f_L)		
High Cutoff Frequency(f_H)		
Output Swing(SW)		
Total Power Consumption(P_{total})		

Attach the Bode plot of voltage gain (in dB) with frequency from 100Hz to 100kHz (in log scale). Mark A_{mid} , f_L and f_H on the curve.

Attach output waveform with $V_{source}=1V$ at middle band frequency. Record the magnitude (pk-pk) and frequency of the function generator aside.

Attach output waveform when output is swing limited. Record the magnitude (pk-pk) and frequency of the function generator aside.

Reference

[1] UNIVERSITY OF CALIFORNIA AT BERKELEY, College of Engineering
Department of Electrical Engineering and Computer Sciences, EE105 Lab Experiments