
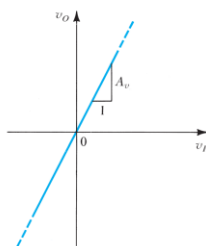


EE112 - Fall 2016

Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
 5210 Research Bldg.

Amplifier Gain (增益)

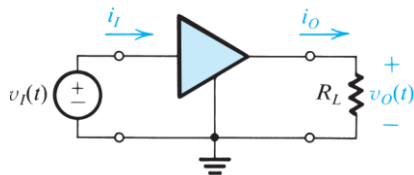

- Voltage Gain:

$$A_v = \frac{v_o}{v_i}$$

- Current Gain:

$$A_i = \frac{i_o}{i_i}$$

- Power Gain:

$$A_p = \frac{p_o}{p_i} = \frac{v_o i_o}{v_i i_i}$$

$$A_p = A_v A_i$$

- Note: A_v and A_i can be **positive**, **negative**, or even **complex** numbers. Negative gain means the output is 180° out of phase with input. However, A_p should always be a **positive** number.


- Gain is usually expressed in Decibel (dB, 分贝)

$$A_v(dB) = 10 \log|A_v|^2 = 20 \log|A_v|$$

$$A_i(dB) = 10 \log|A_i|^2 = 20 \log|A_i|$$

$$A_p(dB) = 10 \log|A_p|$$

Amplifier Power Supply and Dissipation

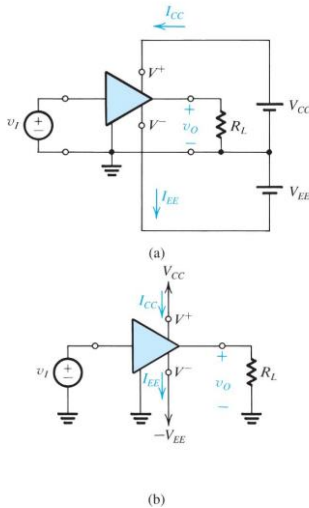

- Circuit needs dc power supplies to function
- Typical power supplies are denoted as V_{CC} and $-V_{EE}$
- Total dc power dissipation

$$P_{dc} = V_{CC} I_{CC} + V_{EE} I_{EE}$$

- Power balance

$$P_{dc} + P_I = P_L + P_{diss}$$

- » P_I : power drawn from signal source
- » P_L : power delivered to the load
- » P_{diss} : power dissipated in the amplifier circuit

- Power efficiency

$$\eta = \frac{P_L}{P_{dc}}$$

- » Important for power amplifiers: stereo output, transmitters

Figure 1.13 An amplifier that requires two dc supplies (shown as batteries) for operation.

Linear Range vs. Saturation(饱和) Range

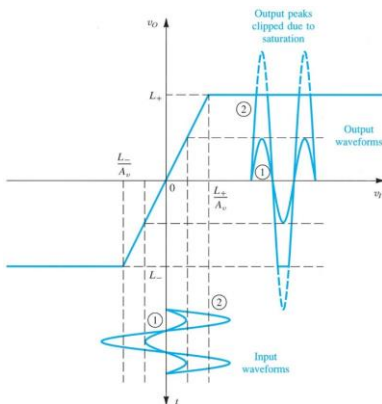


Figure 1.14 An amplifier transfer characteristic that is linear except for output saturation.

- Within linear range, the output voltage (or current) is **proportional** to the input voltage (or current)
- Beyond **linear range**, the output voltage (or current) waveforms **saturates**, resulting in distortions
 - » Lose fidelity (失真) in stereo system
 - » Cause interference in wireless system

Symbol Notation

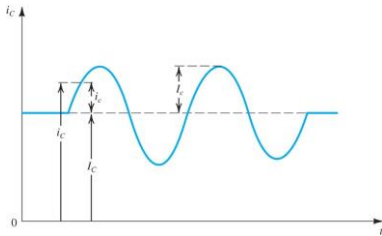


Figure 1.15 Symbol convention employed throughout the book.

$$i_c(t) = I_C + i_c(t)$$

- where, $i_c(t)$
 - » Lowercase-uppercase-> total current
- I_C
 - » Uppercase-uppercase-> dc current
- $i_c(t)$
 - » Lowercase-lowercase -> small signal ac current
$$i_c = I_c \sin(\omega t)$$
- where, I_c
 - » Uppercase-lowercase-> amplitude of ac current

▪ We will stick to this notation system throughout this course, including your homework and labs.

Circuit Model of Voltage Amplifiers

(Two-Port Model)

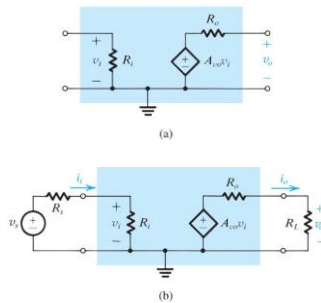


Figure 1.16 (a) Circuit model for the voltage amplifier. (b) The voltage amplifier with input signal source and load.

- A_{vo} : open-circuit voltage gain
- R_i : input resistance of the amplifier
- R_o : output resistance of the amplifier
- R_s : source resistance
- R_L : load resistance

Cascaded Amplifier

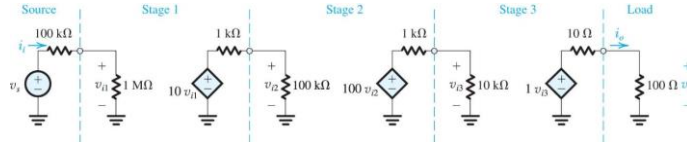


Figure 1.17 Three-stage amplifier for Example 1.3.





For most practical applications, multiple stages of amplifiers are cascaded to

1. Provide sufficient **gain**
2. Provide adequate input and output **resistances/impedances**

For example, in a voltage amplifier

- The **input stage** is designed to have **high input impedance**
- The **output stage** is designed to have **low output impedance**
- **Middle stage** provides the necessary **gain**

Amplifier Types

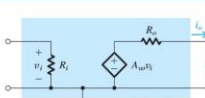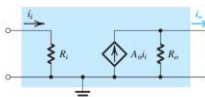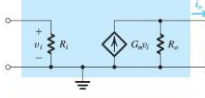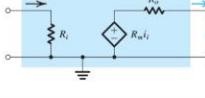Type	Circuit Model	Gain Parameter	Ideal Characteristics
Voltage Amplifier		Open-Circuit Voltage Gain $A_{vo} \equiv \left. \frac{v_o}{v_i} \right _{i_o=0}$ (V/V)	$R_i = \infty$ $R_o = 0$
Current Amplifier		Short-Circuit Current Gain $A_{sc} \equiv \left. \frac{i_o}{i_i} \right _{v_o=0}$ (A/A)	$R_i = 0$ $R_o = \infty$
Transconductance Amplifier		Short-Circuit Transconductance $G_m \equiv \left. \frac{i_o}{v_i} \right _{v_o=0}$ (A/V)	$R_i = \infty$ $R_o = \infty$
Transresistance Amplifier		Open-Circuit Transresistance $R_m \equiv \left. \frac{v_o}{i_i} \right _{i_o=0}$ (V/A)	$R_i = 0$ $R_o = 0$

Depending on the nature of the source signals and output loads, different types of amplifiers are needed:

- **Voltage** amplifier
- **Current** amplifier
- **Transconductance** (跨导) amplifier
 - * voltage to current
- **Transimpedance** (跨阻) amplifier
 - * current to voltage
- 4 models interchangeable via **Thevenin equivalent** or **Norton equivalent**

Amplifier Frequency Response

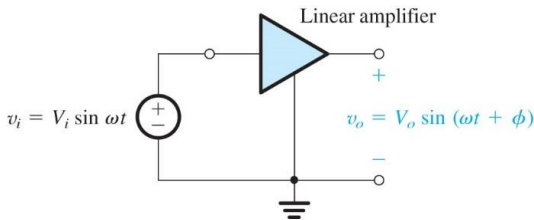


Figure 1.20 Measuring the frequency response of a linear amplifier: At the test frequency, the amplifier gain is characterized by its magnitude (V_o/V_i) and phase ϕ .

When a sinusoidal signal is applied to a linear amplifier, the output is sinusoidal:

- With the same frequency as the input
- But different **amplitude (幅度)** and **phase (相位)**

Transfer function (传递函数):

Frequency Response

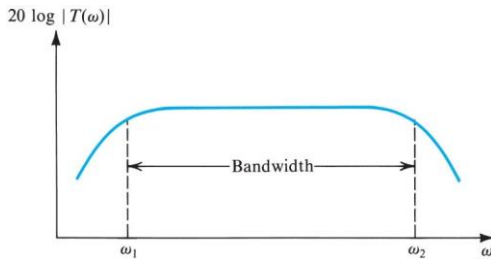


Figure 1.21 Typical magnitude response of an amplifier: $|T(\omega)|$ is the magnitude of the amplifier transfer function—that is, the ratio of the output $V_o(\omega)$ to the input $V_i(\omega)$.

Log-log plot of the **transfer function** vs. **angular frequency, ω**

- Vertical axis: $20\log |T(\omega)|$
- Horizontal axis: $10\log \omega$

This is called **Bode Plot(波特图)**

Bandwidth(带宽)

- Band of frequencies over which the gain response falls by 3dB

Frequency Response of Low-Pass Filters

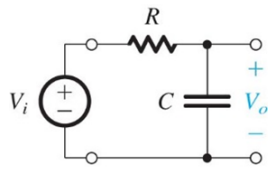
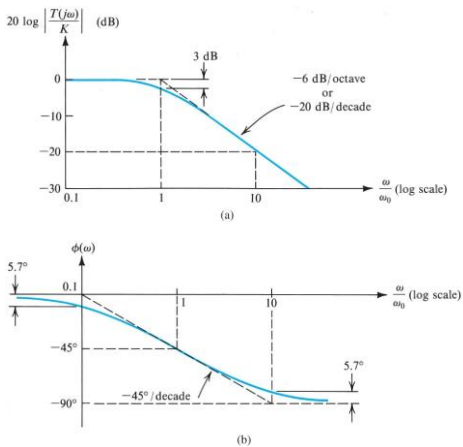


Figure 1.22 (a) a low-pass network.

Transfer function:

Figure 1.23 (a) Magnitude and (b) phase response of STC networks of the low-pass type.

Frequency Response of High-Pass Filters

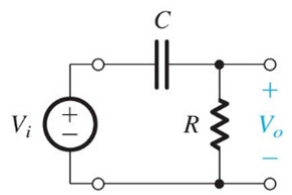


Figure 1.22 (a) a high-pass network.

Transfer function:

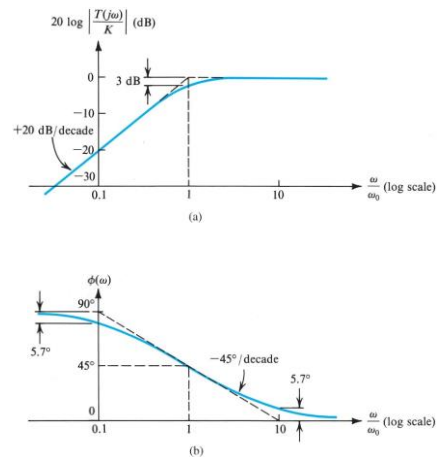


Figure 1.24 (a) Magnitude and (b) phase response of STC networks of the high-pass type.

Example: Amplifier Frequency Response

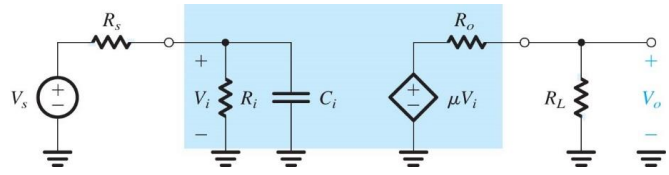


Figure 1.25 Circuit for Example 1.5.

Typical Frequency Responses

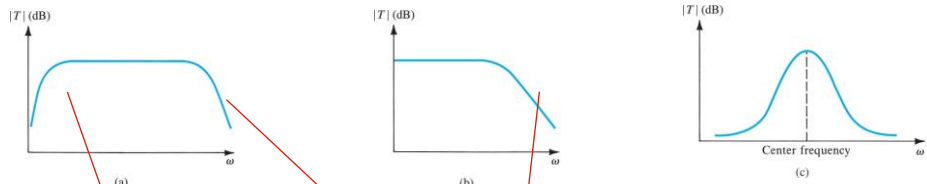


Figure 1.26 Frequency response for (a) a capacitively coupled amplifier, (b) a direct-coupled amplifier, and (c) a tuned or bandpass amplifier.

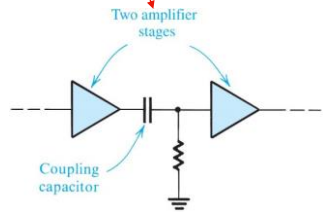


Figure 1.27 Use of a capacitor to couple amplifier stages.

High frequency cut-off due to **intrinsic capacitors** of the transistors

Low frequency roll-off due to **coupling capacitor**