
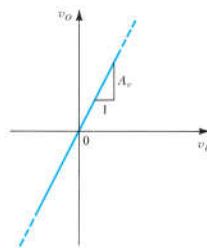


EE112 - Fall 2016

Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
 5210 Research Bldg.

Amplifier Gain (增益)

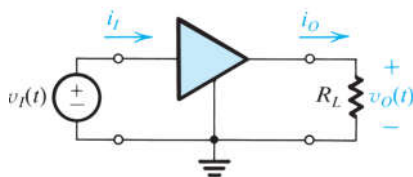

- Voltage Gain:

$$A_v = \frac{v_o}{v_i}$$

- Current Gain:

$$A_i = \frac{i_o}{i_i}$$

- Power Gain:

$$A_p = \frac{p_L}{p_i} = \frac{v_o i_o}{v_i i_i}$$

$$A_p = A_v A_i$$

- Note: A_v and A_i can be **positive**, **negative**, or even **complex** numbers. Negative gain means the output is 180° out of phase with input. However, A_p should always be a **positive** number.
- Gain is usually expressed in Decibel (dB, 分贝)

$$A_v(dB) = 10 \log |A_v|^2 = 20 \log |A_v|$$

$$A_i(dB) = 10 \log |A_i|^2 = 20 \log |A_i|$$

$$A_p(dB) = 10 \log |A_p|$$

Amplifier Power Supply and Dissipation

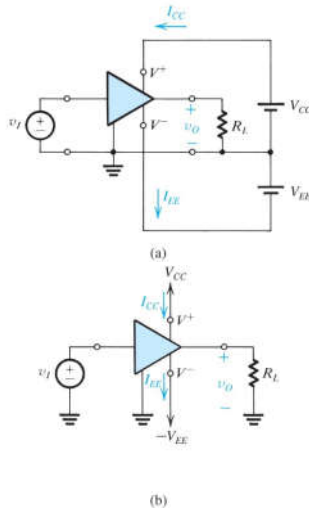


Figure 1.13 An amplifier that requires two dc supplies (shown as batteries) for operation.

- Circuit needs dc power supplies to function
- Typical power supplies are denoted as V_{CC} and $-V_{EE}$
- Total dc power dissipation

$$P_{dc} = V_{CC}I_{CC} + V_{EE}I_{EE}$$

- Power balance

$$P_{dc} + P_i = P_L + P_{diss}$$

- » P_i : power drawn from signal source
- » P_L : power delivered to the load
- » P_{diss} : power dissipated in the amplifier circuit

- Power efficiency

$$\eta = \frac{P_L}{P_{dc}}$$

- » Important for power amplifiers: stereo output, transmitters

Linear Range vs. Saturation(饱和) Range

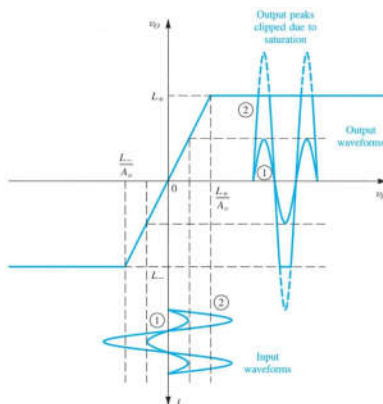


Figure 1.14 An amplifier transfer characteristic that is linear except for output saturation.

- Within linear range, the output voltage (or current) is proportional to the input voltage (or current)
- Beyond linear range, the output voltage (or current) waveforms saturates, resulting in distortions
 - » Lose fidelity (失真) in stereo system
 - » Cause interference in wireless system

Symbol Notation

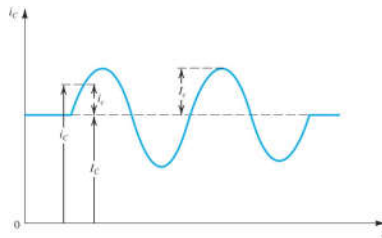


Figure 1.15 Symbol convention employed throughout the book.

$$i_c(t) = I_c + i_c(t)$$

- where, $i_c(t)$
 - » Lowercase-uppercase-> total current
 - I_c
 - » Uppercase-uppercase-> dc current
 - $i_c(t)$
 - » Lowercase-lowercase -> small signal ac current
- $$i_c(t) = I_c \sin(\omega t)$$
- where, I_c
 - » Uppercase-lowercase-> amplitude of ac current

▪ We will stick to this notation system throughout this course, including your homework and labs.

Circuit Model of Voltage Amplifiers

(Two-Port Model)

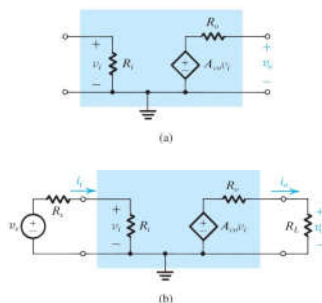


Figure 1.16 (a) Circuit model for the voltage amplifier. (b) The voltage amplifier with input signal source and load.

- A_{vo} : open-circuit voltage gain
- R_i : input resistance of the amplifier
- R_o : output resistance of the amplifier
- R_s : source resistance
- R_L : load resistance

Cascaded Amplifier

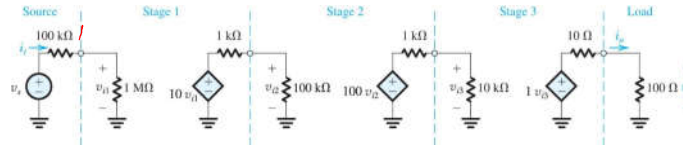


Figure 1.17 Three-stage amplifier for Example 1.3.





For most practical applications, multiple stages of amplifiers are cascaded to

1. Provide sufficient **gain**
2. Provide adequate input and output **resistances/impedances**

For example, in a voltage amplifier

- The **input stage** is designed to have **high input impedance**
- The **output stage** is designed to have **low output impedance**
- **Middle stage** provides the necessary **gain**

Amplifier Types

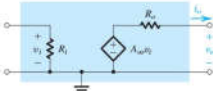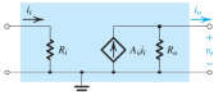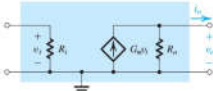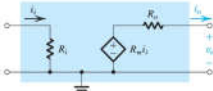Type	Circuit Model	Gain Parameter	Ideal Characteristics
Voltage Amplifier		Open-Circuit Voltage Gain $A_{vo} = \left. \frac{v_o}{v_i} \right _{i_o=0}$ (V/V)	$R_i = \infty$ $R_o = 0$
Current Amplifier		Short-Circuit Current Gain $A_{is} = \left. \frac{i_o}{i_i} \right _{v_o=0}$ (A/A)	$R_i = 0$ $R_o = \infty$
Transconductance Amplifier		Short-Circuit Transconductance $G_m = \left. \frac{i_o}{v_i} \right _{v_o=0}$ (A/V)	$R_i = \infty$ $R_o = \infty$
Transresistance Amplifier		Open-Circuit Transresistance $R_m = \left. \frac{v_o}{i_i} \right _{v_o=0}$ (V/A)	$R_i = 0$ $R_o = 0$

Depending on the nature of the source signals and output loads, different types of amplifiers are needed:

- **Voltage** amplifier
- **Current** amplifier
- **Transconductance** (跨导) amplifier
 - * voltage to current
- **Transimpedance** (跨阻) amplifier
 - * current to voltage
- 4 models interchangeable via **Thevenin equivalent** or **Norton equivalent**

Amplifier Frequency Response

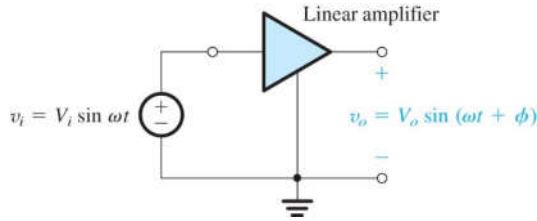


Figure 1.20 Measuring the frequency response of a linear amplifier: At the test frequency, the amplifier gain is characterized by its magnitude (V_o/V_i) and phase ϕ .

When a sinusoidal signal is applied to a linear amplifier, the output is sinusoidal:

- With the same frequency as the input
- But different **amplitude** (幅度) and **phase** (相位)

Transfer function (传递函数):

$$T(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

Amplitude response $|T(\omega)| = \frac{V_o}{V_i}$

Phase response $\angle T(\omega) = \phi$

Frequency Response

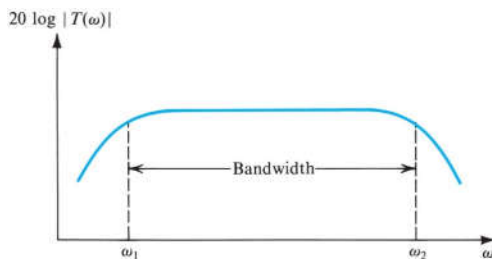


Figure 1.21 Typical magnitude response of an amplifier: $|T(\omega)|$ is the magnitude of the amplifier transfer function—that is, the ratio of the output $V_o(\omega)$ to the input $V_i(\omega)$.

Log-log plot of the **transfer function** vs. **angular frequency**, ω

- Vertical axis: $20 \log |T(\omega)|$
- Horizontal axis: $10 \log \omega$

This is called **Bode Plot**(波特图)

Bandwidth(带宽)

- Band of frequencies over which the gain response falls by 3dB

Frequency Response of Low-Pass Filters

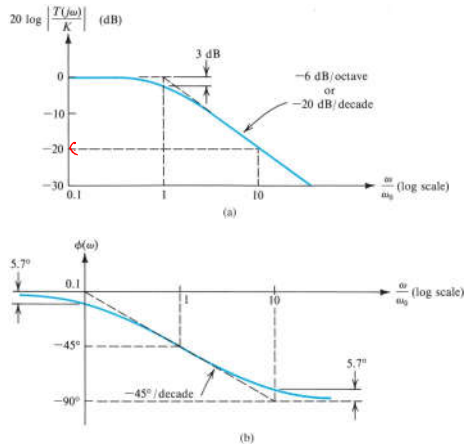


Figure 1.23 (a) Magnitude and (b) phase response of STC networks of the low-pass type.

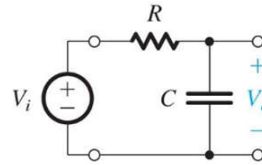


Figure 1.22 (a) a low-pass network.

Transfer function:

$$T(\omega) = \frac{1}{R + j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega/\omega_0}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

$$\angle T(\omega) = -\tan^{-1} \frac{\omega}{\omega_0}$$

$\omega_0 = \frac{1}{RC}$

Frequency Response of High-Pass Filters

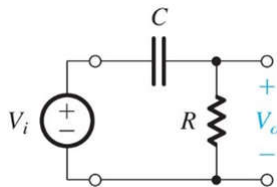


Figure 1.22 (a) a high-pass network.

LPF

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

Transfer function:

$$T(\omega) = \frac{R}{R + j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 - j\omega_0/\omega}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega_0/\omega)^2}}$$

$$\angle T(\omega) = +\tan^{-1} (\omega_0/\omega)$$

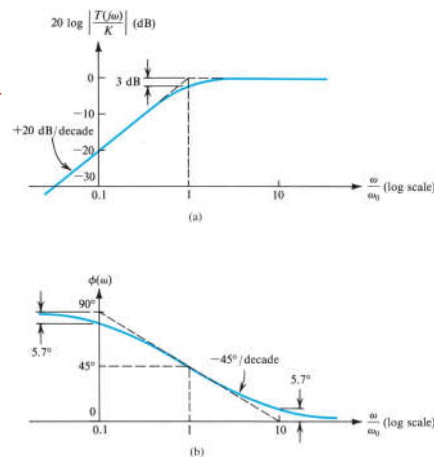


Figure 1.24 (a) Magnitude and (b) phase response of STC networks of the high-pass type.

Example: Amplifier Frequency Response

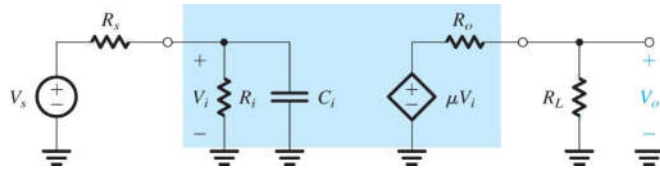


Figure 1.25 Circuit for Example 1.5.

Transfer function

$$Z_i = R_i \parallel C_i = \frac{R_i / (j\omega C_i)}{R_i + 1/(j\omega C_i)} = \frac{R_i}{1 + j\omega R_i C_i}$$

$$V_i = V_s \cdot \frac{Z_i}{R_s + Z_i} = V_s \cdot \frac{R_i}{R_s + R_i + j\omega R_i R_s C_i}$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i} \cdot \frac{1}{1 + j\omega R_{11} C_i}$$

Where $R_{11} = R_s \parallel R_i = \frac{R_s R_i}{R_s + R_i}$

$$T(\omega) = \frac{V_o}{V_s} = \frac{V_i}{V_s} \cdot \frac{V_o}{V_i} = \mu \cdot \frac{R_L}{R_o + R_L} \cdot \frac{R_i}{R_s + R_i} \cdot \frac{1}{1 + j\omega R_{11} C_i}$$

$$\frac{V_o}{V_i} = \mu \cdot \frac{R_L}{R_o + R_L}$$

$$T(\omega) = \frac{K}{1 + j(\omega/\omega_0)}$$

$$\omega_0 = \frac{1}{R_{11} C_i} \quad K = \mu \cdot \frac{R_L}{R_o + R_L} \cdot \frac{R_i}{R_s + R_i}$$

Typical Frequency Responses

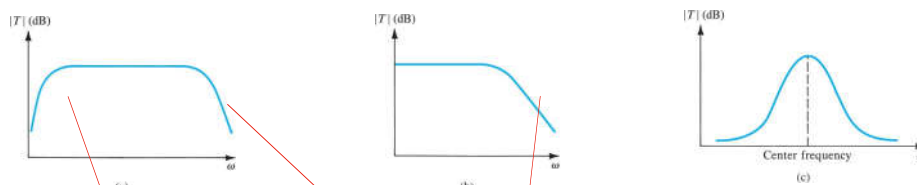


Figure 1.26 Frequency response for (a) a capacitively coupled amplifier, (b) a direct-coupled amplifier, and (c) a tuned or bandpass amplifier.

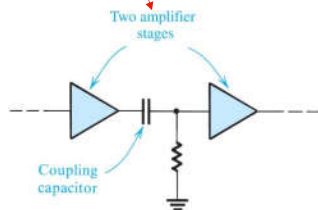


Figure 1.27 Use of a capacitor to couple amplifier stages.

High frequency cut-off due to **intrinsic capacitors** of the transistors

Low frequency roll-off due to **coupling capacitor**