

EE112 - Fall 2016

Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
5210 Research Bldg.

Review: Ideal Op-Amp

- Infinite input impedance
 - » No current goes in, virtual open circuit (虚断)
- Zero output impedance
- Infinite open-loop gain, A
 - » Virtual short circuit between the inverting and non-inverting input ports (虚短)
- Infinite bandwidth
- Infinite common-mode rejection
 - » Common mode rejection ratio (CMRR)

7.3 Electrical Characteristics μA741C , μA741M

at specified virtual junction temperature, $V_{CC\pm} = \pm 15\text{ V}$ (unless otherwise noted)

PARAMETER	TEST CONDITIONS	$T_A^{(1)}$	μA741C			μA741M			UNIT
			MIN	TYP	MAX	MIN	TYP	MAX	
V_{IO}	Input offset voltage	$V_O = 0$	25°C	1	6	1	5	mV	
			Full range		7.5	± 15	6		
$\Delta V_{IO(oad)}$	Offset voltage adjust range	$V_O = 0$	25°C	± 15		20	200	mV	
I_{IO}	Input offset current	$V_O = 0$	25°C	20	200		500	nA	
			Full range		300		500		
I_{IB}	Input bias current	$V_O = 0$	25°C	80	500	80	500	nA	
			Full range		800		1500		
V_{ICR}	Common-mode input voltage range		25°C	± 12	± 13	± 12	± 13	V	
			Full range	± 12		± 12			
V_{OM}	Maximum peak output voltage swing	$R_L = 10\text{ k}\Omega$	25°C	± 12	± 14	± 12	± 14	V	
		$R_L \geq 10\text{ k}\Omega$	Full range	± 12		± 12			
		$R_L = 2\text{ k}\Omega$	25°C	± 10		± 10	± 13		
			Full range	± 10		± 10			
A_{VO}	Large-signal differential voltage amplification	$R_L \geq 2\text{ k}\Omega$	25°C	20	200	50	200	V/mV	
		$V_O = \pm 10\text{ V}$	Full range	15		25			
r_i	Input resistance		25°C	0.3	2	0.3	2	M Ω	
r_o	Output resistance	$V_O = 0$, See (2)	25°C	75		75		Ω	
C_i	Input capacitance		25°C	1.4		1.4		pF	
CMRR	Common-mode rejection ratio	$V_{IC} = V_{IC(min)}$	25°C	70	90	70	90	dB	
			Full range	70		70			
k_{VDS}	Supply voltage sensitivity ($\Delta V_{IO}/\Delta V_{CC}$)	$V_{CC} = \pm 9\text{ V}$ to $\pm 15\text{ V}$	25°C	30	150	30	150	$\mu\text{V/V}$	
			Full range		150		150		
I_{OS}	Short-circuit output current		25°C	± 25	± 40	± 25	± 40	mA	
I_{CC}	Supply current	$V_O = 0$, No load	25°C	1.7	2.8	1.7	2.8	mA	
			Full range		3.3		3.3		
P_D	Total power dissipation	$V_O = 0$, No load	25°C	50	85	50	85	mW	
			Full range		100		100		

Switching Characteristics of a Real Op-Amp

over operating free-air temperature range, $V_{CC\pm} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ (unless otherwise noted)

PARAMETER	TEST CONDITIONS	μA741C			μA741M			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
t_r	Rise time	$V_I = 20\text{ mV}$, $R_L = 2\text{ k}\Omega$, $C_L = 100\text{ pF}$, See Figure 1						μs
	Overshoot factor							—
SR	Slew rate at unity gain	$V_I = 10\text{ V}$, $R_L = 2\text{ k}\Omega$, $C_L = 100\text{ pF}$, See Figure 1						V/ μs

- Finite open-loop gain ($A_o < \infty$)
- Finite input resistance ($R_i < \infty$)
- Non-zero output resistance ($R_o > 0$)
- Finite bandwidth
- Offset (偏移) voltage
- Input bias and offset currents

Offset (偏移) Voltage

 


Figure 2.28 Circuit model for an op amp with input offset voltage V_{OS} .

 


Figure E2.21 Transfer characteristic of an op amp with $V_{OS} = 5$ mV.

Trimming of Offset Voltage

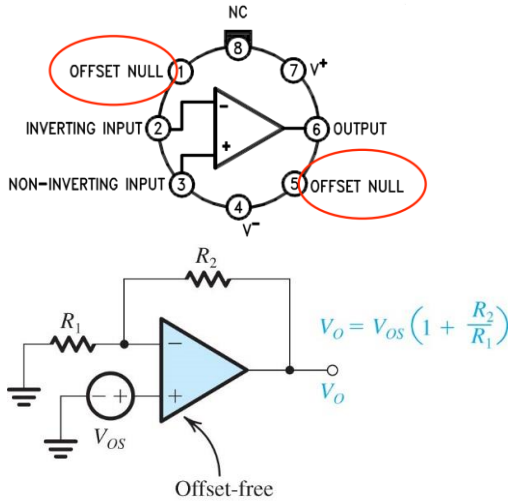


Figure 2.29 Evaluating the output dc offset voltage due to V_{OS} in a closed-loop amplifier.

 


Figure 2.30 The output dc offset voltage of an op amp can be trimmed to zero by connecting a potentiometer to the two offset-nulling terminals. The wiper of the potentiometer is connected to the negative supply of the op amp.

Input Bias Currents and Offset Currents


 


Figure 2.32 The op-amp input bias currents represented by two current sources I_{B1} and I_{B2} .

- The input terminals need to be supplied with bias currents, I_{B1} and I_{B2} , for Op Amp to function. (This will become clear towards the end of the semester).
- Input bias current: $I_B = (I_{B1} + I_{B2})/2$
- Input offset current: $I_{OS} = |I_{B1} - I_{B2}|$
- Typical bipolar transistor Op amps:
 - » $I_B \sim 100 \text{ nA}$
 - » $I_{OS} \sim 10 \text{ nA}$

 

- In the absence of input voltage, the output should be zero for ideal Op Amp. **However**, with non-zero I_B ,

- $V_O = I_{B1} R_2 \approx I_B R_2$

Figure 2.33 Analysis of the closed-loop amplifier, taking into account the input bias currents.

 


Figure 2.34 Reducing the effect of the input bias currents by introducing a resistor R_3 .

 


Figure 2.34 Reducing the effect of the input bias currents by introducing a resistor R_3 .


 


Figure 2.39 Open-loop gain of a typical general-purpose, internally compensated op amp.


Single pole response with a dominant pole at ω_b

 Frequency Response of Closed-Loop Op Amp (Inverting Amplifier Example)



- Steps to find frequency response of closed-loop amp

Continued

 

Frequency Response of Closed-Loop (Noninverting Amplifier Example)


 


Figure 2.12 The noninverting configuration.

Continued

 

Output Saturation

- The output voltage swing is limited by
 - » 1. Saturation voltage (usually a volt or two lower than power supply voltage)
 - » 2. Maximum output current (in case of small load resistance)
- Output waveform appears to be “clipped” when either condition happens

 


Figure 2.42 (a) A noninverting amplifier with a nominal gain of 10 V/V designed using an op amp that saturates at ± 13 -V output voltage and has ± 20 -mA output current limits. (b) When the input sine wave has a peak of 1.5 V, the output is clipped off at ± 13 V.

Slew Rate (压摆率)

- Amplifier output is limited by "slew rate": maximum rate of change possible at output

$$SR = \left. \frac{dv_o}{dt} \right|_{max}$$

- SR is specified in datasheet in V/ μ s.
- Note: SR limit is different from bandwidth limit:
 - » Limited bandwidth is a linear phenomenon, it does not result in a change the shape of an input sinusoid
 - » SR limitation can cause nonlinear distortion to input sinusoidal signal


 


Figure 2.43 (a) Unity-gain follower. (b) Input step waveform. (c) Linearly rising output waveform obtained when the amplifier is slew-rate limited. (d) Exponentially rising output waveform obtained when V is sufficiently small so that the initial slope (ωV) is smaller than or equal to SR.


Comparison of Slew Rate and Bandwidth Limits

 - For step function input waveform, both SR and bandwidth limits cause the output to rise with a finite slope, but there is an important difference:



Slew rate limited output:

Slope = SR

 

Bandwidth limited output:

Slope = $\omega_t V < SR$

(V is the steady state output voltage)

Full-Power Bandwidth

 


Figure 2.43 (a) Unity-gain follower.

- For sinusoidal input to unity-gain follower:

$$v_I = V_i \sin \omega t$$

- Rate of change:

$$\frac{dv_I}{dt} = V_i \omega \cos \omega t \leq SR$$

- Full-power bandwidth:**

The frequency at which SR-limited distortion starts to occur for an output sinusoid with maximum rated output voltage, V_{Omax} ,

$$\omega_M V_{Omax} = SR$$

$$f_M = \frac{SR}{2\pi V_{Omax}}$$

 


Figure 2.44 Effect of slew-rate limiting on output sinusoidal waveforms.

Summary

- Open loop gain
- Input impedance
- Output impedance
- Input offset & Bias
- CMRR
- Saturation
- Unity-gain bandwidth
- Slew rate
- Full-power bandwidth