

EE112 - Fall 2016 Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
 5210 Research Bldg.

I-V Characteristics of BJT

- The I-V looks similar to MOSFET's I-V, though the **physical equations** governing the saturation (triode for MOSFET) and active (saturation for MOSFET) are **different**.
- i_C has a finite slope in the active region, due to **base width modulation** (called **Early Effect**).
 - » Similar to channel length modulation in MOSFET

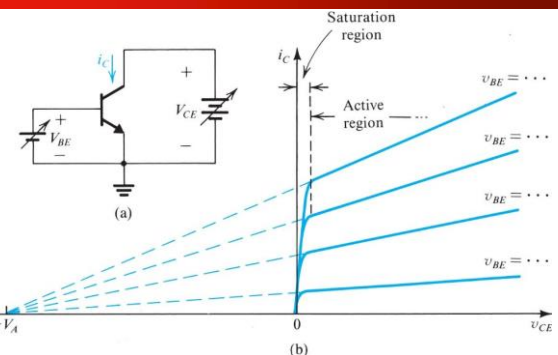


Figure 4.18 (a) Conceptual circuit for measuring the $i_C - v_{CE}$ characteristics of the BJT. (b) The $i_C - v_{CE}$ characteristics of a practical BJT.


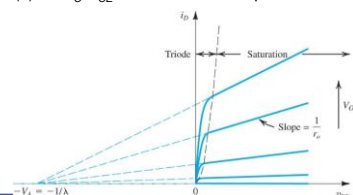


Figure 5 ShanghaiTech University

Early Effect

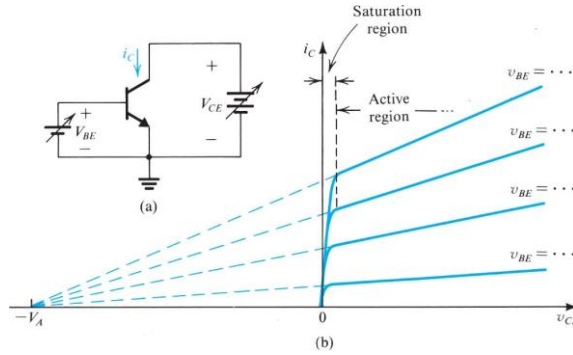

Large-Signal Model of BJT in Active Mode

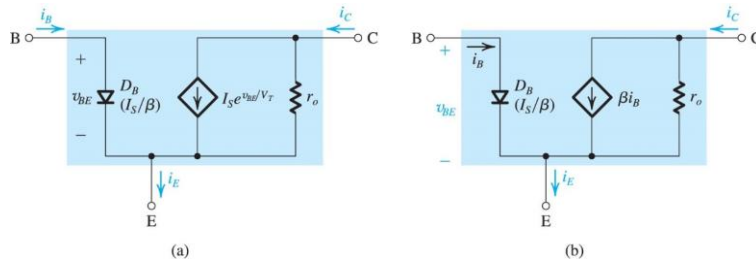


Figure 4.19 Large-signal, equivalent-circuit models of an npn BJT operating in the active mode in the common-emitter configuration with the output resistance r_o included.

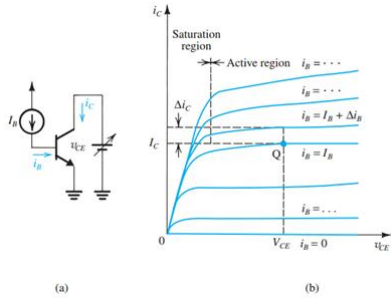


Figure 4.20 Common-emitter characteristics. (a) Basic CE circuit; note that in (b) the horizontal scale is expanded around the origin to show the saturation region in some detail.

- Usually the I-V curves are plotted with I_B as parameter rather than V_{BE} so the family of curves are roughly equally spaced.
- The current gain can be simply measured by

$$\beta = \frac{\Delta i_C}{\Delta i_B}$$

Saturated BJT

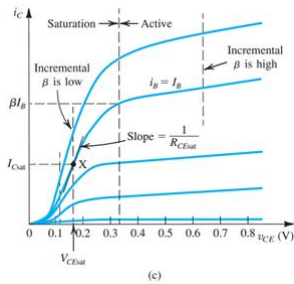


Fig 4.20 (c) A much greater expansion of the saturation region.

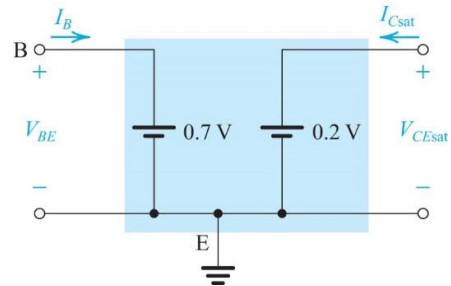


Figure 4.21 A simplified equivalent-circuit model of the saturated transistor.

Discussion: Circuit Modeling

Question: why do we use simplified models in hand calculation?

1. Better models can be used to obtain more accurate results.
2. However, at the expense of speed of analysis: the attendant complexity could impede the circuit designer's ability to gain **insight** regarding circuit behavior.
3. Accurate results using high level models can be obtained using **circuit simulation** with SPICE: done as the final stages of a design and certainly before circuit fabrication.
4. However, computer simulation is **not** a substitute for quick pencil-and-paper circuit analysis, **an essential ability that aspiring circuit designers must master.**

Example: BJT Bias Point (偏置点)

- $\beta = 100$, Find the bias point of the BJT circuit (i.e., I_C and all nodal voltages)


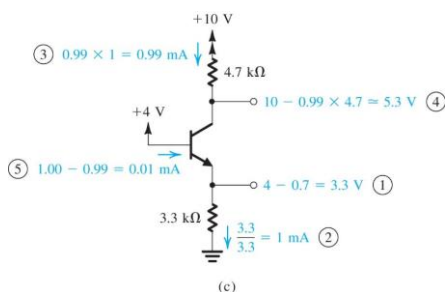


Figure 4.23 Analysis of the circuit for Example 4.4:

Note: in DC analysis, we can usually approximate $I_C \approx I_E$


BJT Bias Example

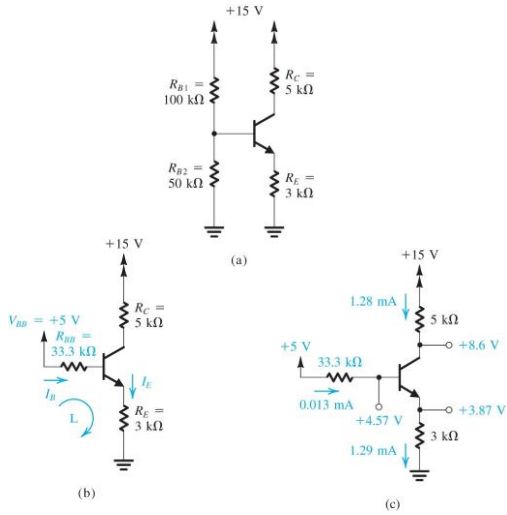

▪ $\beta = 100$, find the bias point.

Figure 4.29 Circuits for Example 4.10.


BJT Bias Example

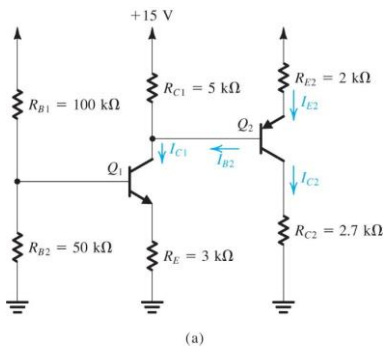

▪ $\beta = 100$, find the bias point.

Figure 4.30 Circuits for Example 4.11.

“Digital” Circuit Example

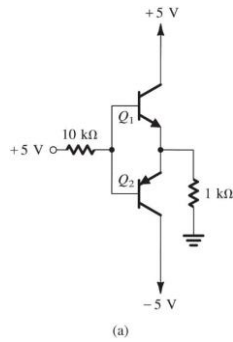

- $\beta = 100$, find the bias point.

Figure 4.31 Example 4.12: (a) circuit;