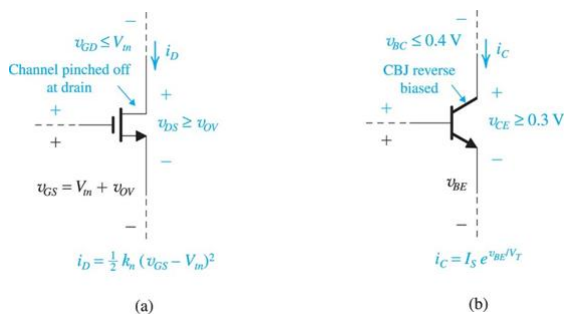


# EE112 - Fall 2016

## Analog Integrated Circuits I

Prof. Haoyu Wang  
[wanghy@shanghaitech.edu.cn](mailto:wanghy@shanghaitech.edu.cn)  
 5210 Research Bldg.

### Transistor Operating Mode in Amplifiers



- Transistors are biased in flat part of the I-V curves
  - » Saturation mode for MOSFET, and active mode for BJT
    - MOSFET: Channel pinched off at drain
    - BJT: base-collector junction reverse-biased
  - » Drain (collector) voltage can vary without changing current

**Figure 6.1** Operating (a) an NMOS transistor and (b) an npn transistor in the active mode. Note that  $v_{GS} = V_m + v_{OV}$  and  $v_{DS} \geq v_{OV}$ , thus  $v_{GD} \leq V_m$ , which ensures channel pinch-off at the drain end. Similarly,  $v_{BE} \approx 0.7$  V, and  $v_{CE} \geq 0.3$  V results in  $v_{BC} \leq 0.4$  V, which is sufficient to keep the CBJ from conducting

# Voltage Transfer Curves

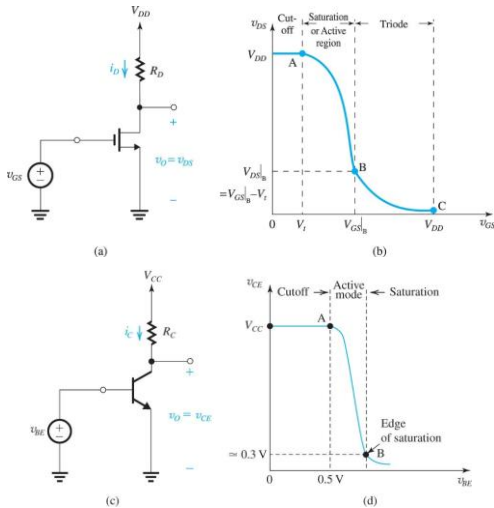


Figure 6.2 (a) An NMOS amplifier and (b) its VTC; and (c) an *npn* amplifier and (d) its VTC.

- Transistors are **transimpedance** amplifiers
  - » MOSFET:  $v_{GS}$  controls  $i_D$
  - » BJT:  $v_{BE}$  controls  $i_C$
- Adding load resistors **converts** current to voltage  $\rightarrow$  voltage amplifiers
  - » Drain (collector) voltage free to change in saturation (active) mode

# Voltage Amplifier


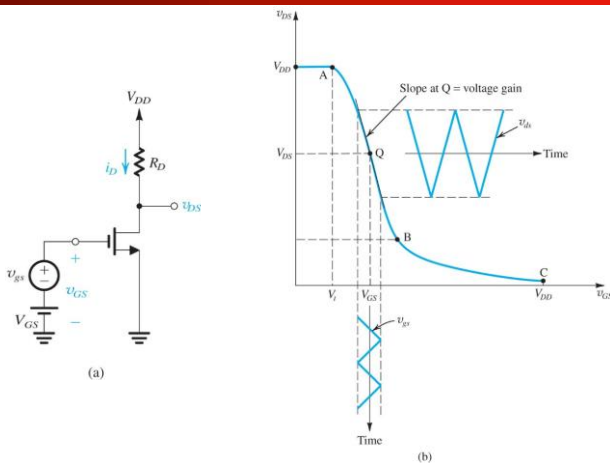


Figure 6.4 The MOSFET amplifier with a small time-varying signal  $v_{gs}(t)$  superimposed on the dc bias voltage  $V_{GS}$ . The MOSFET operates on a short almost-linear segment of the VTC around the bias point Q and provides an output voltage  $v_{ds} = A_v v_{gs}$


# Maximum Input Signal Amplitude

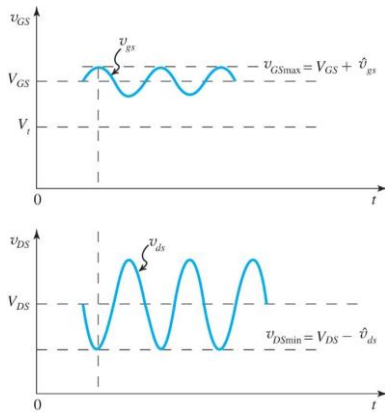

To keep the MOSFET in saturation region:

**Figure 6.5** Signal waveforms at gate and drain for the amplifier in Example 6.1. Note that to ensure operation in the saturation at all times,  $v_{DSmin} \geq v_{GSmax} - V_T$

# BJT Amplifier

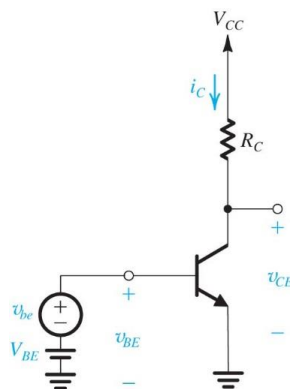

**Figure 6.6** BJT amplifier biased at a point  $Q$ , with a small voltage  $v_{be}$  superimposed on the dc bias voltage  $V_{BE}$ . The resulting output signal  $v_{ce}$  appears superimposed on the dc collector voltage  $V_{CE}$ . The amplitude of  $v_{ce}$  is larger than that of the  $v_{be}$  by the voltage gain  $A_v$ .

# Graphical Analysis with Load Line

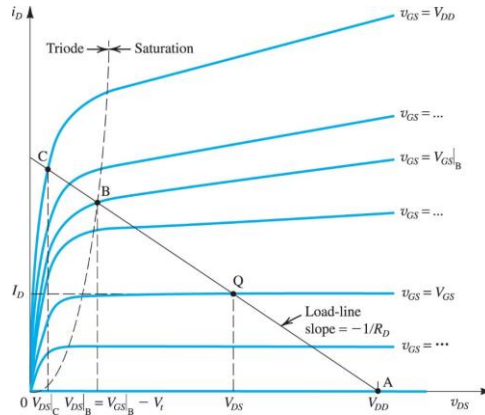


Figure 6.7 Graphical construction to determine the voltage-transfer characteristic of the amplifier in Fig. 6.4(a).

# Consideration for Bias Point


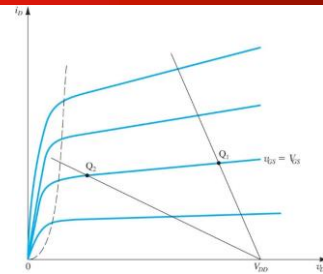
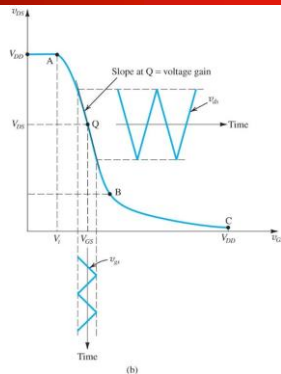


Figure 6.9 Two load lines and corresponding bias points. Bias point  $Q_1$  does not leave sufficient room for positive signal swing at the drain (too close to  $V_{DD}$ ). Bias point  $Q_2$  is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.

# Small signal model for MOSFET



## Hybrid- $\pi$ Model

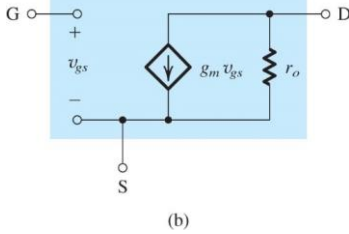

**Figure 6.13** Small-signal models for the MOSFET: (b) including the effect of channel-length modulation, modeled by output resistance  $r_o = |V_A|/I_D$ . These models apply equally well for both NMOS and PMOS transistors.


- The equivalent circuit is valid for both NMOS and PMOS
- In PMOS, use absolute sign for all parameters:  $|V_{GS}|$ ,  $|V_t|$ ,  $|V_{OV}|$ ,  $|V_A|$ , and replace  $k_n$  with  $k_p$

## Applying small-signal model

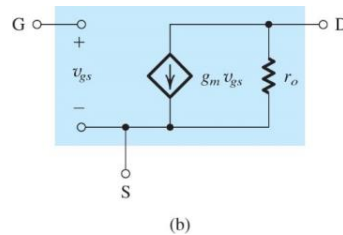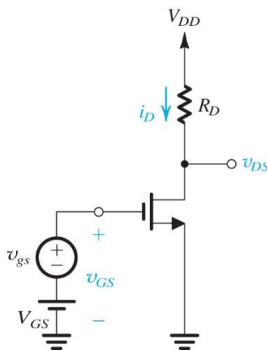


**Figure 6.10** Conceptual circuit utilized to study the operation of the MOSFET as a small-signal amplifier.

# Small signal model for BJT

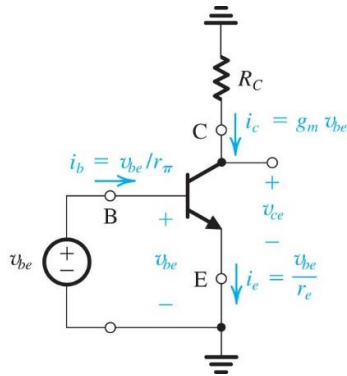



**Figure 6.23** The amplifier circuit of Fig. 6.20(a) with the dc sources ( $V_{BE}$  and  $V_{CC}$ ) eliminated (short-circuited). Thus only the signal components are present. Note that this is a representation of the signal operation of the BJT and not an actual amplifier circuit.

# Hybrid- $\pi$ model for BJT

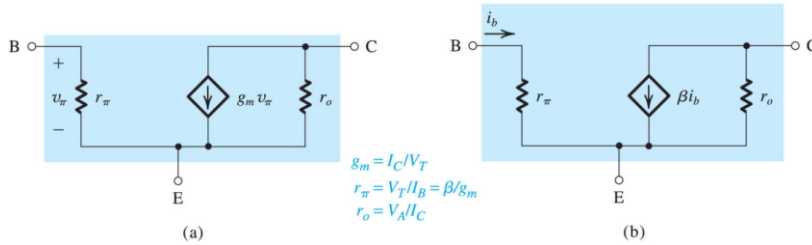

**Figure 6.25** The hybrid- $\pi$  small-signal model, in its two versions, with the resistance  $r_o$  included.

# Applying Small-Signal Model

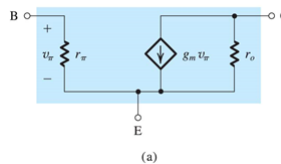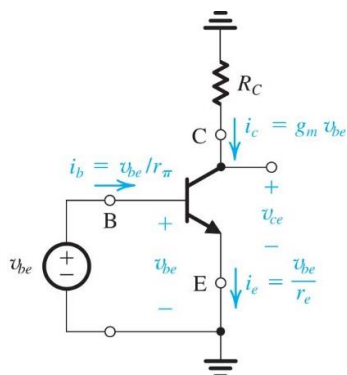

# BJT Amplifier Example

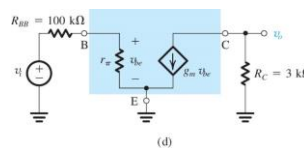
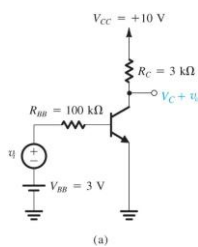


Figure 6.28 Example 6.5: (a) amplifier circuit; (d) amplifier circuit with transistor replaced by its hybrid- $\pi$ , small-signal model.

# Systematic Procedure for Transistor Amplifier Analysis

- 1. Perform **DC analysis** (ignore small signal source)
- 2. Calculate **small-signal parameters** ( $g_m$ ,  $r_{\pi}$ ,  $r_o$ , etc)
- 3. Generate **AC small-signal equivalent circuit**
  - » Replace DC voltage source by short circuit
  - » Replace DC current source by open circuit
  - » Replace transistor by hybrid- $\pi$  model (or other model)
- 4. Perform **circuit analysis** to determine voltage gain or other amplifier performance parameters

## MOSFET Amplifier Example

### (1) Solve DC Bias Point


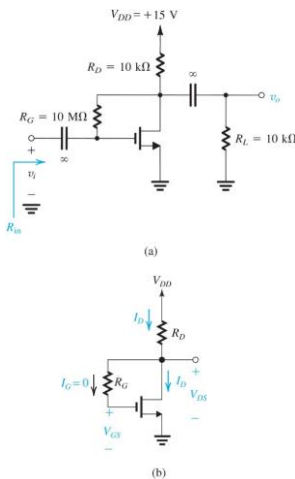


Figure 6.15 Example 6.3: (a) amplifier circuit; (b) circuit for determining the dc operating point;

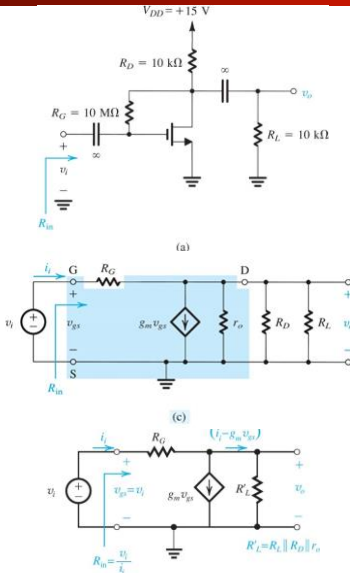

# Continued 1

## (2) Solve AC Small Signal Circuit




© Power Electronics Lab

ShanghaiTech University

# Continued 2

## (3) Additional Parameters of Interest

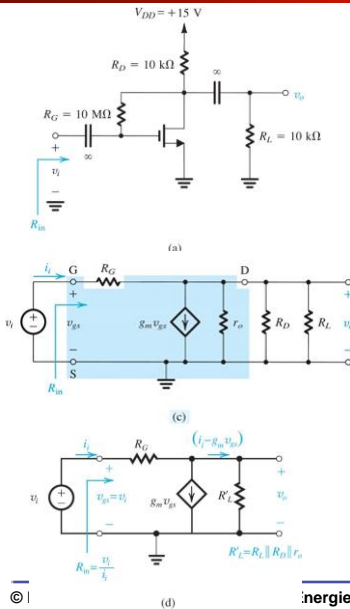

© |

Power Electronics Lab

ShanghaiTech University

# BJT Amplifier Example

## (1) Solve DC Bias Point

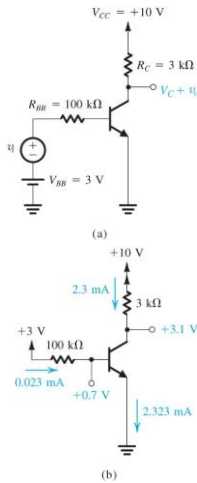


Figure 6.28 Example 6.5: (a) amplifier circuit; (c) amplifier circuit with dc sources replaced by short circuits;

## Continued

## (2) AC Equivalent Circuit

