

EE112 - Fall 2016



Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
5210 Research Bldg.

Purposes of Bias Circuit



- Provide a stable bias drain (collector) current
- Bias insensitive to variations in
 - » Transistor parameters (β for BJT, V_t , k for MOS),
 - » Temperature and other environmental changes
- Keep transistors in flat part of the I-V curves (Saturation for MOS, Active for BJT) for desired output swing

Example of Non-Ideal Bias

  


- Fixed v_{GS} from voltage divider
- Large variation in i_D due to device variations
- Large temperature dependence
 - » μ_n and V_t are temperature sensitive

Adding Source Resistance R_S

  


- R_S provides a negative feedback
 - » If I_D increases, V_{GS} decreases -> reduce I_D
 - » If I_D decreases, V_{GS} increases -> increase I_D
- Stabilize I_D w.r.t. device and temperature variations


Practical Implementations

 

Single Power Supply

 


Dual Power Supply

 

Drain-to-Gate Feedback

 
Coupling Capacitor to Separate AC Signal from DC Bias





- Coupling capacitor is DC-open and AC-short
- Prevent signal source to change bias condition
- The coupling capacitor creates a lower bound of operating frequency

Bias Design Example


 
Goal: design bias for $I_D = 0.5 \text{ mA}$.
 MOS has $V_t = 1 \text{ V}$ and $k_n = 1 \text{ mA/V}^2$



Non-Ideal Biasing Schemes for BJT

  

Good (Stable) Biasing Circuits for BJT

  

- Similar to MOSFET bias, but must consider finite base current:
- First, find Thevenin equivalent circuit of bias circuit:

Design Example of BJT Bias

Goal: design bias circuit for $I_E = 1$ mA with $V_{CC} = 12$ V and $\beta = 100$

