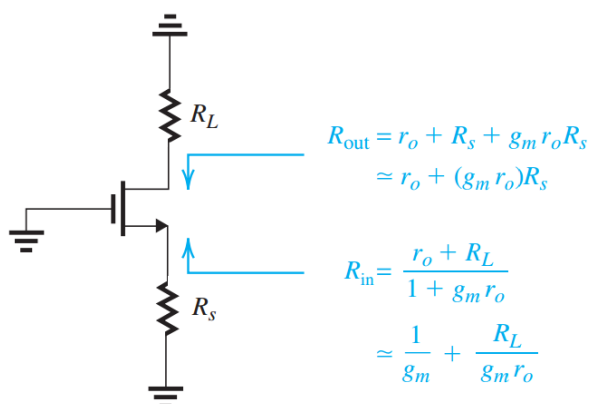


# EE112 - Fall 2016


## Analog Integrated Circuits I

Prof. Haoyu Wang  
[wanghy@shanghaitech.edu.cn](mailto:wanghy@shanghaitech.edu.cn)  
 5210 Research Bldg.



## Impedance Transformation of Common Gate Amplifier




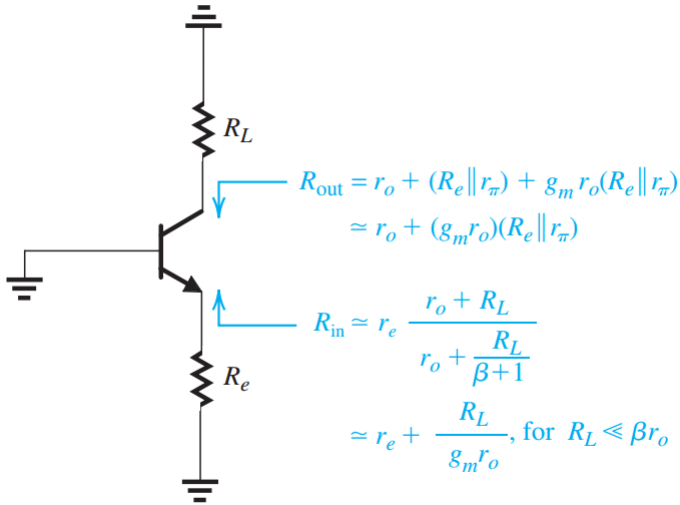
# Impedance Transformation of Common Base Amplifier





# MOS Cascode

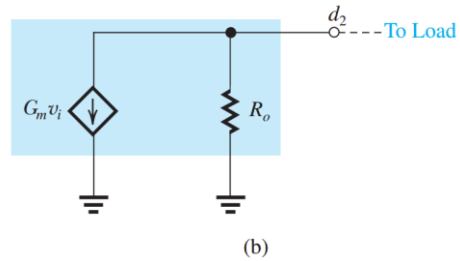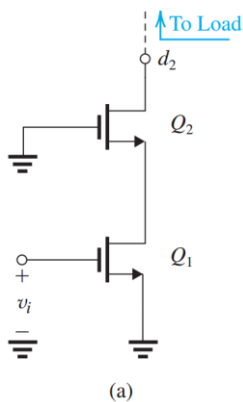



# Continued/ $G_m$

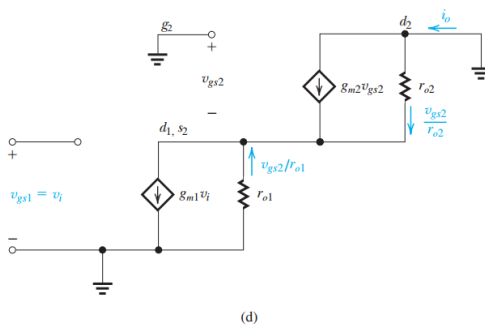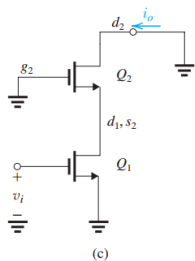



# Continued/ $R_o$

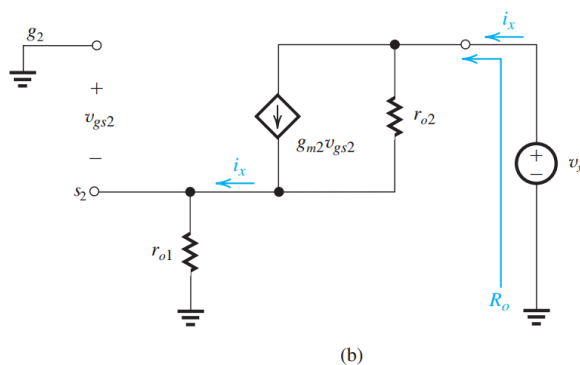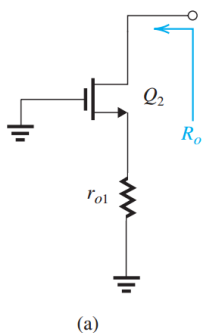



# MOS Cascode Amplifier

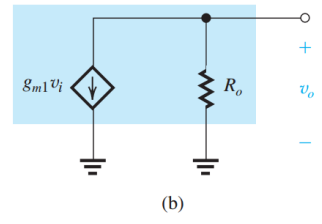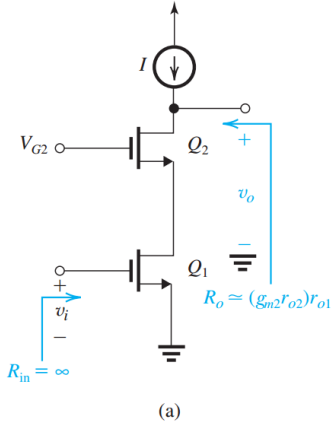

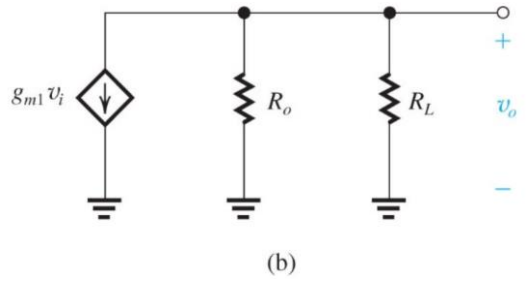
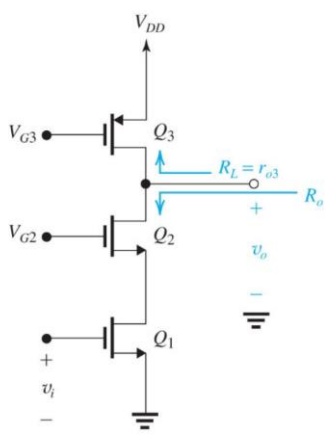
# Cascode Amplifier with Simple Active Load



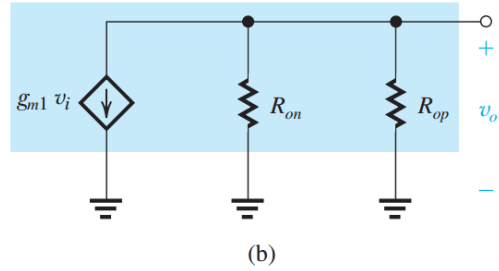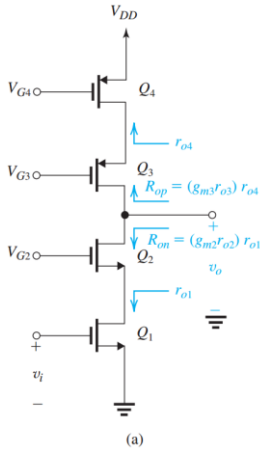
# Cascode Amplifier with Cascode Current-Source Load


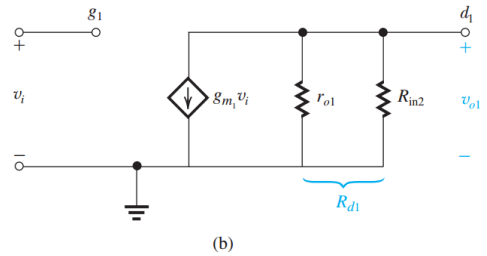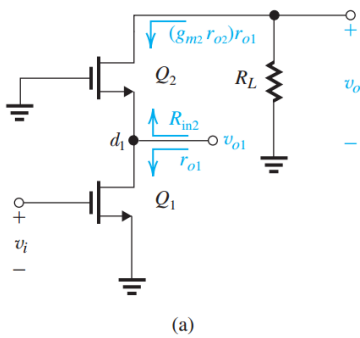
# Think of Cascode as Multistage Amplifier with CS followed by CG



# The Folded Cascode

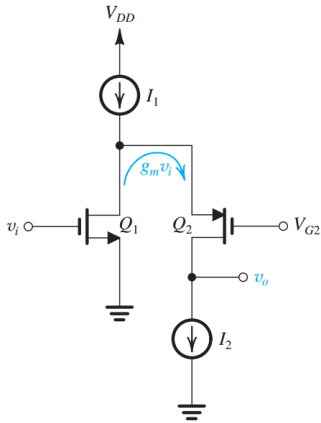


Folding the CG stage using PMOS

- $Q_2$  is biased with  $I_2$
- $Q_1$  is biased with  $I_1 - I_2$


Folded cascode avoids stacking too many transistors vertically, which will be difficult for low  $V_{DD}$

# Useful Transistor Pairings

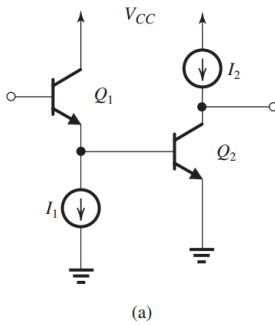


CC+CE

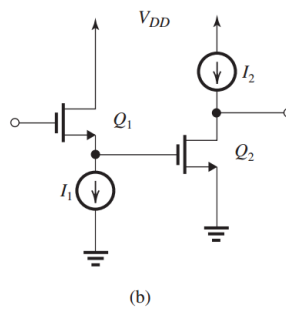- High  $R_{in}$
- Much wider bandwidth than single CE



CD+CS

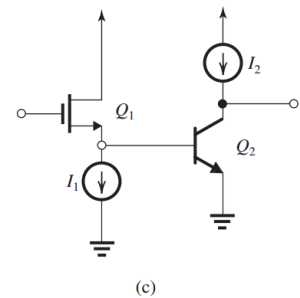
- Main benefit is wider bandwidth than single CS



CD+CE (BiCMOS)

- Similar to MOS version
- Higher  $g_m$


# Darlington Pair

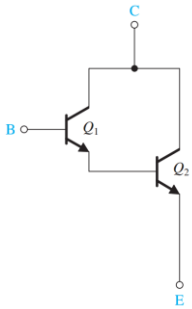

(a)
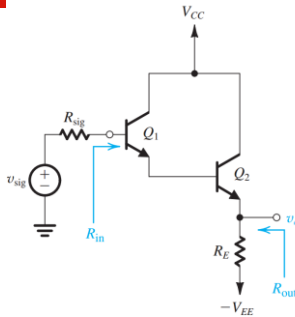
## Darlington pair


- Composite BJT with  $\beta = \beta_1 \beta_2$



(b)

## CC+CC

high performance emitter follower

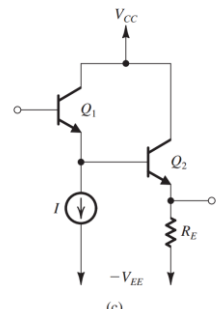

(c)

## CC+CC

high performance emitter follower with separate current bias for  $Q_1 \rightarrow$  high  $\beta_1$