

# EE112 - Fall 2016

## Analog Integrated Circuits I


Prof. Haoyu Wang  
[wanghy@shanghaitech.edu.cn](mailto:wanghy@shanghaitech.edu.cn)  
5210 Research Bldg.

## Why Differential?

- Differential circuits are much **less sensitive** to noises and interferences
- Differential configuration enables us to bias amplifiers and connect multiple stages without using coupling or bypass capacitors
- Differential amplifiers are widely used in IC's
  - » Excellent matching of transistors, which is critical for differential circuits
  - » Differential circuits require more transistors-not an issue for IC

# MOS Differential-Pair


## Basic Configuration

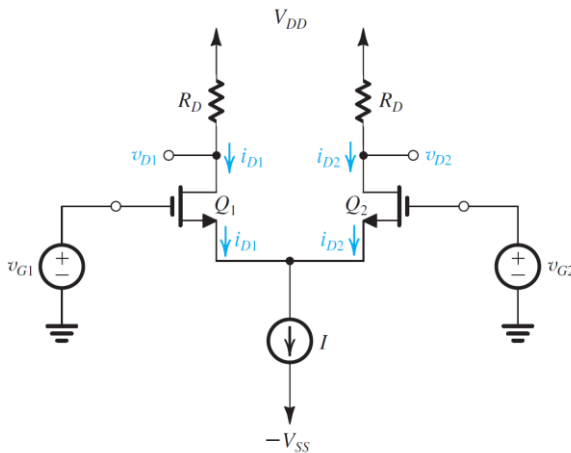

- Two matched MOS transistors Common current bias.
- “Differential signals” applied to  $v_{G1}$  and  $v_{G2}$  (equal amplitude but opposite sign).
- “Differential outputs” are produced at  $v_{D1}$  and  $v_{D2}$ .
- Note: in differential configuration with 0 differential input,  $V_{GS}$  is fixed for both  $Q_1$  and  $Q_2$ .

## Continued

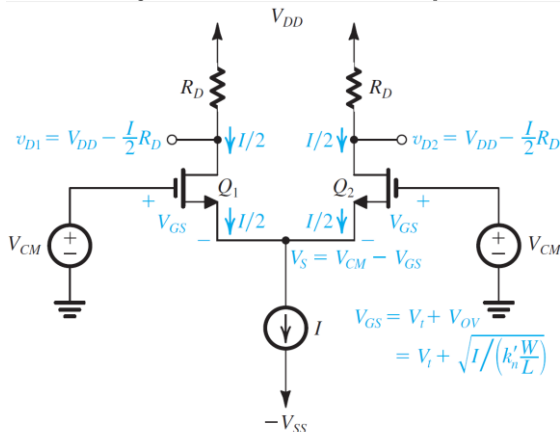
### Differential Pair Rejects Common-Mode Inputs






- The common voltages applied to both  $Q_1$  and  $Q_2$  are referred to as common mode,  $V_{CM}$ .
- Common mode inputs usually come from noises or interferences.
- Differential pair should reject  $V_{CM}$ :
  - » Since  $V_{GS1} = V_{GS2} = V_{tn} + \sqrt{I/k_n}$  is fixed in differential pair,
  - »  $V_{CM}$  simply changes the voltage at Source,  $V_S$ .
- The drain currents remain fixed:
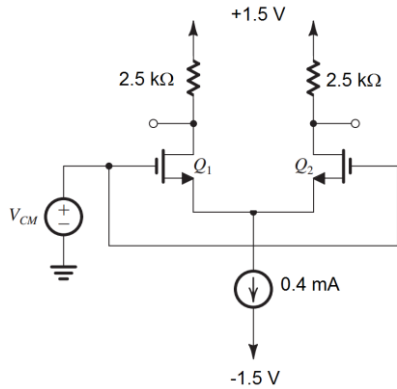
# Example


- $V_{DD} = V_{SS} = 1.5V$ ,  $I = 0.4mA$ ,  $R_D = 2.5k\Omega$ . Minimum voltage across current source  $V_{CS} = 0.4V$ . For  $Q_1$  and  $Q_2$ :  $k_n = 4 mA/V^2$ ,  $V_{th} = 0.5V$ .
- Find  $V_S$ ,  $I_{D1}$ ,  $I_{D2}$ ,  $V_{D1}$ ,  $V_{D2}$  for 3 different  $V_{CM}$  below:




# Continued

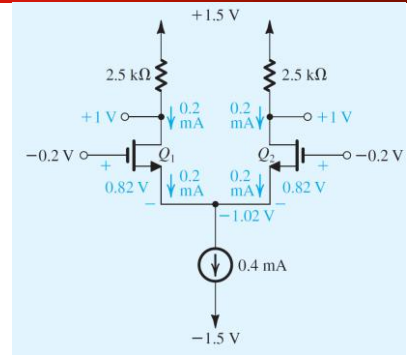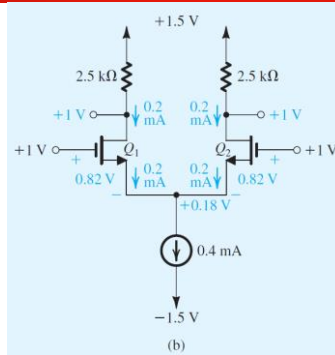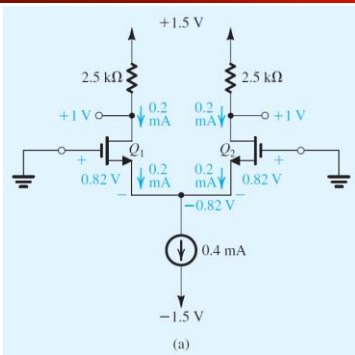

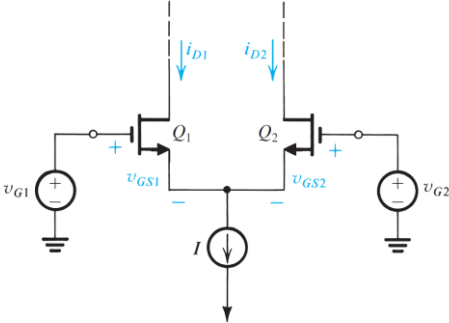
# Operation with Differential Input Voltage


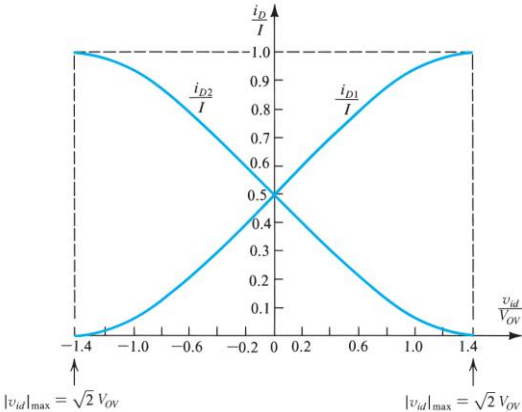
# Operation with Differential Input Voltage




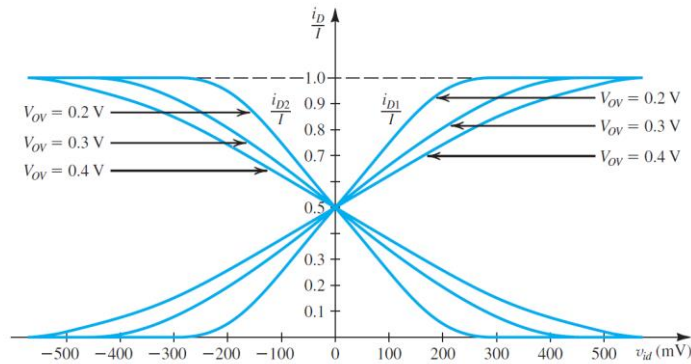
# Current of Differential Pair for Various Overdrive Voltage




- The linear range of operation of the MOS differential pair can be extended by operating the transistor at a higher value of  $V_{OV}$

# Small Signal Operation

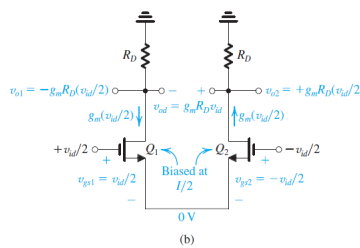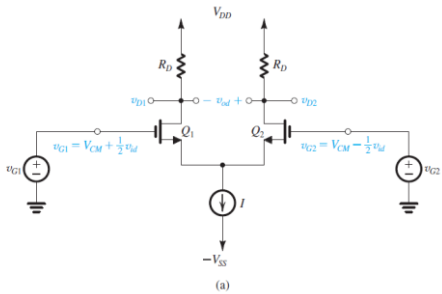


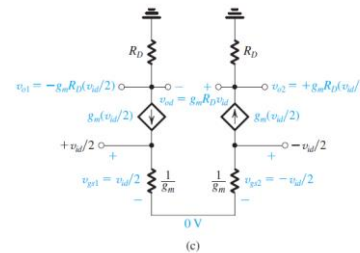For **differential AC small signal**, the differential pair is “anti-symmetric”. The potential at the mid point (Source) is zero. This is called “**Virtual Ground**”




This virtual ground is obtained without using a large bypass capacitor -> much smaller area and better frequency response

# Differential Half Circuit

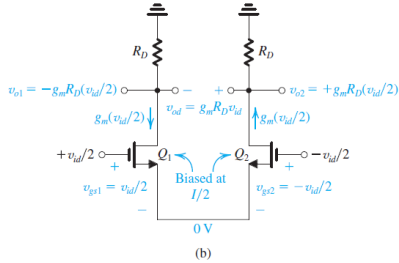


- Because the two halves of the circuits are anti-symmetric, and Source is at virtual ground, we can simplified and just analyze the "half circuit"
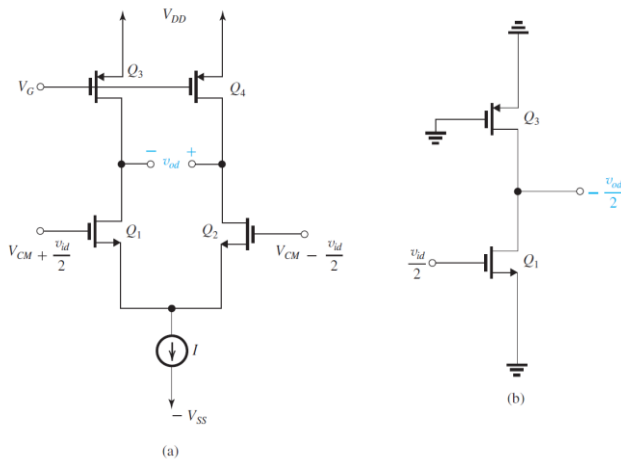
# Differential Amplifier with Current-Source Loads



# Cascode Differential Amplifier

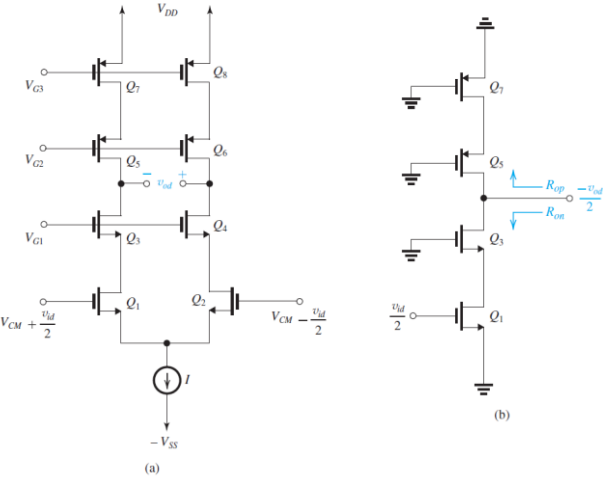

- Cascode configurations for both amplifying transistors and current source loads.