 


EE112 - Fall 2016


Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
 5210 Research Bldg.


Two-Stage CMOS Op-Amp Circuit



Stages Scrutinize

 

Voltage Gains

 

- Voltage gain of the first stage (Q_1, Q_2): Differential input, single-ended output:

$$A_1 = -g_{m1}(r_{o2} \parallel r_{o4})$$

- Voltage gain of the 2nd stage (Q_6): Common source with current source load:


$$A_2 = -g_{m6}(r_{o6} \parallel r_{o7})$$

- Total gain

$$A_o = A_1 A_2$$


Example:

Transistor	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈
W/L	20/0.8	20/0.8	5/0.8	5/0.8	40/0.8	10/0.8	40/0.8	40/0.8

 


- $I_{REF} = 90 \mu A$, $V_{tn} = 0.7 V$, $V_{tp} = -0.8 V$, $\mu_n C_{ox} = 160 \mu A/V^2$, $\mu_p C_{ox} = 40 \mu A/V^2$, $|V_A| = 10 V$ for all devices $V_{DD} = V_{SS} = 2.5 V$.
- Find I_D , $|V_{OV}|$, $|V_{GS}|$, g_m , r_o for all Q's, voltage gain, input common mode range, output voltage range.


Solution: DC Parameters

 


Solution: AC Parameters

 


Solution: Input Common-Mode Ranges

 


Solution: Output Ranges

 

A Four-Stage Bipolar Op-Amp

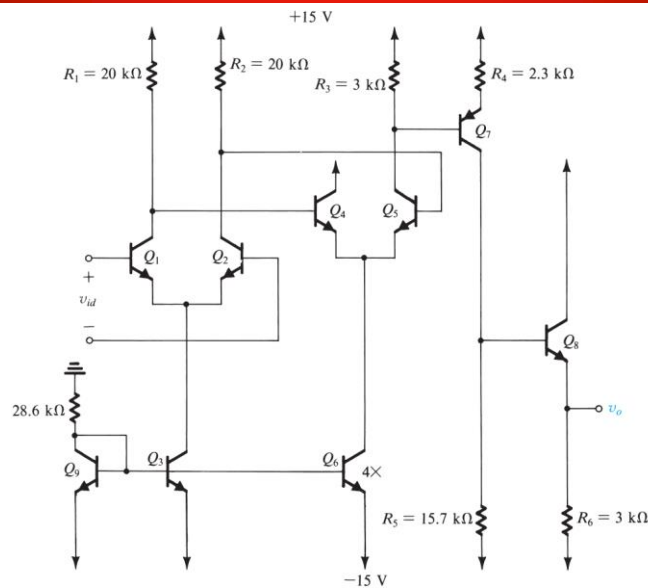

Stages Scrutinize

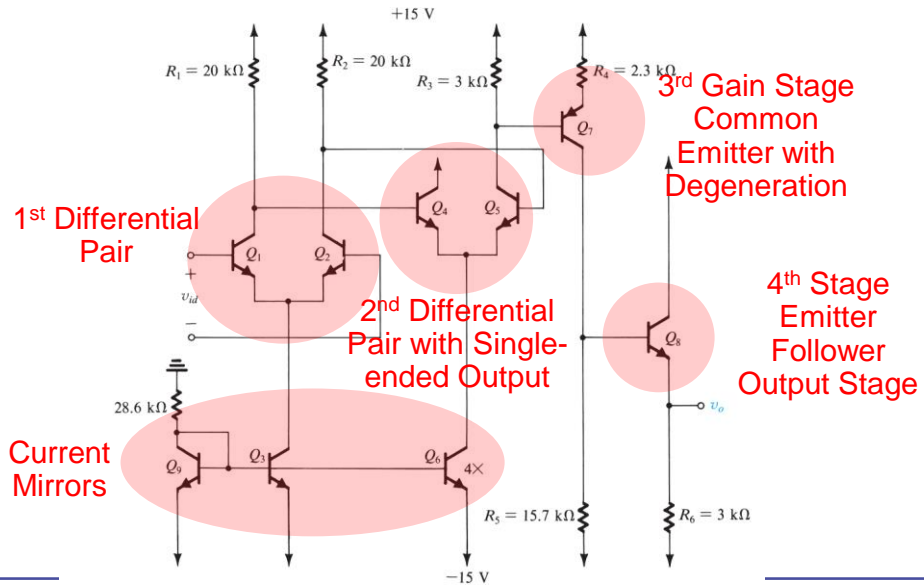

DC Solution

