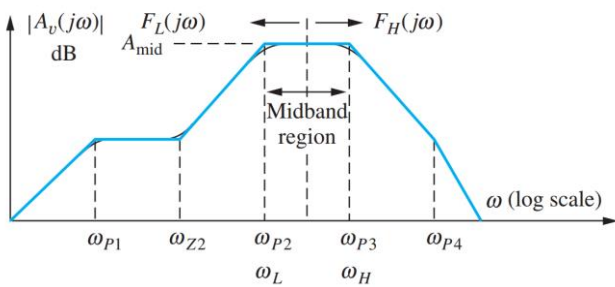


EE112 - Fall 2016


Analog Integrated Circuits I

Prof. Haoyu Wang
wanghy@shanghaitech.edu.cn
 5210 Research Bldg.

Amplifier Frequency Response Transfer Function Analysis



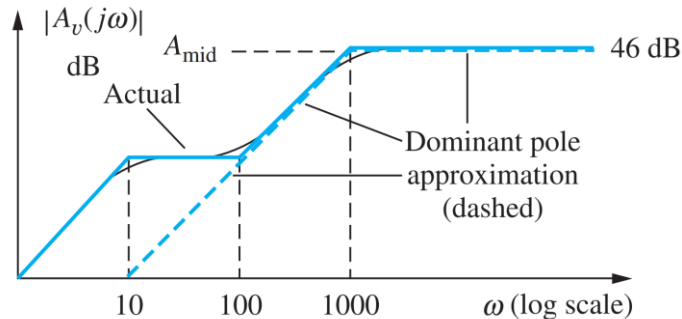- A **Dominant Pole** exists if one of the low frequency poles is much larger than the others.



- » In the graph below case $\omega = 1000$ rad/sec is a dominant pole.
- » All other poles and zeros are at low enough frequencies that they do not affect the lower cutoff frequency ω_L .

- If there is no dominant pole at low frequencies, the poles and zeros interact to determine the lower cutoff frequency ω_L .
- Lower cutoff frequency ω_L will be greater than all the individual pole zero frequencies.

Dominate Pole Example

- Problem: Find midband gain, $F_L(s)$ and f_L for


$$A_L(s) = 2000 \frac{s \left(\frac{s}{100} + 1 \right)}{(0.1s + 1)(s + 1000)}$$

- Analysis:


High-Frequency Dominate Pole

- The lowest of all high frequency poles is called the dominate high-frequency pole
- If there is no dominant pole at high frequencies, the poles and zeros interact to determine ω_H

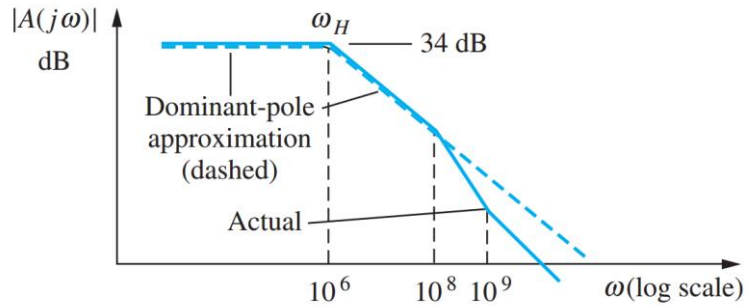
High Frequency Dominate Pole Approximation



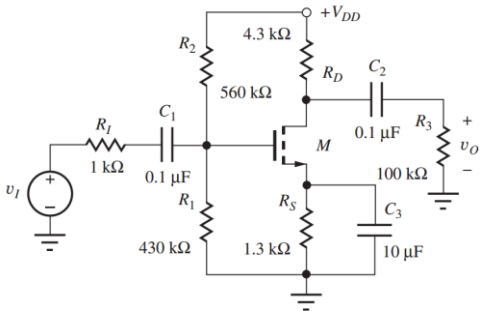Low-Frequency Poles and Zeros Direct Calculation: C-S Amplifier



(a)

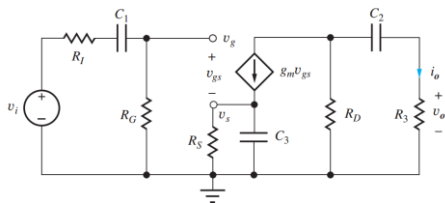

(c)

Continued

- Each independent capacitor in the circuit contributes one pole and one zero.
- Series capacitors C_1 and C_3 contribute the two zeros at $s = 0$ (dc), blocking propagation of dc signals through the amplifier.
- The third zero due to the parallel combination of C_2 and R_S occurs at frequency where signal current propagation through the MOSFET is blocked (output voltage is zero).