

EE112 Analog Integrated Circuits I

Homework 6

Due: Nov 17th before lecture

Read the chapter 7.

1. Various measurements are made on an NMOS amplifier for which the drain resistor R_D is $20\text{ k}\Omega$. First, dc measurements show the voltage across the drain resistor, V_{R_D} , to be 1.5 V and the gate-to-source bias voltage to be 0.7 V . Then, ac measurements with small signals show the voltage gain to be -10 V/V . What is the value of V_t for this transistor? If the process transconductance parameter k_n' is $200\text{ }\mu\text{A/V}^2$, what is the MOSFET's W/L ?
2. For the amplifier circuit in Fig. 1 with $V_{CC} = +5\text{ V}$ and $R_C = 1\text{ k}\Omega$, find V_{CE} and the voltage gain at the following dc collector bias currents: 0.5 mA , 1 mA , 2.5 mA , 4 mA , and 4.5 mA . For each, give the maximum possible positive- and negative-output signal swing as determined by the need to keep the transistor in the active region. Present your results in a table.

 


Figure 1

3. Consider the FET amplifier of Fig. 2 for the case $V_t = 0.4\text{ V}$, $k_n = 5\text{ mA/V}^2$, $V_{GS} = 0.6\text{ V}$, $V_{DD} = 1.8\text{ V}$, and $R_D = 10\text{ k}\Omega$.
 - (a) Find the dc quantities I_D and V_{DS} .
 - (b) Calculate the value of g_m at the bias point.
 - (c) Calculate the value of the voltage gain.
 - (d) If the MOSFET has $\lambda = 0.1\text{ V}^{-1}$, find r_o at the bias point and calculate the voltage gain.

 


Figure 2

4. For the NMOS amplifier in Fig. 3, replace the transistor with its T equivalent circuit, assuming $\lambda = 0$. Derive expressions for the voltage gains v_s/v_i and v_d/v_i .

 


Figure 3