

# EE270 Homework 4

Due April 18th, 2017 @ class

**Read** Erickson textbook, Chapter 7.

**Problems 1-3** Erickson textbook, problems 7.1, 7.10, 7.14.

**Problem 4** Given a buck converter.  $f_s = 10kHz$ ,  $R = 1.5\Omega$ ,  $C = 800\mu F$ . Time range is  $[0, 0.04]$  seconds.

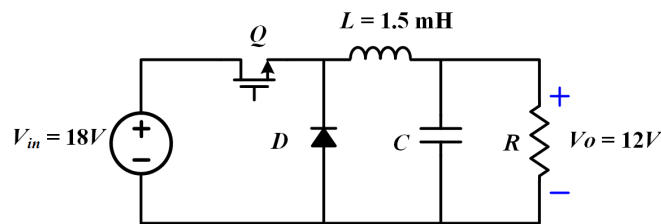


Figure 1: fig

a) Express the circuit operation in matrix form utilizing GSSA technique.

b) Assume the initial condition of the state vector is

$$X_{initial} = [x_1, x_2, x_3, x_4, x_5, x_6]_{initial}^T = [1, 1, 1, 1, 1, 1]^T \quad (1)$$

Write a program in Matlab to solve  $v_o(t)$  and  $i_L(t)$ .

c) Plot  $v_o(t)$  and  $i_L(t)$  in Matlab.