


SI100B
**Introduction to Information
Science and Technology**
**(Part 3: Electrical
Engineering)**

Lecture #5 (Digital)
Sequential Logic Circuits #2

Instructor: Haoyu Wang(王浩宇)

Apr 18th, 2023

The Theme Story

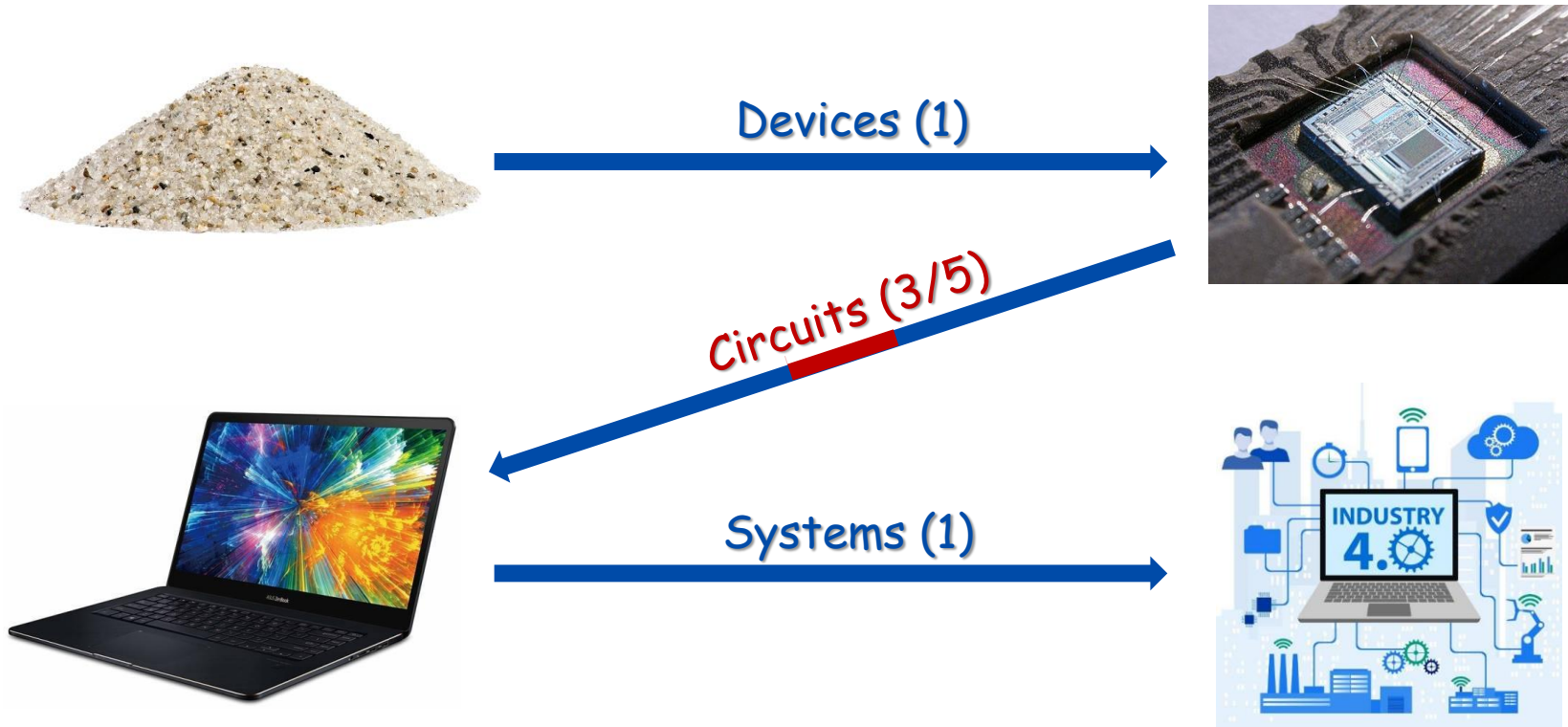

(Figures from Internet)

Study Purpose of Lecture #5

- 哲学三问
 - Who are you?
 - Where are you from?
 - Where are you going?


To answer those questions
throughout your life

你要到哪里去?
你从哪儿来?
你是谁?
哲学终极问题



(Figures from Internet)

 - In this lecture, we ask
 - What is **synchronous sequential circuit**?
 - How do we realize **memory array**?
 - How to use **finite state machine** to build useful applications?




Lecture Outline


- Synchronous sequential circuit
 - The evolution of flip-flops
 - Synchronous and asynchronous circuits
 - Example: 4 x 3 memory
- Memory Array
- Finite state machines (FSM)
 - Traffic light example

Synchronous and asynchronous circuits

- Synchronous circuit

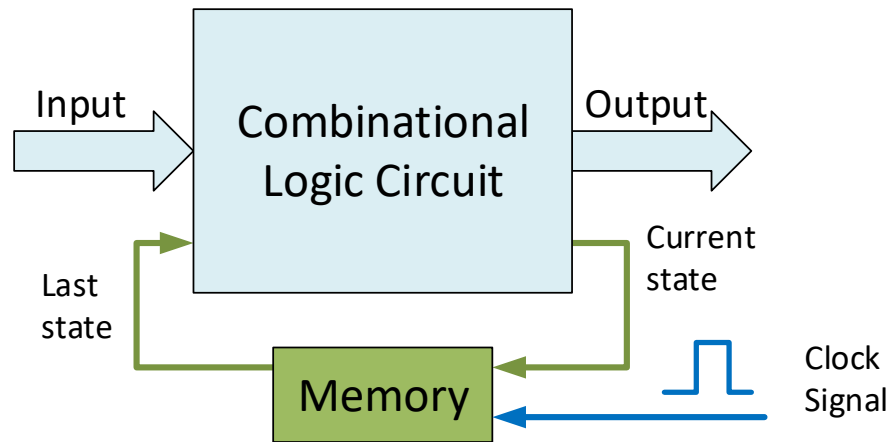


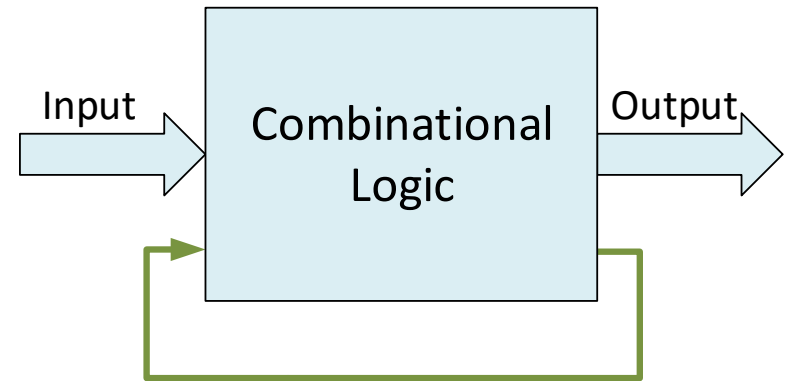- Asynchronous circuit or self-timed circuit




Synchronous and asynchronous circuits

• Synchronous circuit

 

- Common **clock signal**
- Output only change at the **edge** of clock pulse
- clock signal should be long enough so that the **critical path** can settle before next clock edge
- Easy design

 
• Asynchronous circuit or self-timed circuit



- Not governed by global clock
- Resulting state can be sensitive to the relative arrival times of inputs at gates, the **race condition**



Delay in combinational circuit

 - contamination delay t_{cd}
 - Y (output) starts to change after the change of A (input)
- propagation delay t_{pd}
 - Y (output) definitely settles in new value





Racing condition

- In combinational circuit

  



Racing condition

- In combinational circuit

  

- In asynchronous sequential circuit
  
$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$



- $D = 1$
 $CLK = 1; \overline{CLK} = 0$
 $Q_{prev} = 1 \cdot 1 + 0 \cdot X = 1$
- $CLK = 1 \rightarrow 0; \overline{CLK} = 1$
 $Q = 1 \cdot 0 + 1 \cdot 1 = 1$
- Suppose the delay through the inverter from CLK to \overline{CLK} is rather long compared to the delays of the AND and OR gates
- **eventually $Q=0$ because of the race condition**

Rules of synchronous sequential circuit

- Every circuit element is either a **register** or a **combinational** circuit
- At least one circuit element is a **register**
- All registers receive the **same clock signal**
- Every cyclic path contains **at least one register**

Example: 2 x 2 memory


- **2 words** and each can store **2 bits** of information
- To represent **2 words** need **1-bit** for address
 - Address decoder performs the address decoding
- To store information we use **D Flip-Flop** for each bit (total 4, as each location as **2 bits** and we have **2 total locations**)
- Need select variable to chose if we want to **read** or **write** data and that is combined with clock signal (using some combinational logic)
- Also need some other combinational logic...

Example: 2 x 2 memory

Example: 4 x 3 memory


- **4 words** and each can store **3 bits** of information
- To represent **4 words** need **2-bits** for address
 - Address decoder performs the address decoding
- To store information we use **D Flip-Flop** for each bit (total 12, as each location as **3 bits** and we have **4 total locations**)
- Need select variable to chose if we want to **read** or **write** data and that is combined with clock signal (using some combinational logic)
- Also need some other combinational logic...

Example: 4 x 3 memory

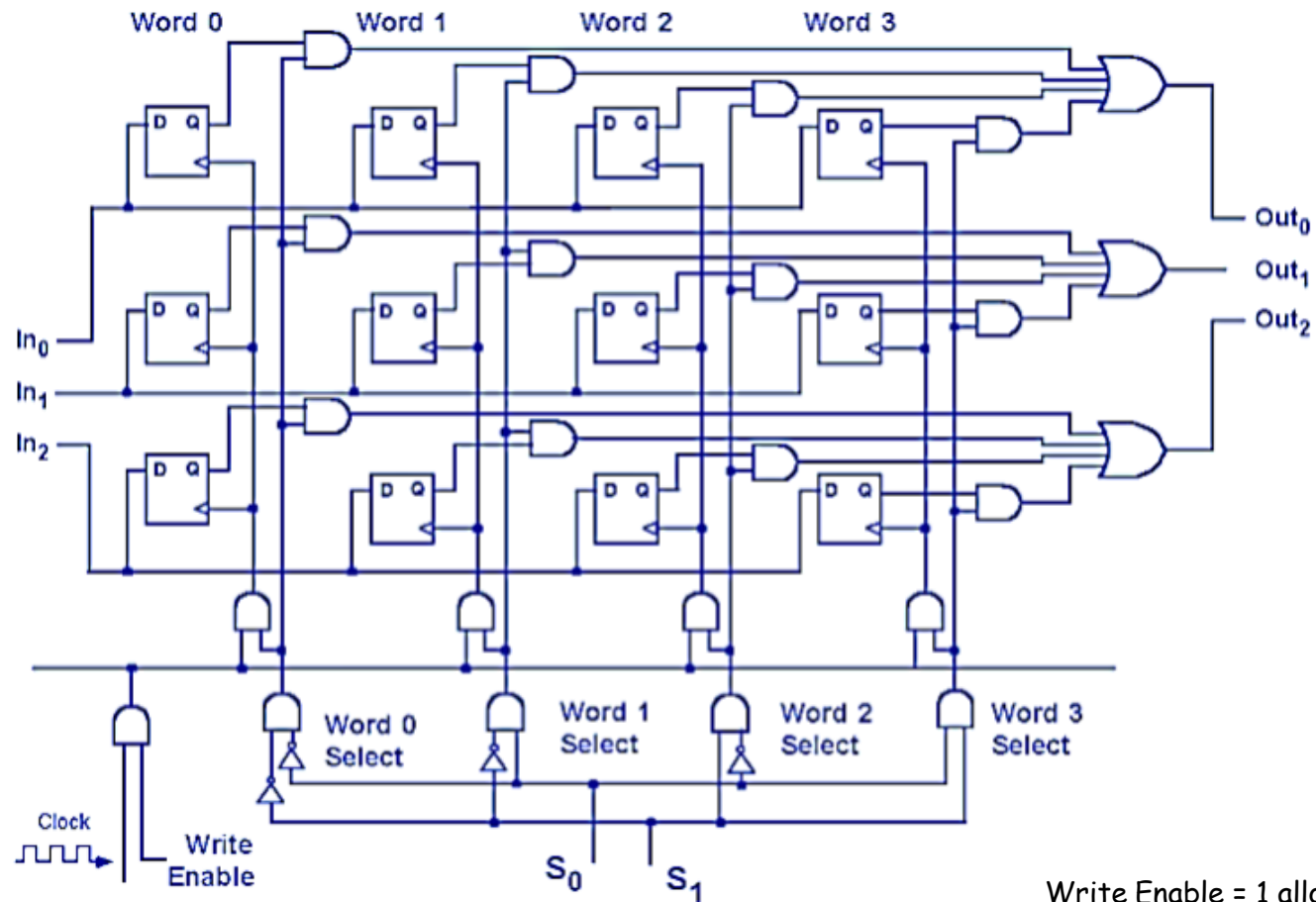


Write Enable = 1 allows memory write
Write Enable = 0 allows memory read

Write operation to word 1

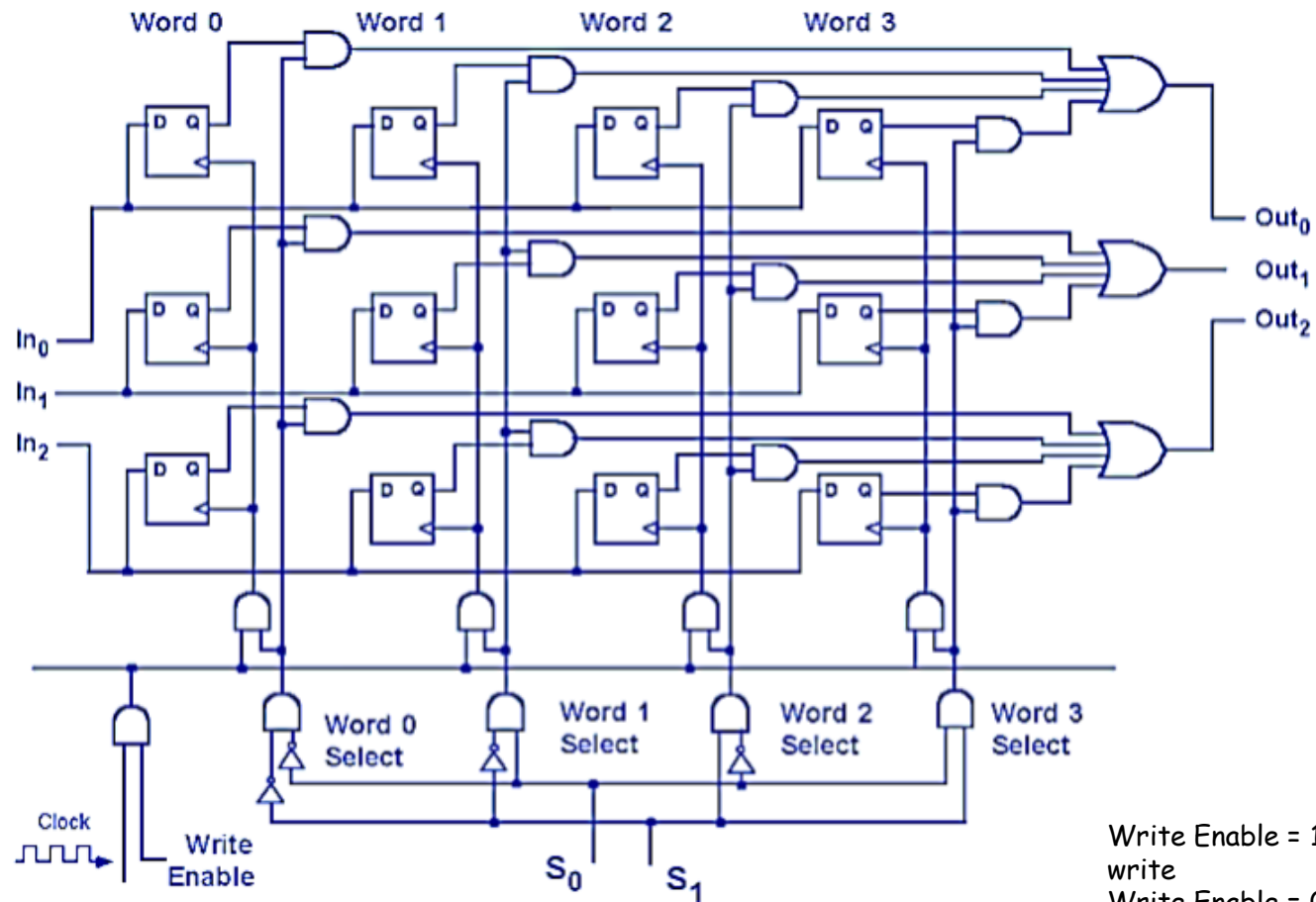

Write Enable = 1 allows memory write
 Write Enable = 0 allows memory read


Read operation from word 3

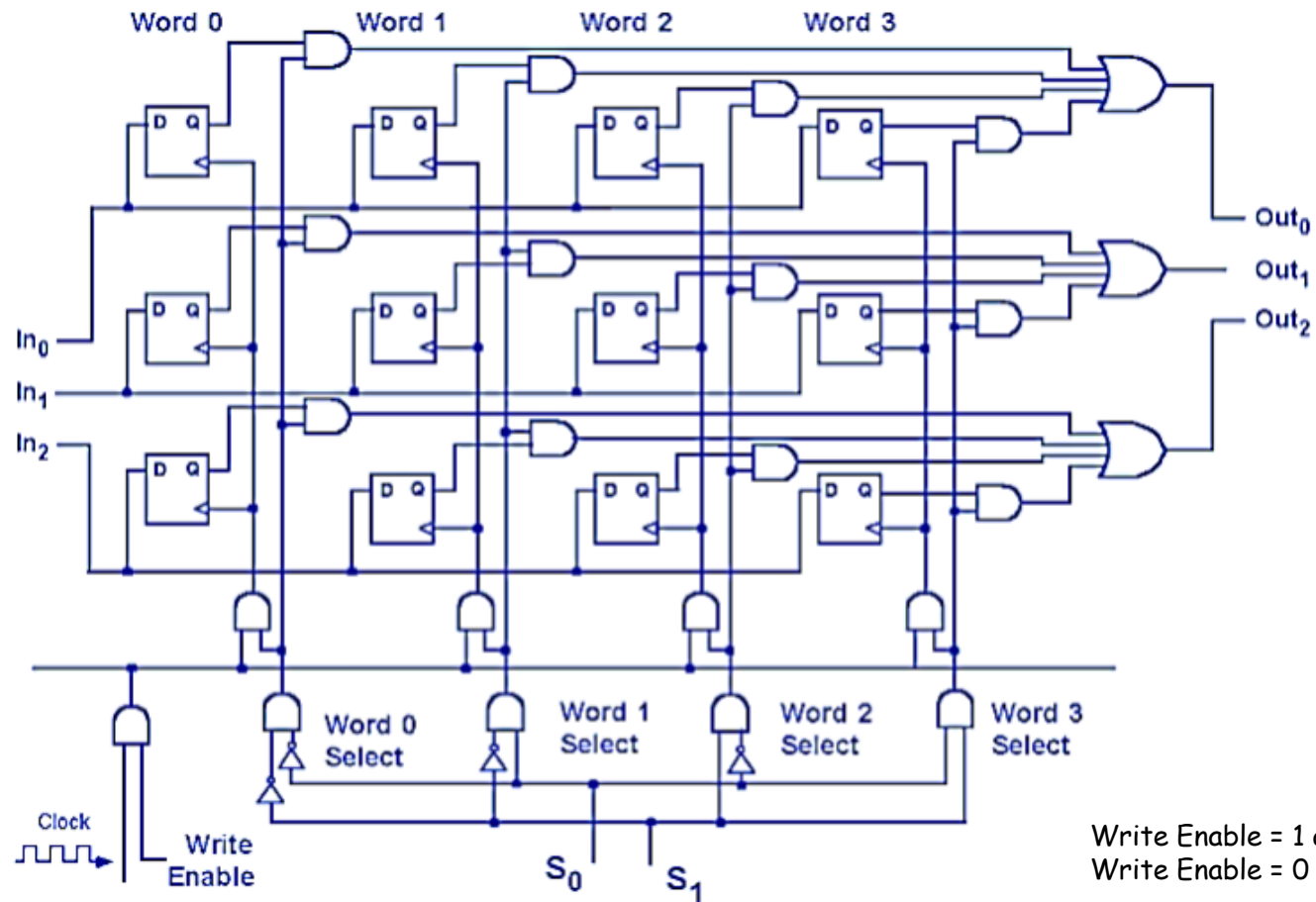


Memory array

- Two-dimensional array of memory cells
- The row is specified as *Address*
- Each row of data is called a *Word*
- The array contains 2^N *M-bit* words
- *Depth* = 2^N
- *Width* = 2^M
- Types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)
 - etc.


General symbol

 

Bit cell

 


Example: 4 × 3 Memory Array

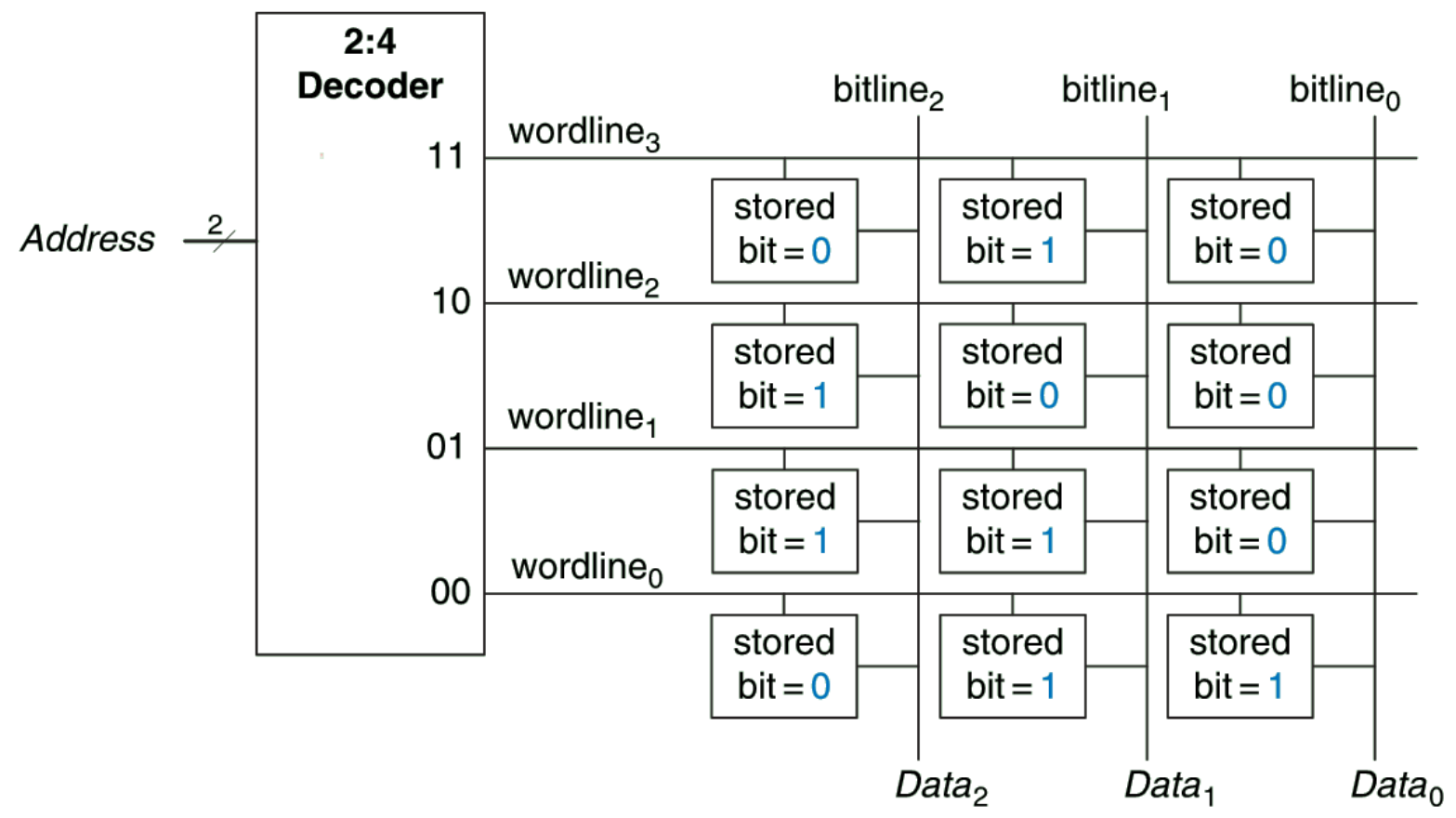


Volatile memory

- Static Random Access Memory (SRAM)


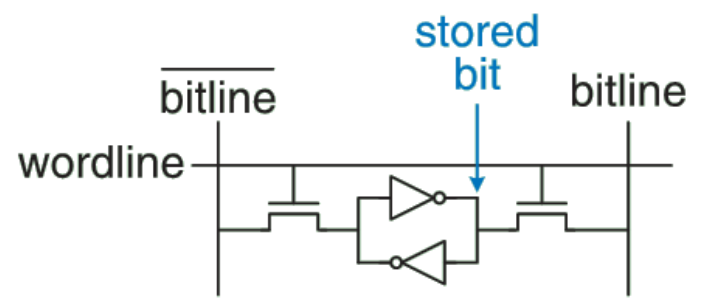


- Dynamic Random Access Memory (DRAM)


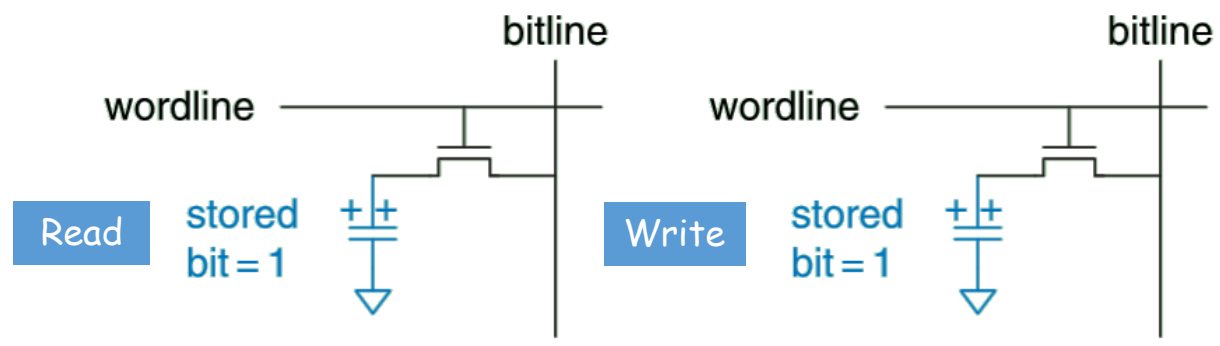


Nonvolatile memory

- Read only memory (ROM)

  

ROM bit cells

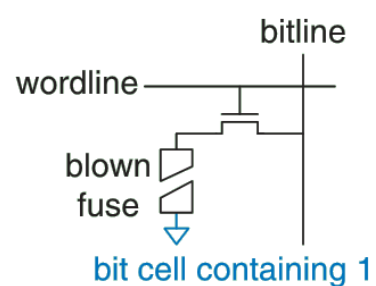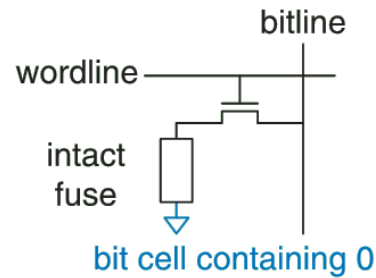

Programmable ROM

- Modern ROMs can be programmed (written) as well. For example flash memory
- Generally, ROMs take a longer time to write than RAMs, but are nonvolatile.

Memory comparison


- The best memory type for a particular design depends on the *speed*, *cost*, and *power constraints*.

Memory Type	Transistors per Bit Cell	Latency
flip-flop	~20	fast
SRAM <i>register, cache</i>	6	medium
DRAM <i>main memory</i>	1	slow




Finite-state machine

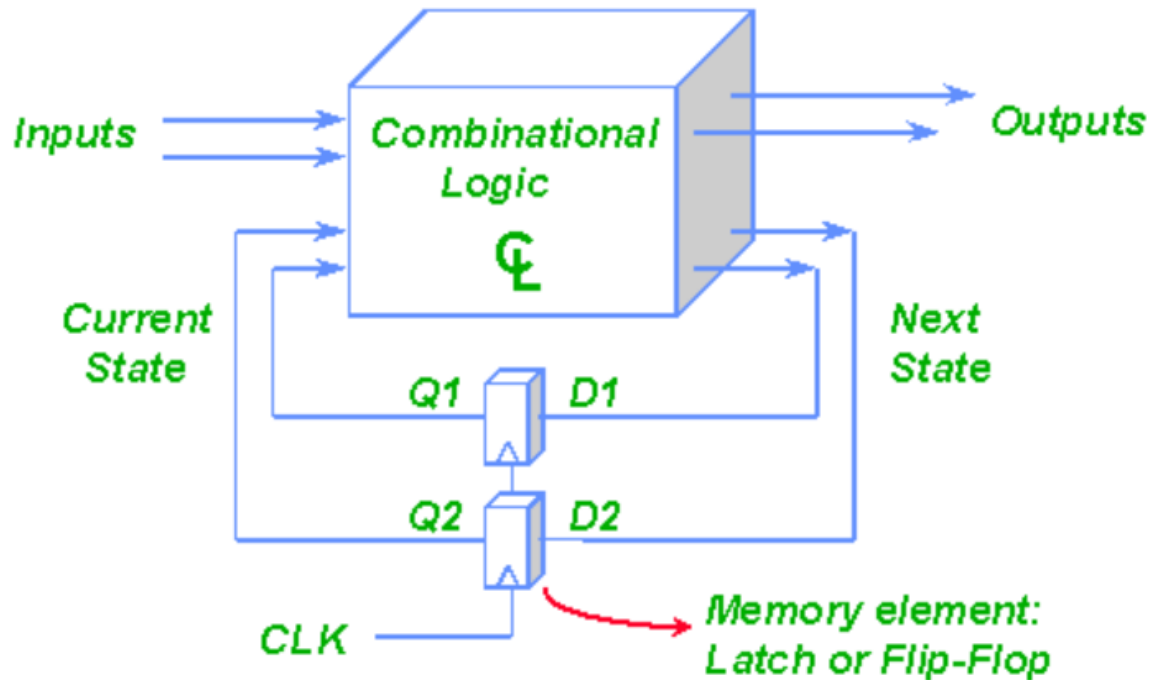
- FSM - a **mathematical model of computation** used to design both computer programs and sequential logic circuits




The most seen FSM

 

Moore machine

 


Mealy machine

 


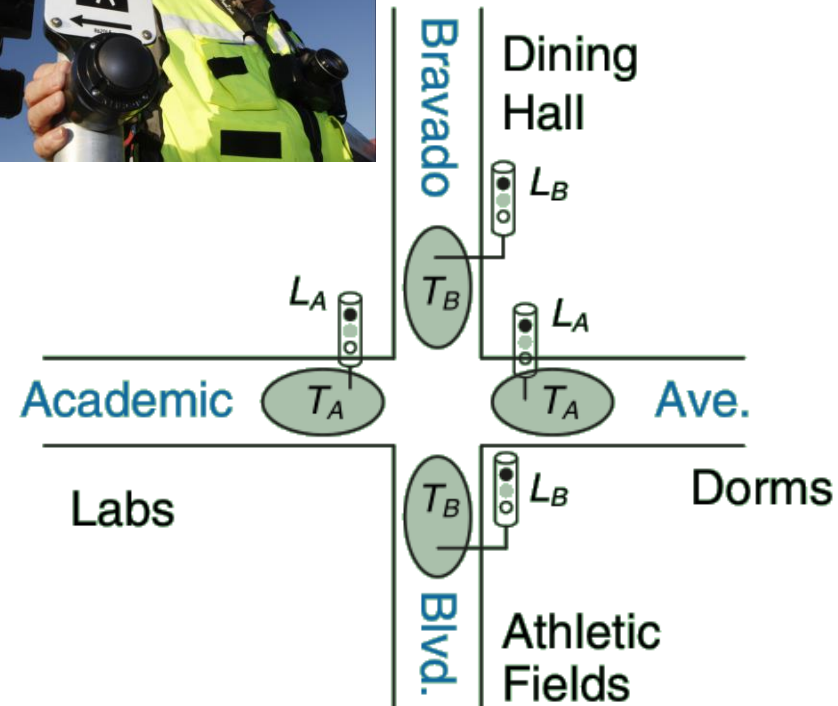Example: traffic light controller



- **Traffic sensors** T_A and T_B ("1" busy, "0" empty)
- **Traffic lights** L_A and L_B (each light have red, yellow, and green)
- **5-second clock**, at each rising edge, lights may change based on the sensors
- **Reset button**



Black box view

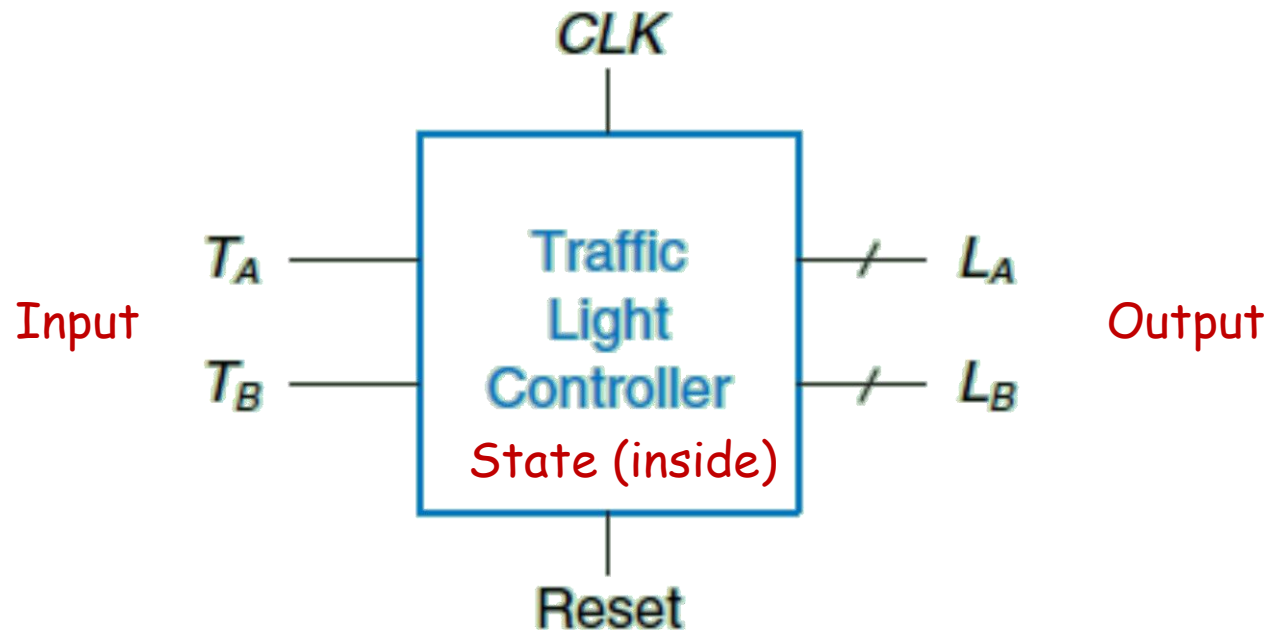


State transition diagram

  

State table

State encoding

State	Encoding $S_{1:0}$
S0	00
S1	01
S2	10
S3	11

 

State transition table

Current State S	Inputs T_A T_B		Next State S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

Binary encoded state transition table

Current State S_1 S_0		Inputs T_A T_B		Next State S'_1 S'_0	
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

Output table


Output encoding

Output	Encoding $L_{1:0}$
green	00
yellow	01
red	10



Output table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

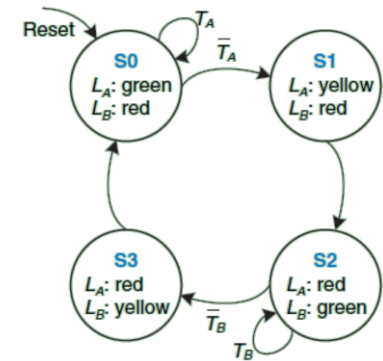

Sum-of-product form

State table



Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

Output

State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1


State & output logic

  - State logic (sequential)
- Output Logic (combinational)




FSM with more states

 Finite State Machine:
Soda Machine State Diagram



FSM with more states

- Digital clock

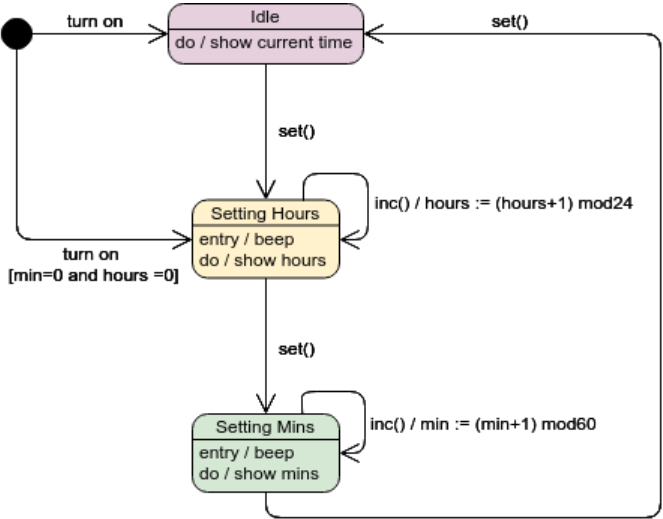

- Microwave oven

