


SI100B
Introduction to Information
Science and Technology
(Part 3: Electrical Engineering)

Lecture #6 Analog Circuits

Instructor: Haoyu Wang(王浩宇)

Apr 20th, 2023

The Theme Story

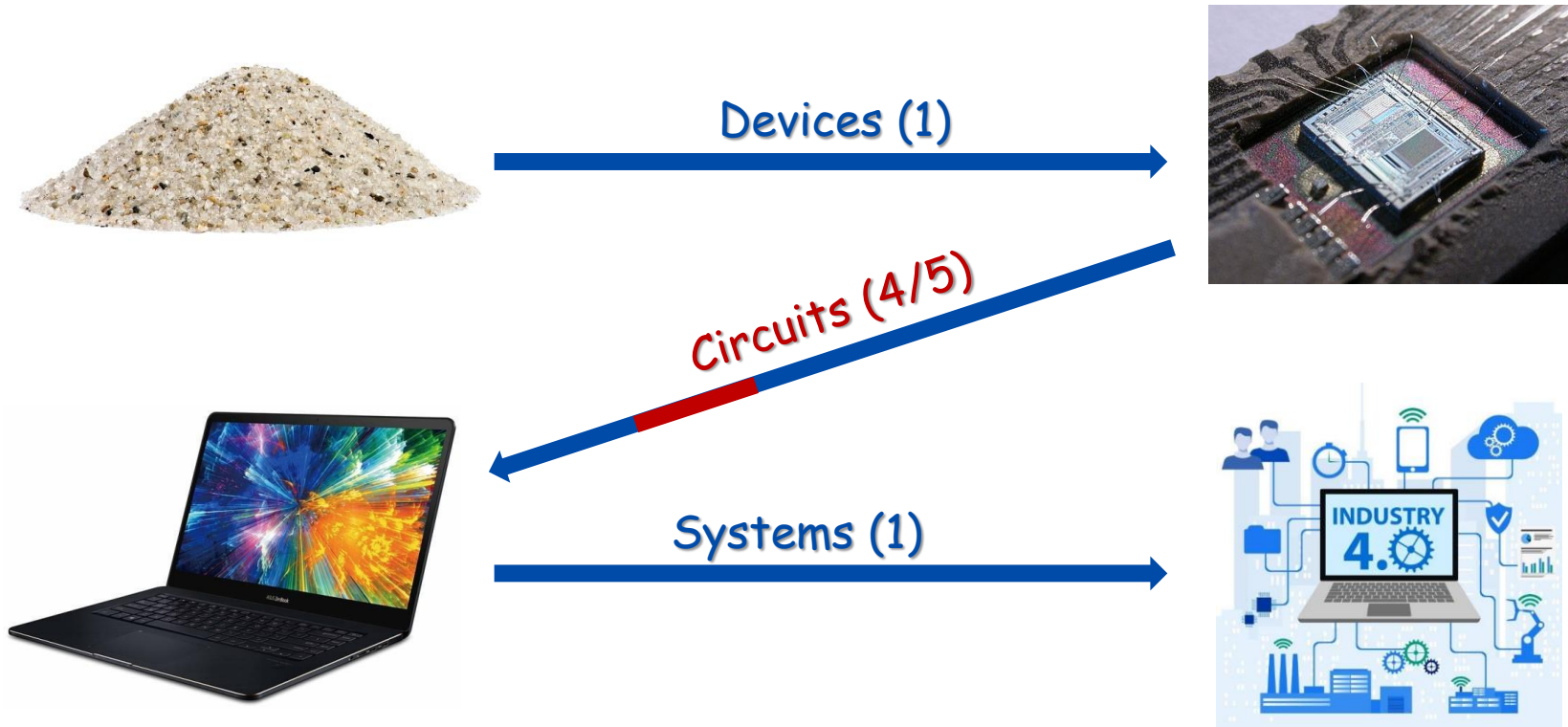

(Figures from Internet)

Study Purpose of Lecture #6

- 哲学三问
 - Who are you?
 - Where are you from?
 - Where are you going?


To answer those questions
throughout your life

你要到哪里去?
你从哪儿来?
你是谁?
哲学终极问题
门房大爷的问题



(Figures from Internet)

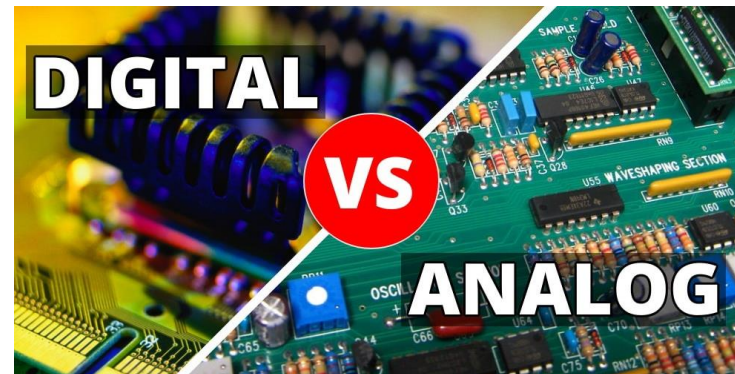
- In this lecture, we ask
 - How to connect a discrete digital machine to the physical world?
 - What are the purpose and basic principle of an **analog circuit**?
 - How to convert analog (continuous) signal into digital (discrete) signal?



Lecture Outline


- The real world vs. a binary world
- Fundamentals of **analog (linear) circuit Amplification**
 - Operational amplifier
- Basic MOS **amplifier**
 - Voltage range
 - Frequency limitations
- Analog to digital conversion (ADC)
- Digital to analog conversion (DAC)

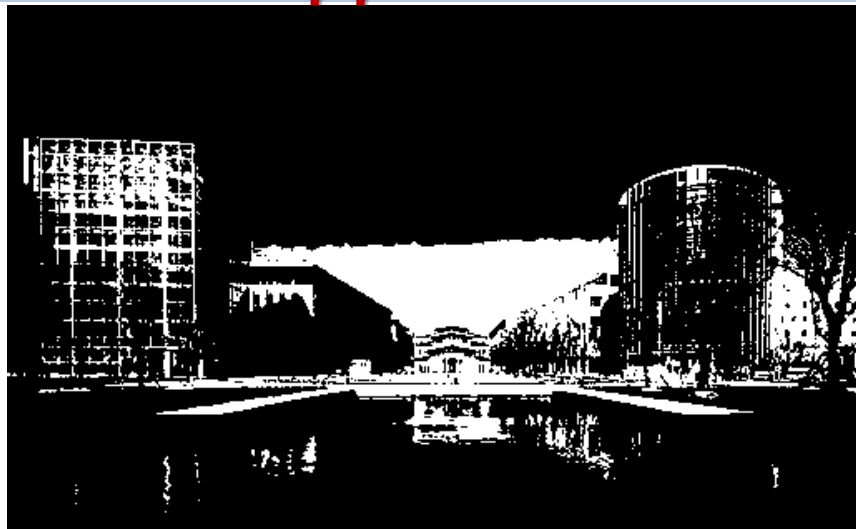How to approximate the real world graphically?



A binary world

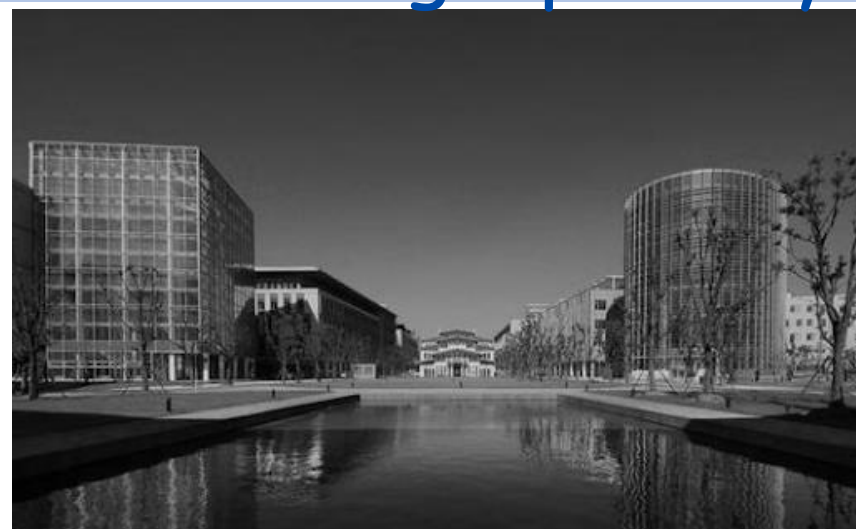every pixel can only be either 1 (black) or 0 (white)



A gray scale world

every pixel can only be a number between 1 (black) or 0 (white)




The colorful real world

How to approximate the real world vocally?




The real world vs. a binary world

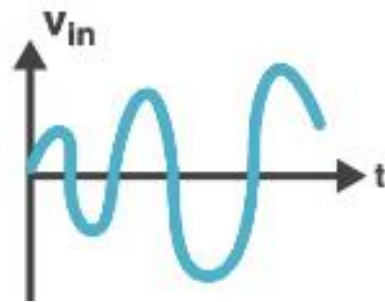

Real-world signal




Digital data

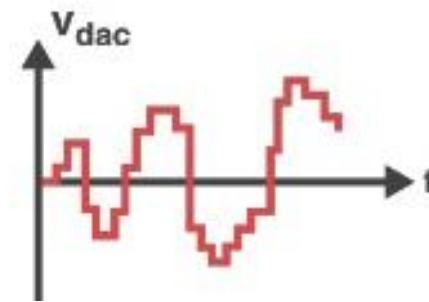

Real-world approximation

The importance of amplification

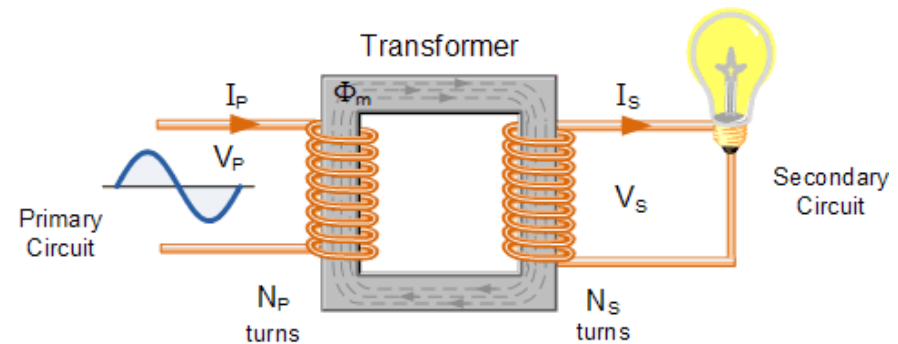- In the mechanical domain
 - What is amplified?
 - What is reduced?
- In the electrical domain
 - What is amplified?
 - What is reduced?




How about these?

- In the mechanical domain
 - What is amplified?
 - What is reduced?
- In the electrical domain
 - What is amplified?
 - What is reduced?





(Electronic) amplifier

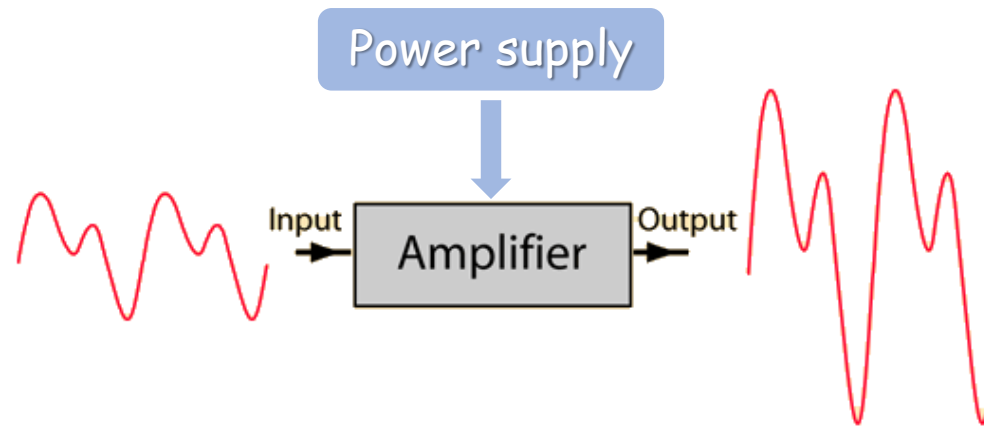- An electronic device that increases the power of a signal
 - Taking energy from a **power supply**
 - Controlling the output to match the input signal shape but with a larger **amplitude**
 - The opposite of an attenuator
 - An amplifier provides **gain**, an attenuator provides loss




Operational amplifier (op amp)

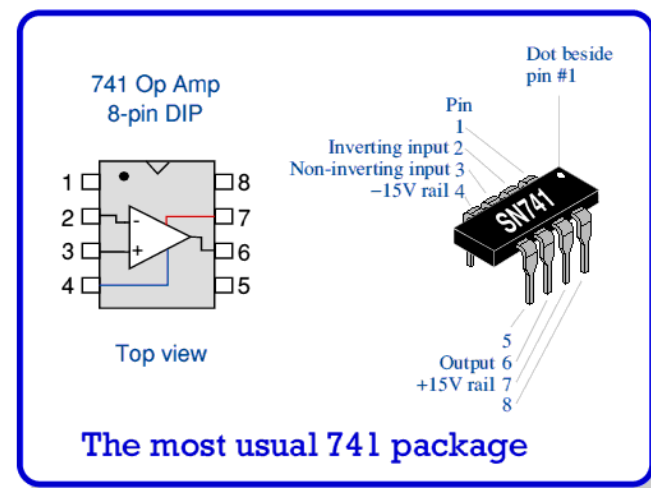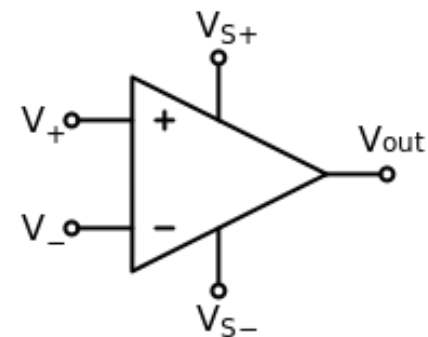- One of the most widely used electronic devices
- Originally from analog computers for doing mathematical operations
- Characteristics
 - DC-coupled
 - Voltage amplifier
 - High gain ($A \rightarrow \infty$)
 - A differential input ($V_+ - V_-$)
 - A single-ended output (V_{out})




Realization

- CMOS Technology

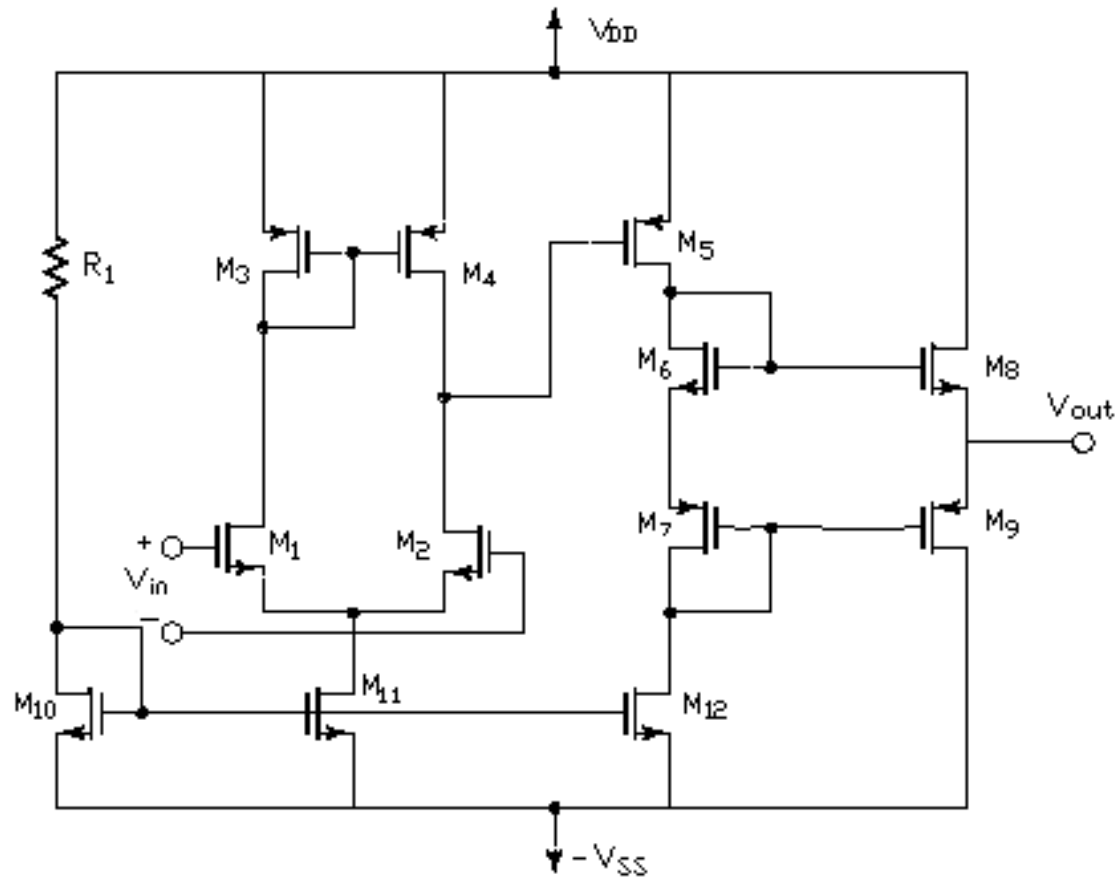

Realization


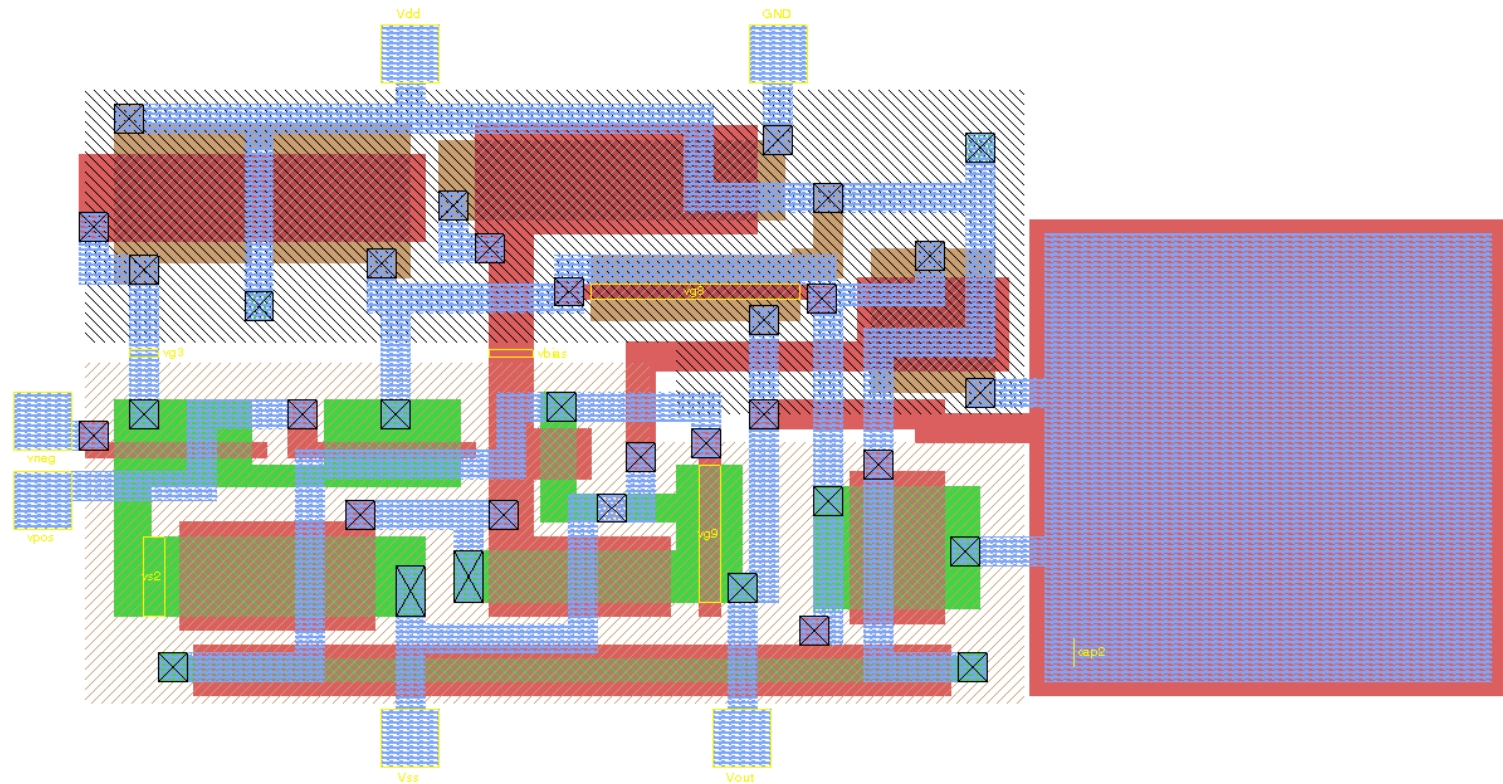
- Layout view of a simple CMOS operational amplifier




Applications

- Audio system

- Bio-electric signal

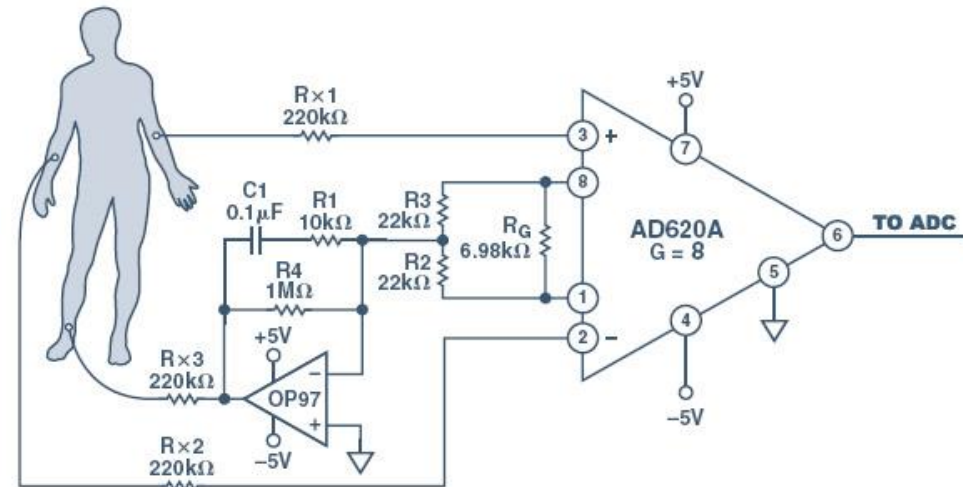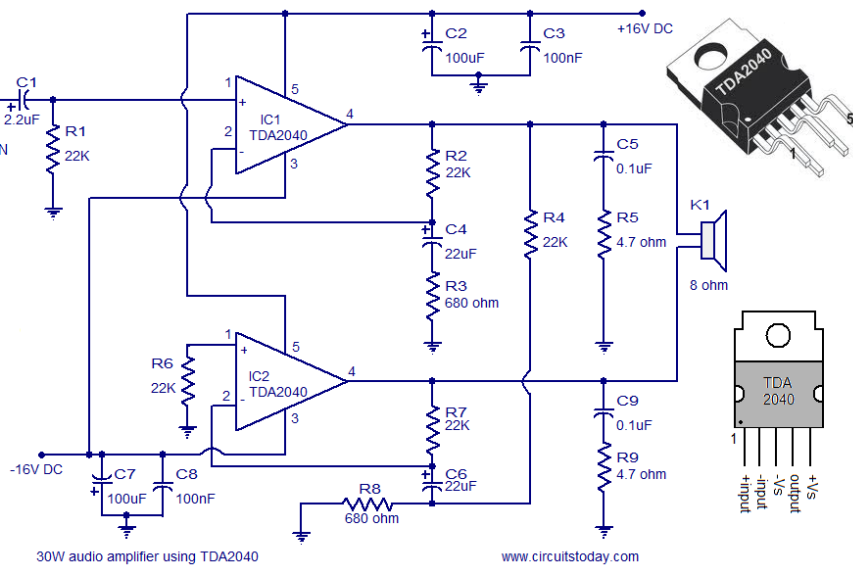


Ideal op amp

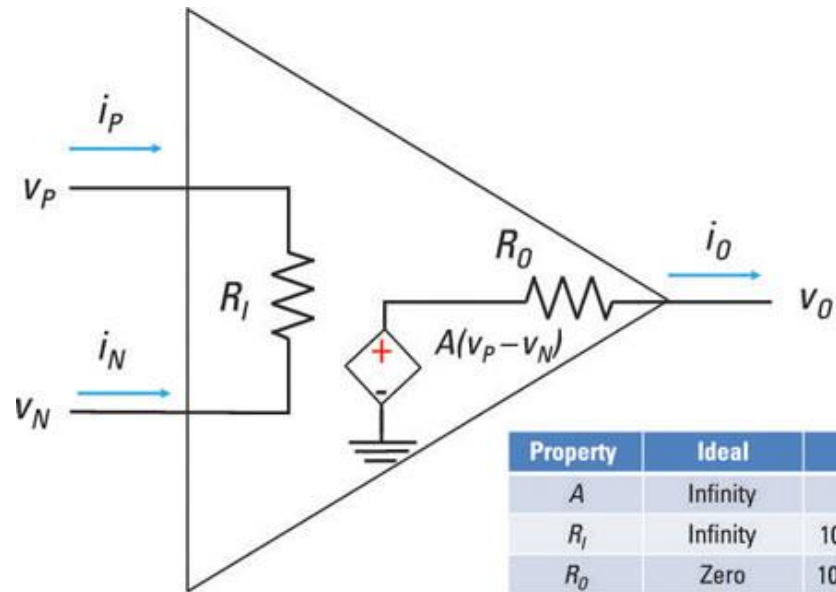

Property	Ideal	Typical
A	Infinity	$10^5 < A < 10^8$
R_I	Infinity	$10^5 \Omega < R_I < 10^8 \Omega$
R_O	Zero	$10^5 \Omega < R_O < 10^8 \Omega$

Voltage follower

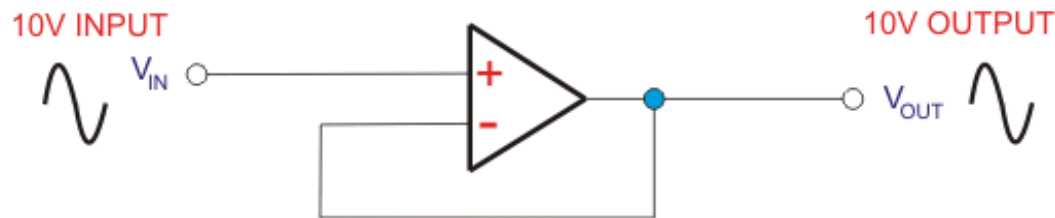
- A voltage follower is a op-amp circuit which has a voltage **gain of 1**





Open-loop and closed-loop gain

- Open-loop gain

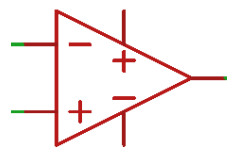
- Large but finite
- Instable subjected to the manufacturing process, temperature, etc.



- Closed-loop gain

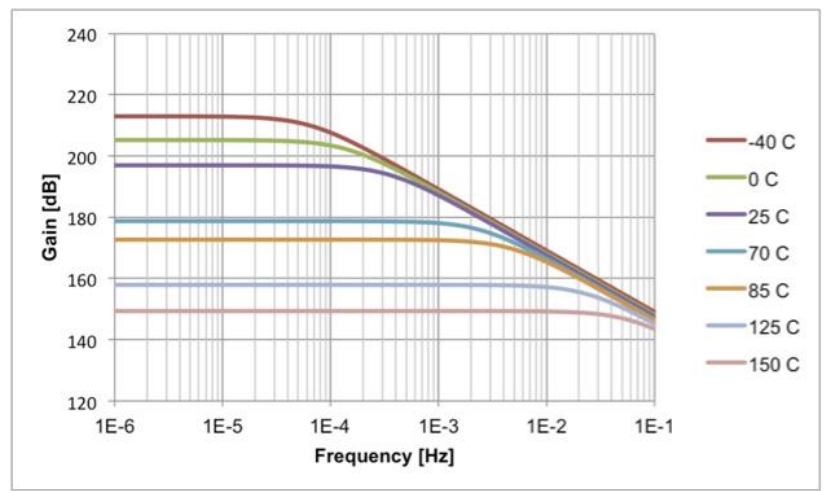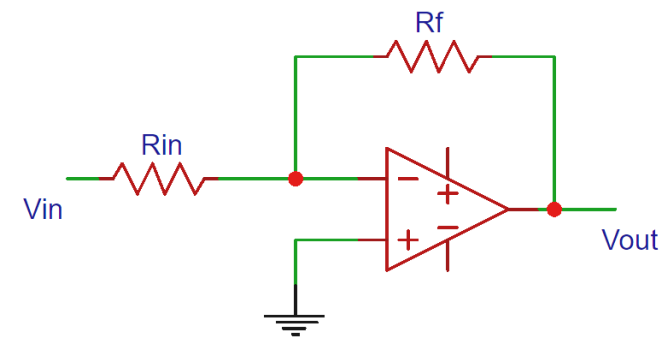

Summing amplifier circuit

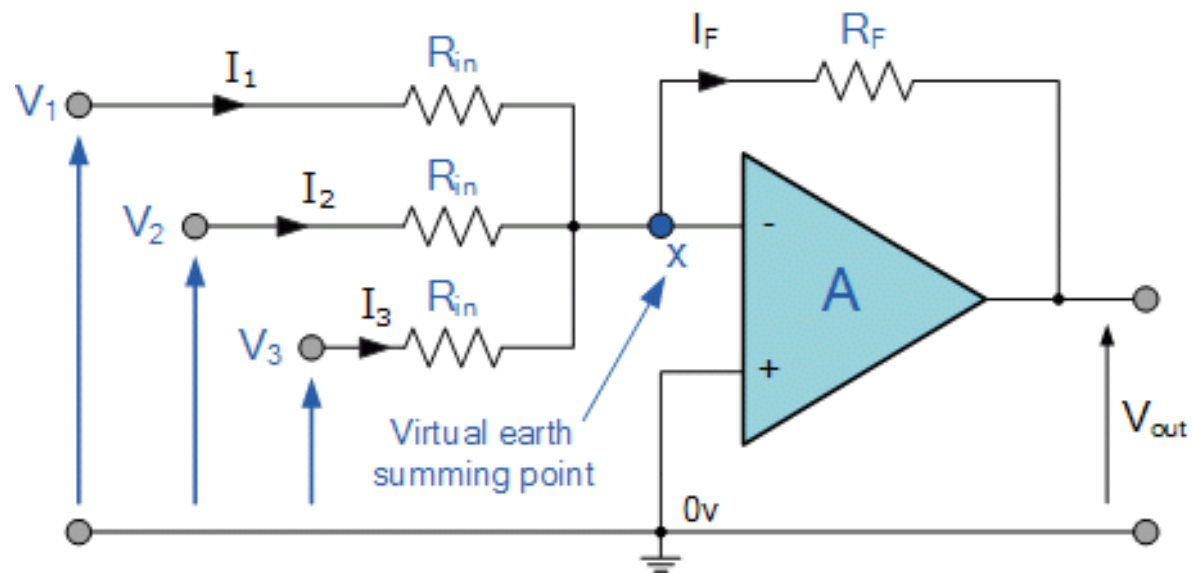

Linear Range vs. Saturation Range


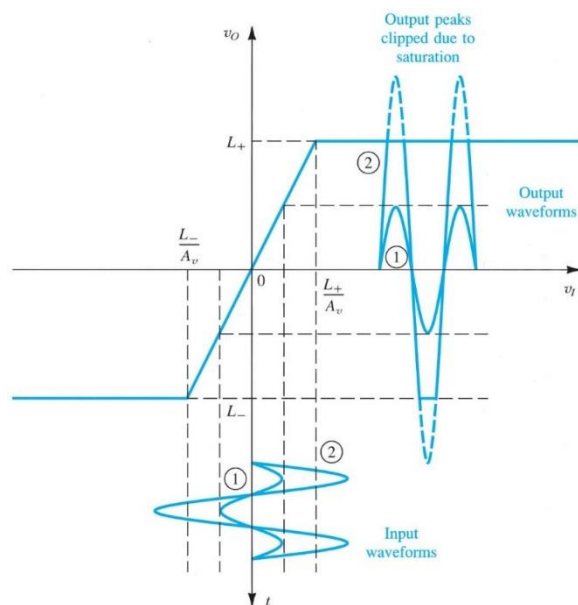
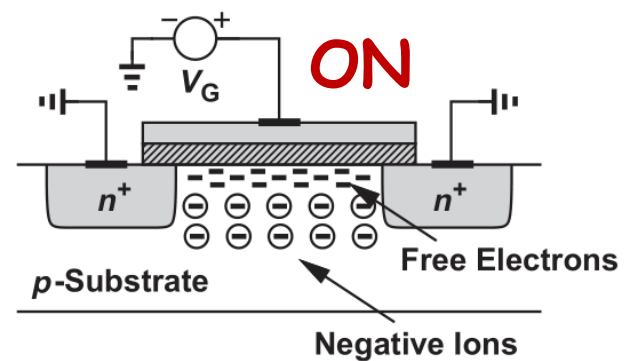
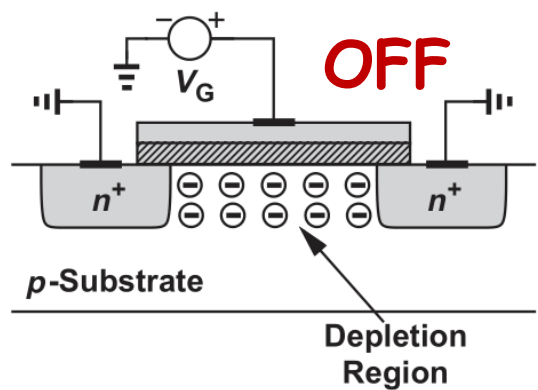


Figure 1.14 An amplifier transfer characteristic that is linear except for output saturation.

- Within linear range, the output voltage (or current) is **proportional** to the input voltage (or current)
- Beyond **linear range**, the output voltage (or current) waveforms **saturates**, resulting in distortions
 - Lose fidelity in stereo system
 - Cause interference in wireless system


MOSFET in digital applications: a review

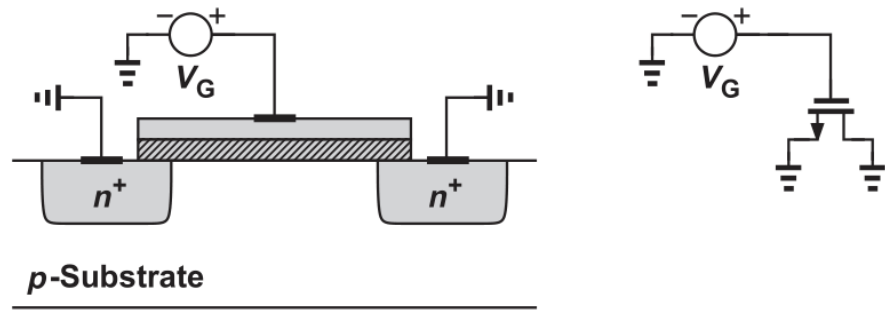


(Razavi, Fundamentals of Microelectronics)

Beyond the on/off states

- For digital electronics
 - Cut off



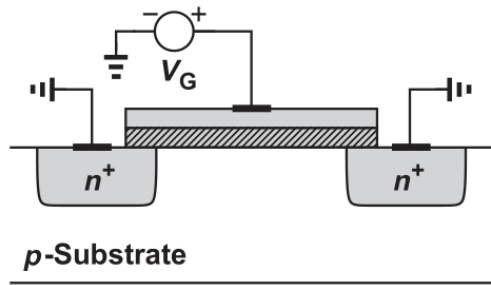


- Conducting


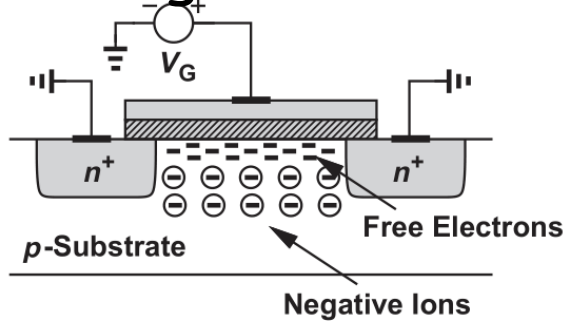


(Razavi, Fundamentals of Microelectronics)

- For analog electronics

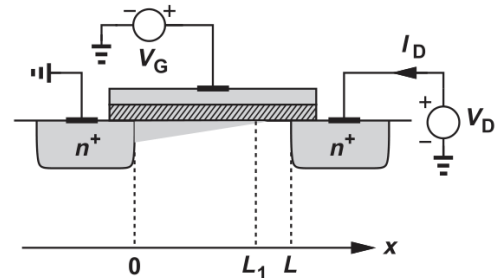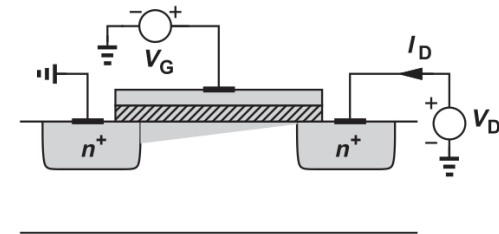
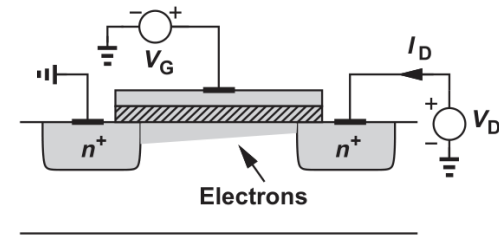


I/V characteristics

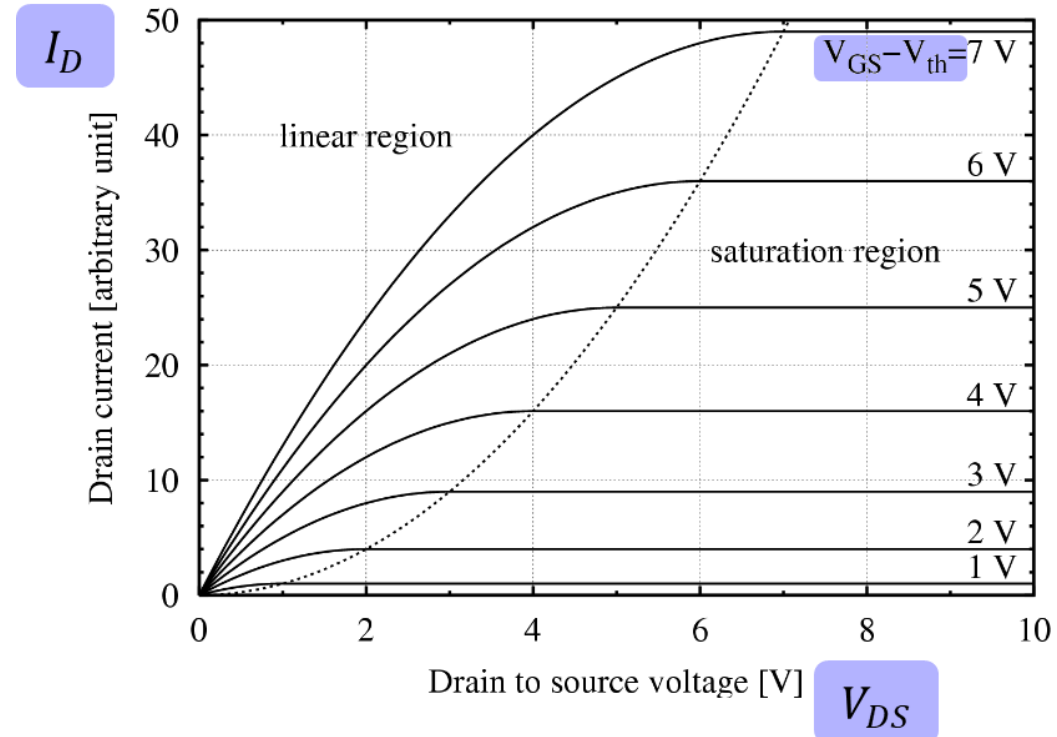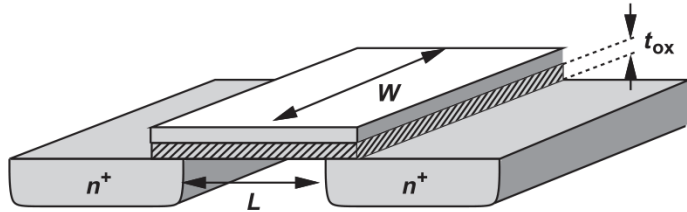

(Razavi, Fundamentals of Microelectronics)


Basic MOS amplifier

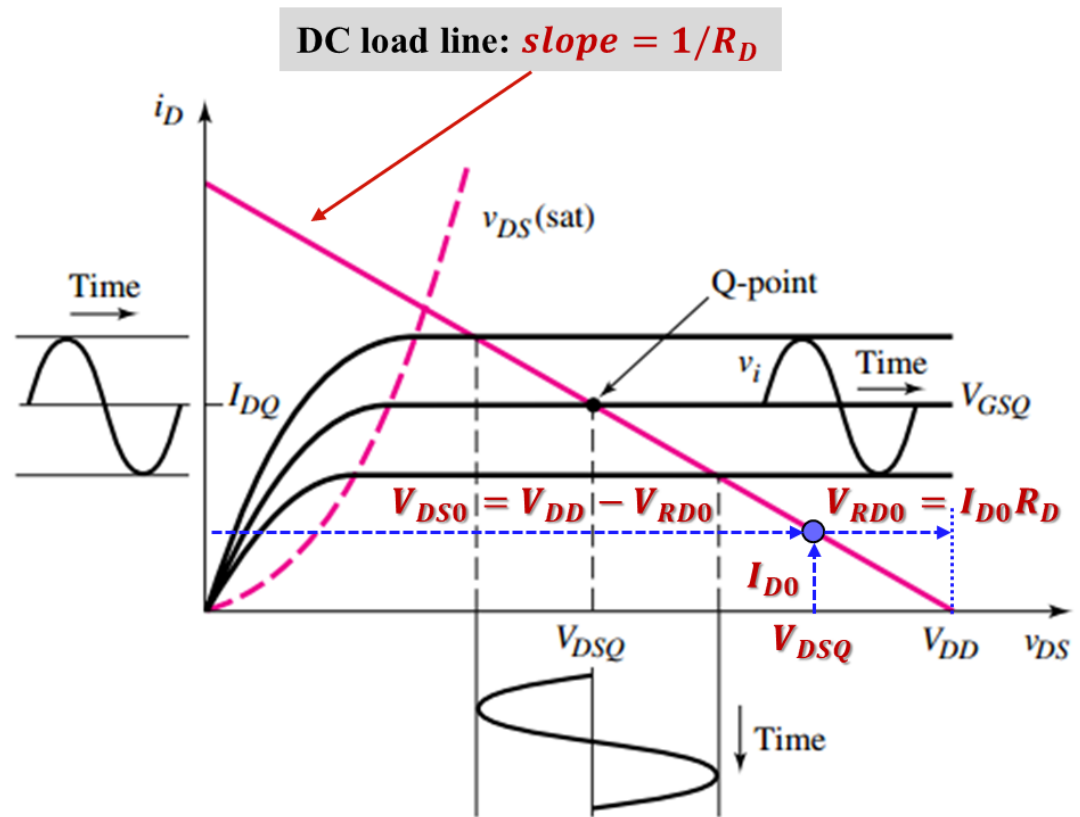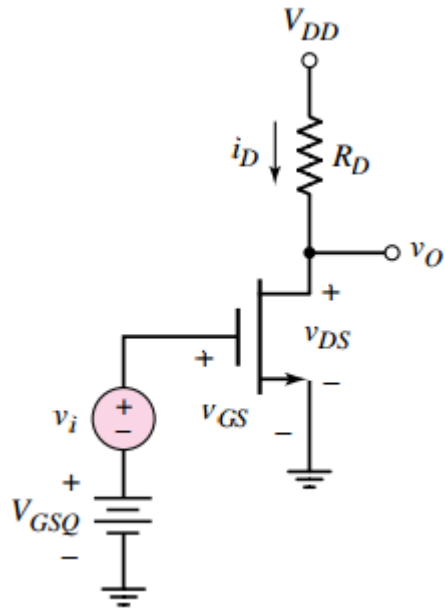

(Neamen, Electronic Circuit Analysis and Design)

Voltage range limitations



- In a real transistor circuit

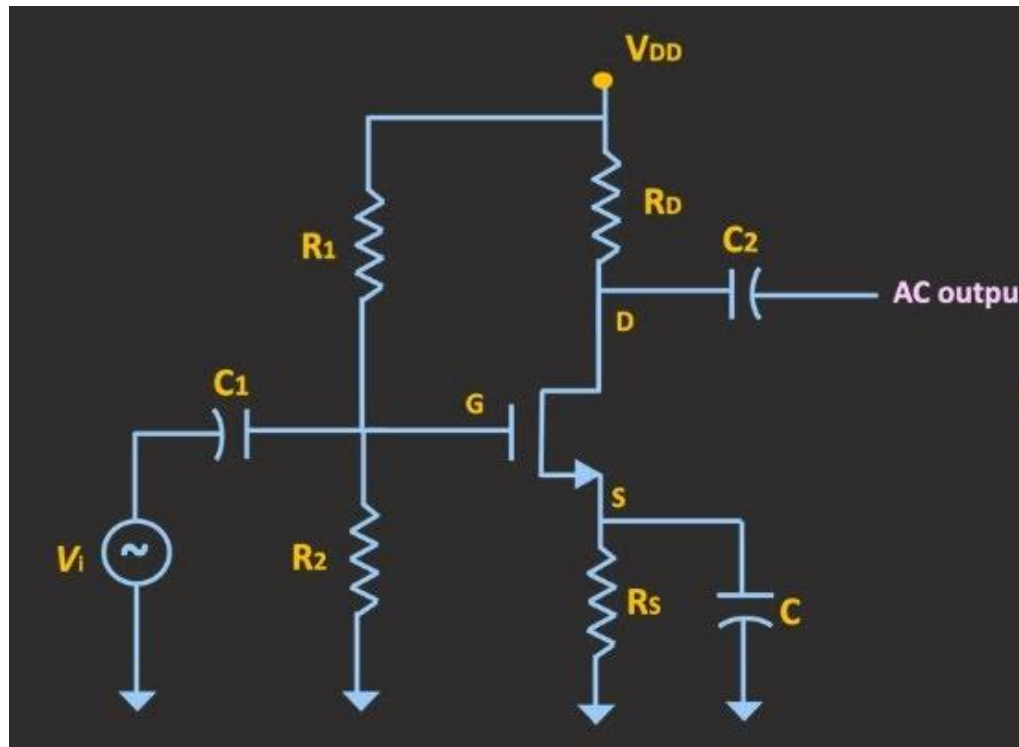

Voltage range limitations



- In a real transistor circuit

- A lever example

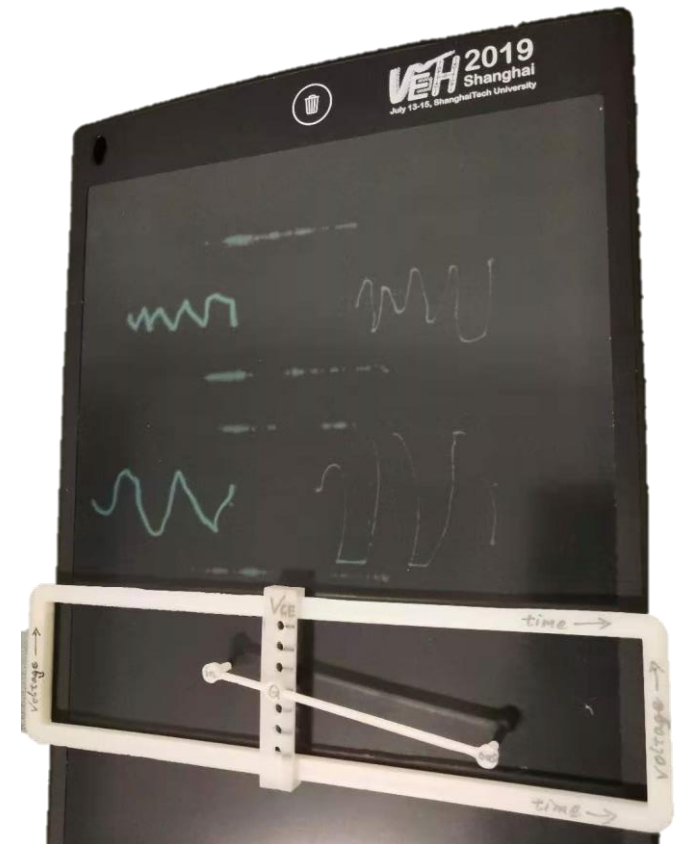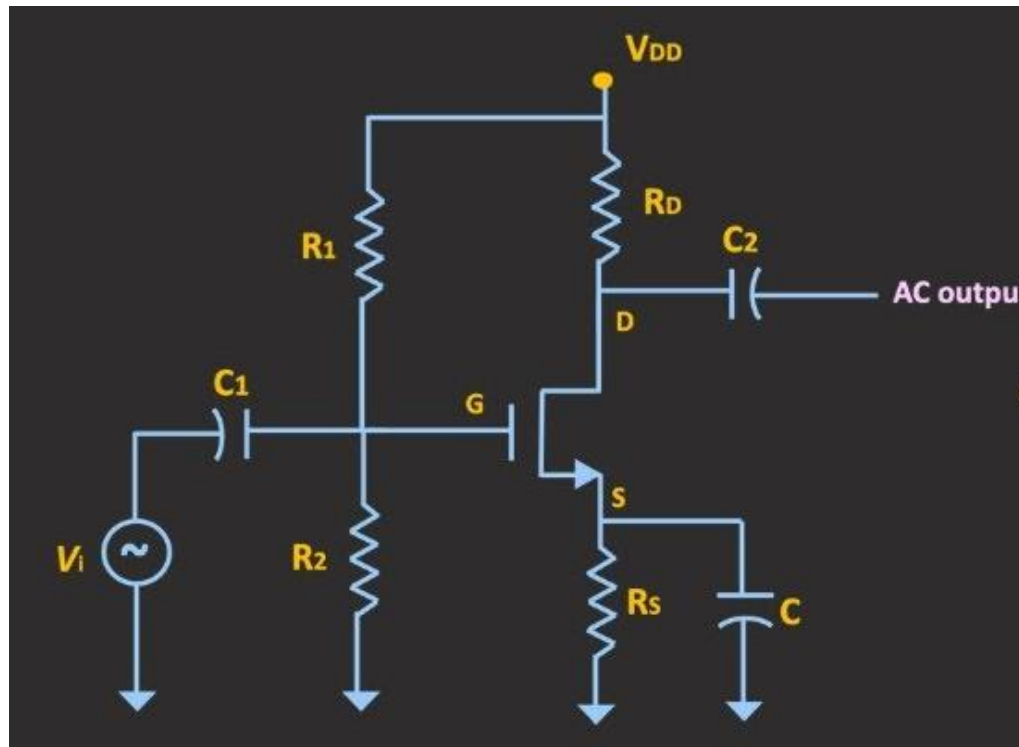


Frequency limitations

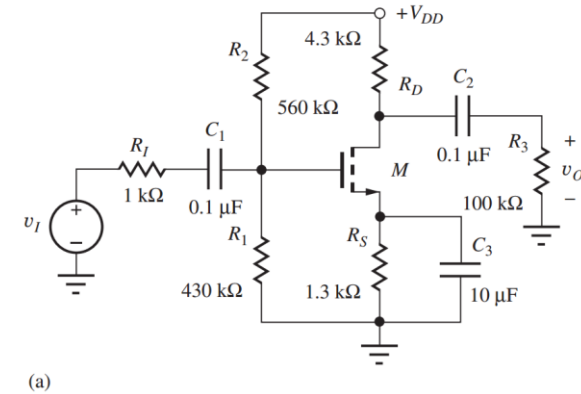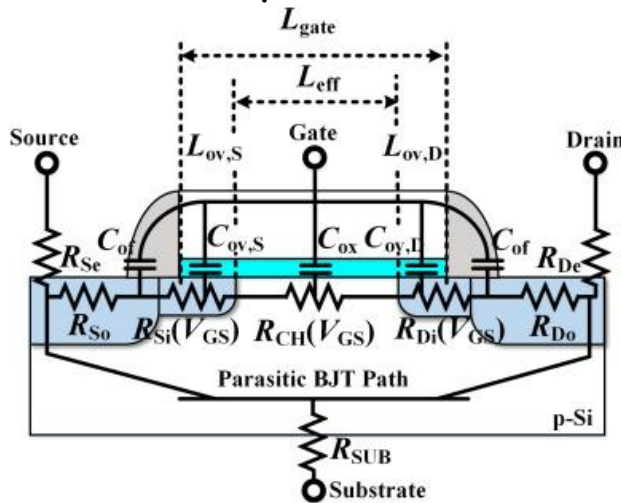
- Parasitic components of a MOSFET
- Coupling capacitance




- Frequency response

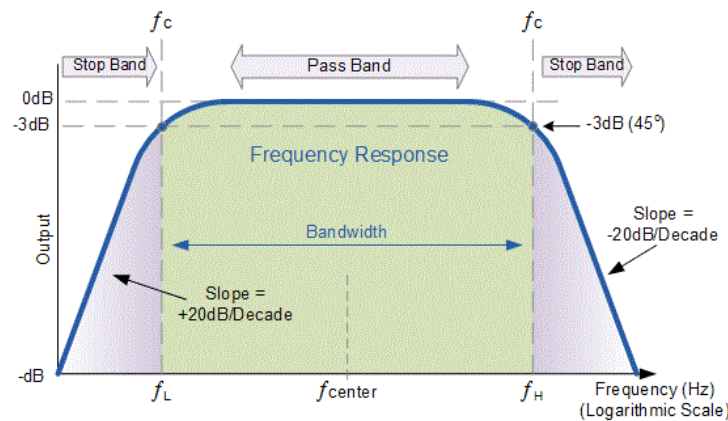

ADC & DAC

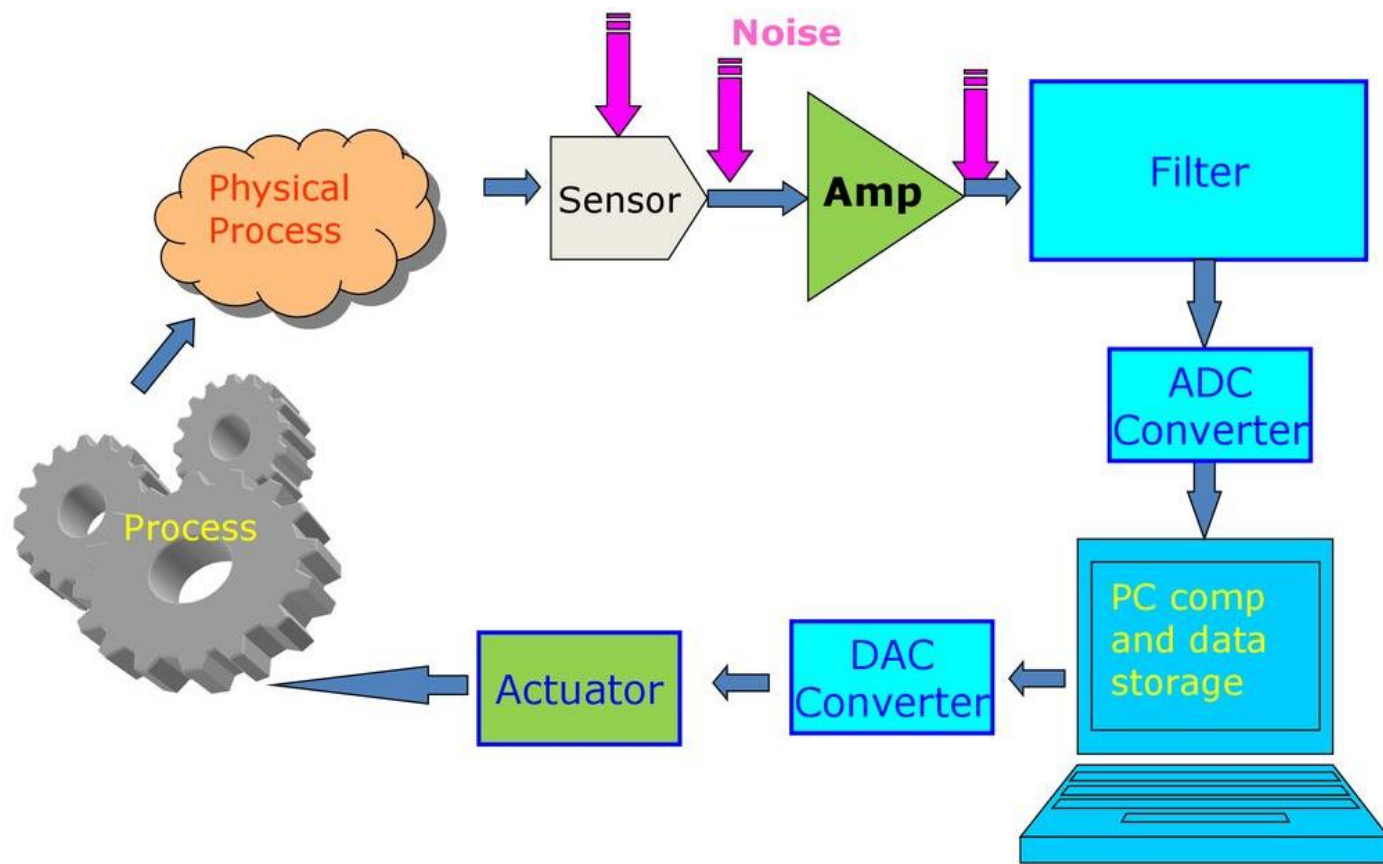


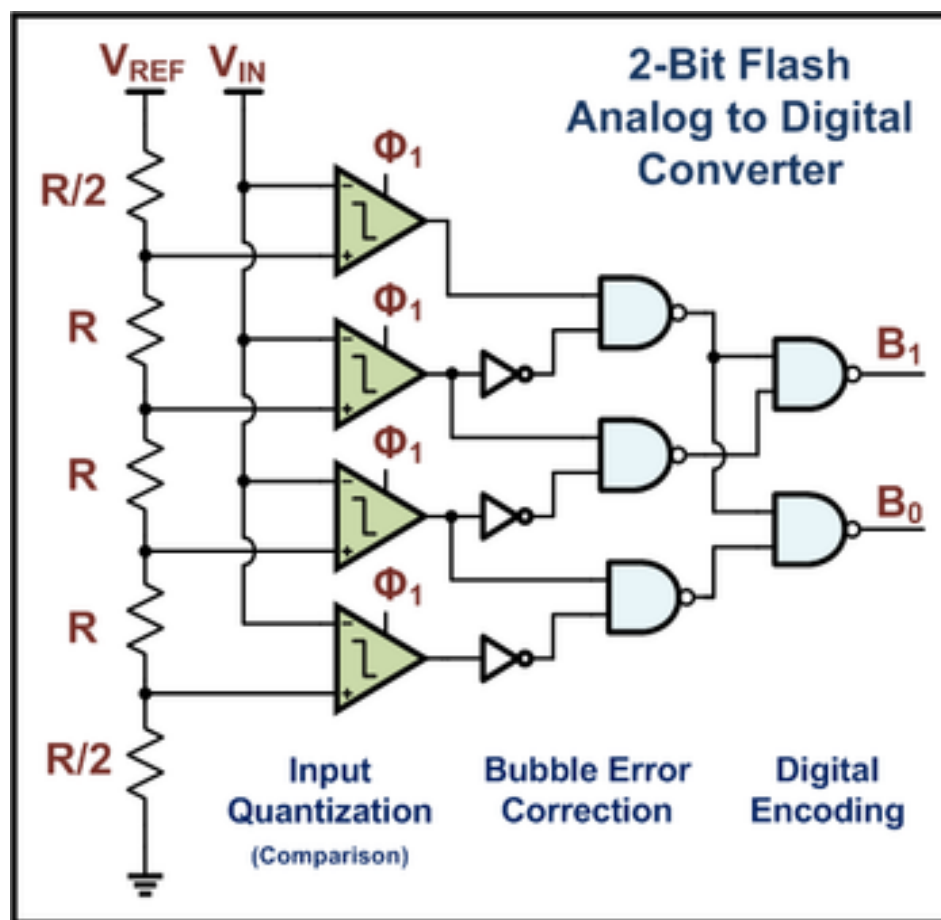ADC example: Flash ADC (direct-conversion ADC)




Digital-to-analog converter (DAC)

- The simplest form

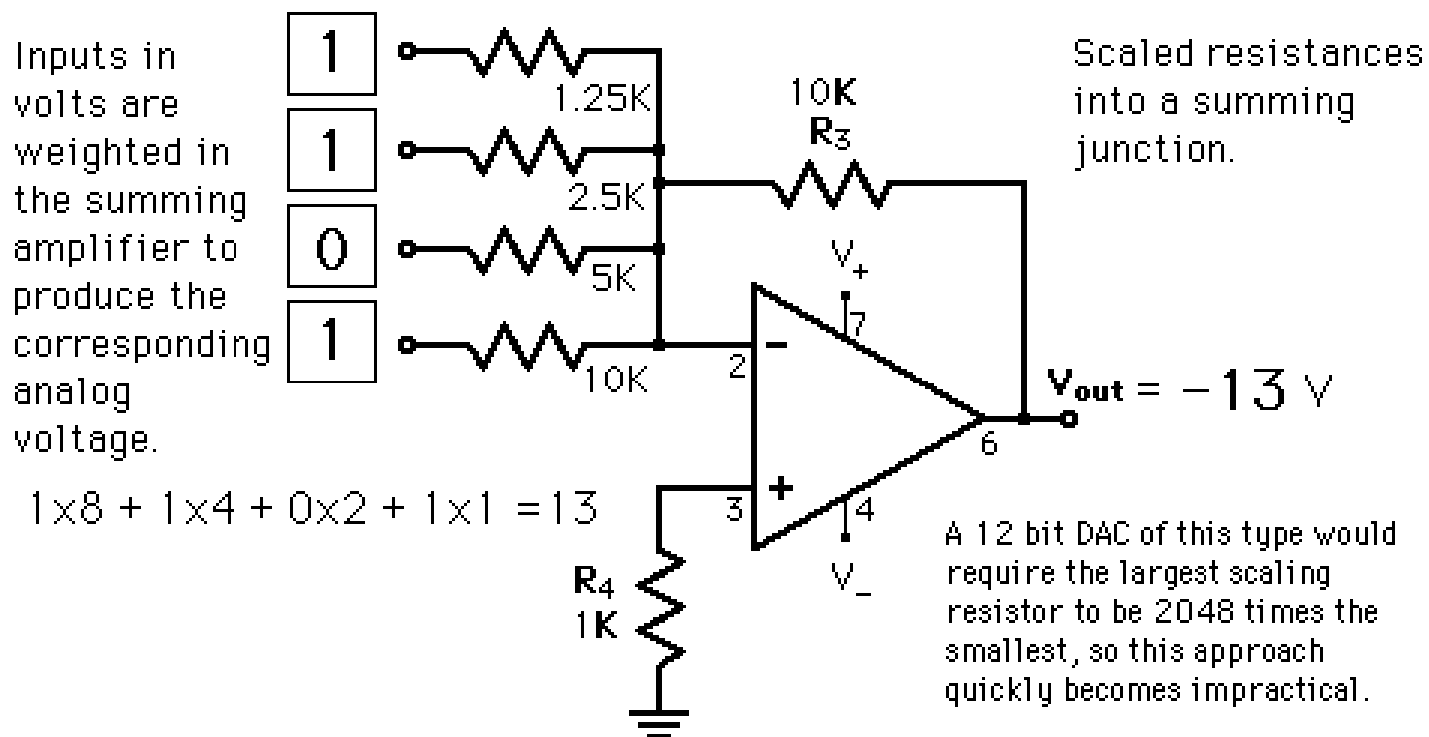


Digital-to-analog converter (DAC)

- The R-2R ladder

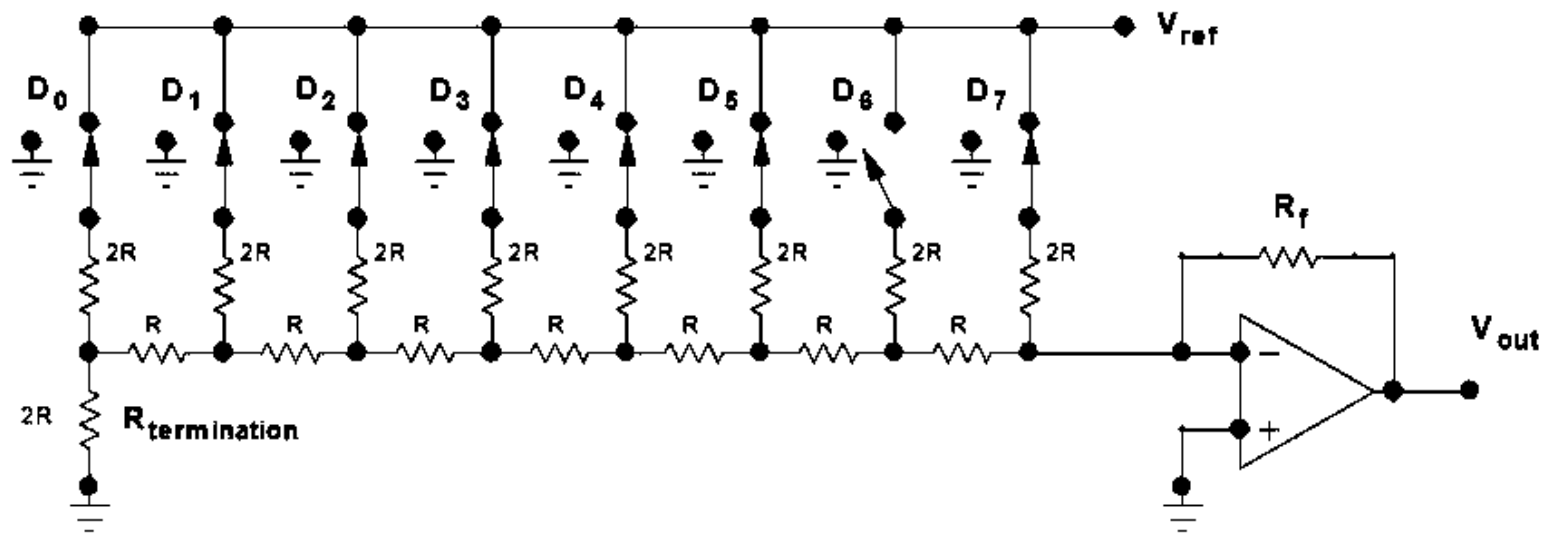


The R-2R ladder DAC


R-2R DAC with Input V_A

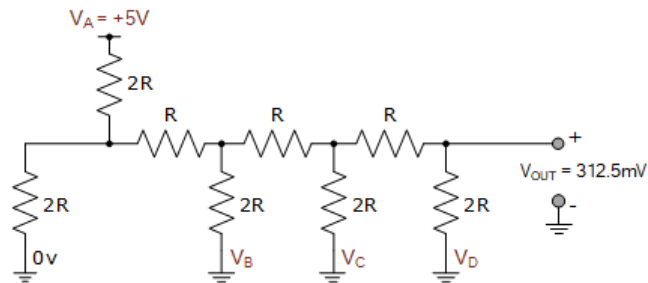

R-2R DAC with Input V_B

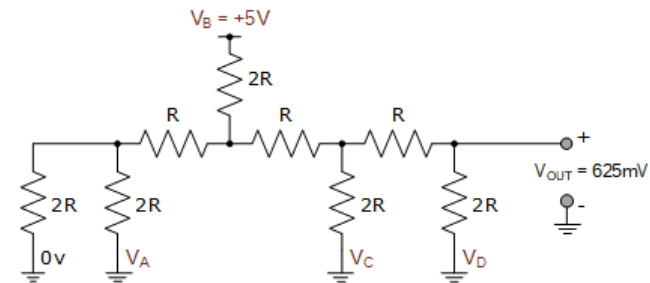

R-2R DAC with Input V_C

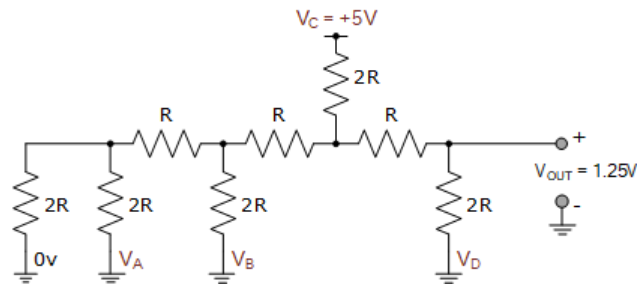

R-2R DAC with Input V_D

