


SI100B
Introduction to Information
Science and Technology
(Part 3: Electrical Engineering)

Lecture #7 Power Electronics

Instructor: Haoyu Wang(王浩宇)

Apr. 26th, 2023

The Theme Story

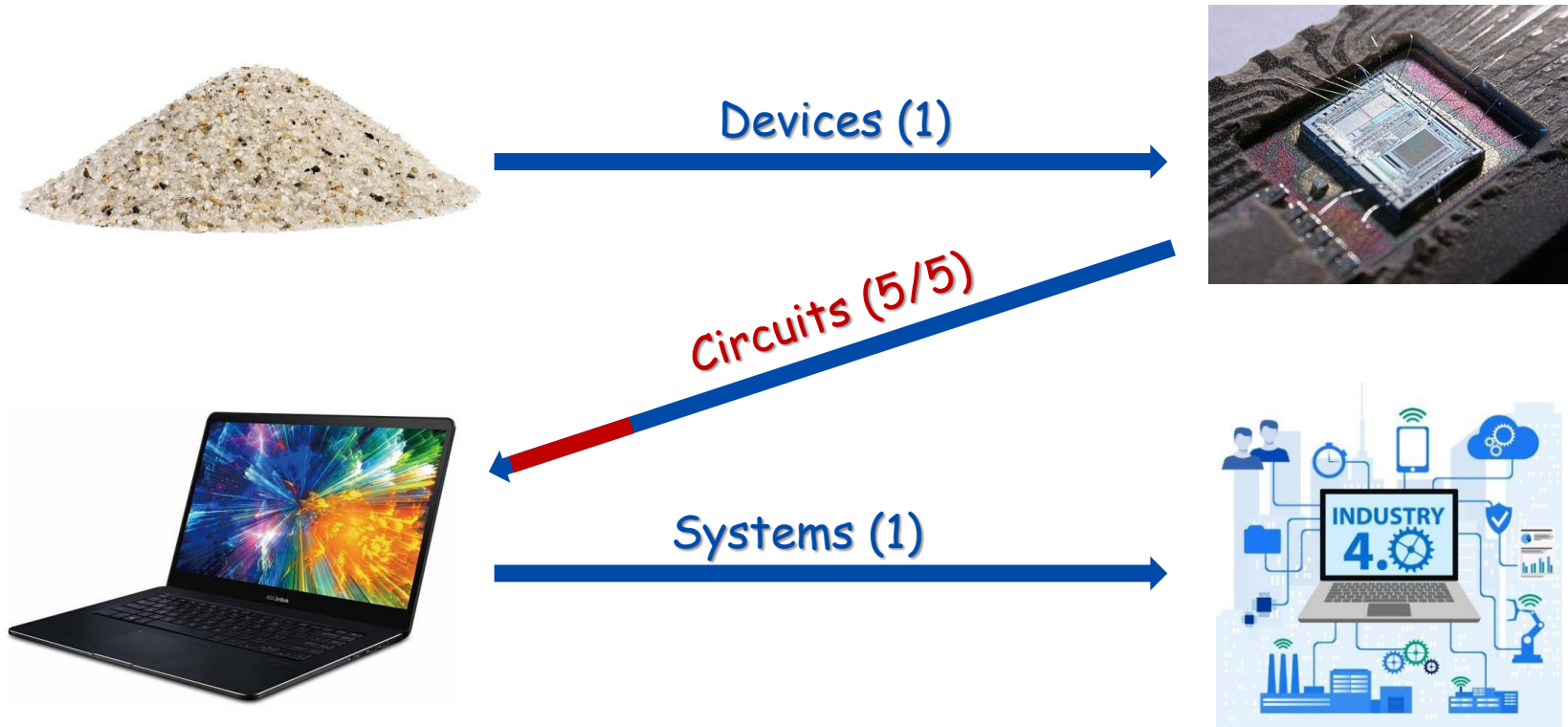

(Figures from Internet)

Study Purpose of Lecture #6

- 哲学三问
 - Who are you?
 - Where are you from?
 - Where are you going?


To answer those questions
throughout your life

你要到哪里去?
你从哪儿来?
你是谁?
哲学终极问题
门房大爷的问题



(Figures from Internet)

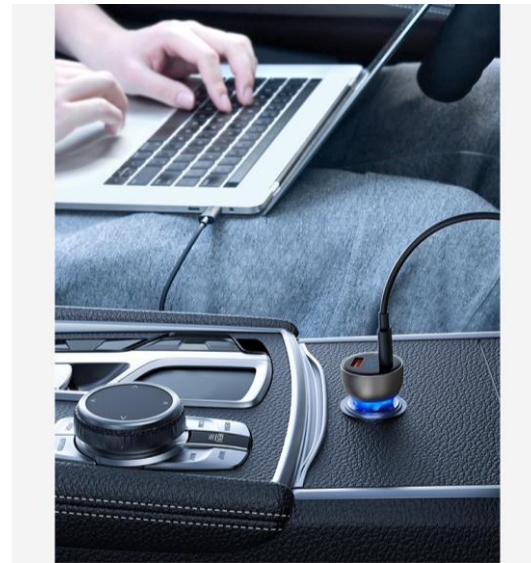- In this lecture, we ask
 - What are **power electronics**?
 - How do we **step-up** and **step-down** a dc voltage?
 - How do we model power converters?




Lecture Outline

- Introduction
- Switched mode power supply
- Buck converter
 - Small ripple approximation
 - Volt-second balance
 - Charge balance
 - Estimating more accurate ripple
- Boost converter
- Closed loop control and negative feedback

Power Electronics

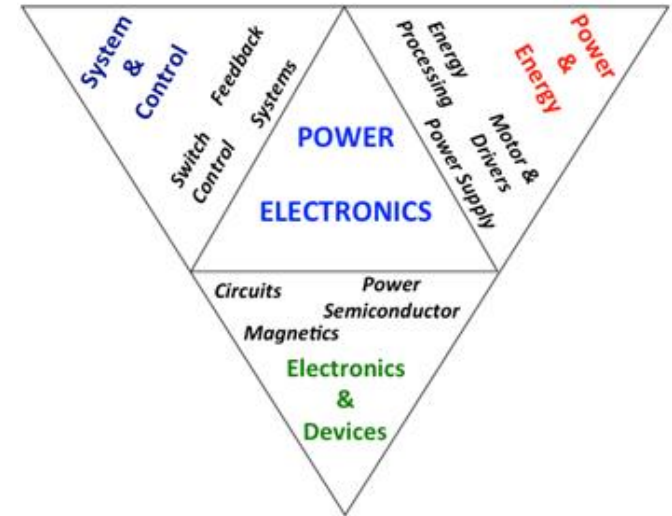- Power electronics is the application of **solid-state electronics** to the **control** and conversion of **electric power**.
 - Semiconductor functions as switch
 - High frequency
 - Compact size
 - High efficiency
 - Reliable



(Figures from Internet)



UPS



Consumer AC/DC power supply



Telecom & server power



Battery pack & charger

Ubiquitous Power Electronics



上海科技大学
ShanghaiTech University



PEARL
电力电子与再生能源实验室
POWER ELECTRONICS AND RENEWABLE ENERGIES LAB



Electric Vehicle
电动汽车



Data Center
数据中心



Wearable Devices
可穿戴设备



Smart Grid
智能电网





PV Generation
光伏发电



Internet of Things
物联网


- Power electronics is the **enabling** and **transformative** technology
- Evolving towards more **reliable, compact, efficient, low cost**...

DC vs AC

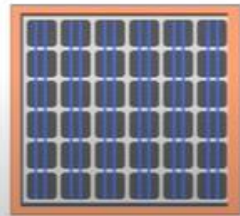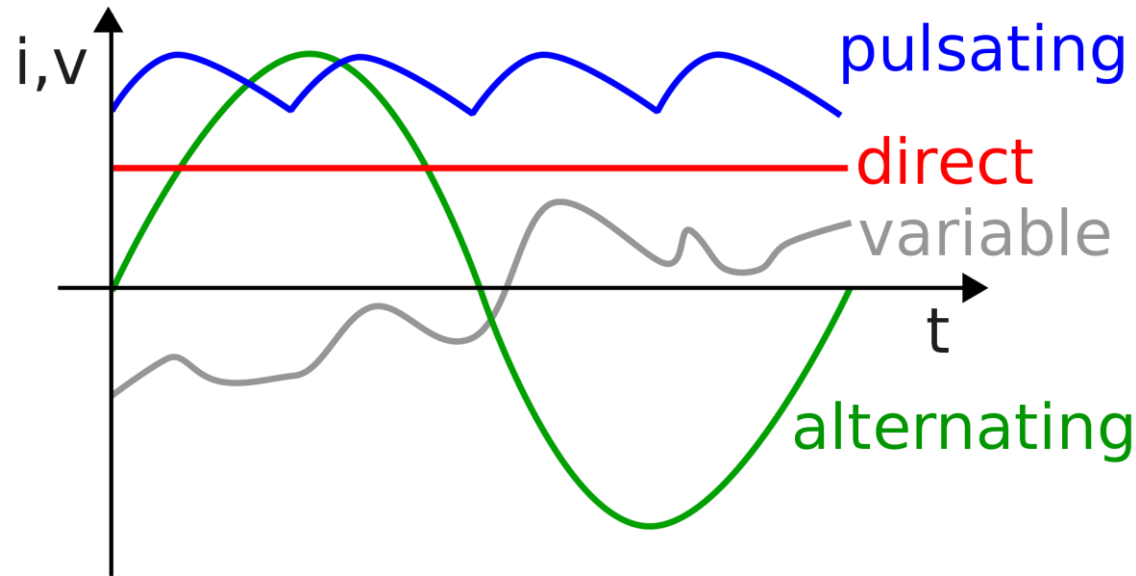

(Figures from Internet)

AC/DC Converter

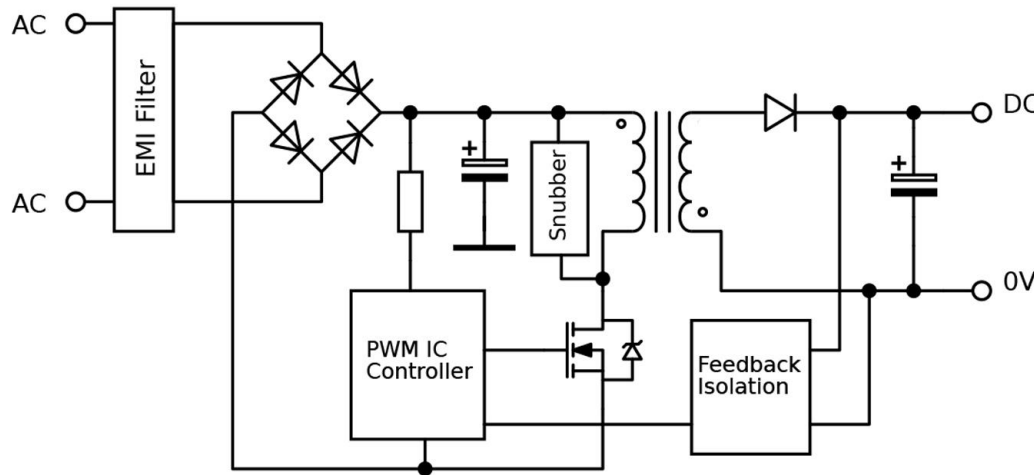


Rectification:
Converting Alternating
Current to Direct Current
(**AC**→**DC**)

(Figures from Internet)

DC/AC Converter


Power Inverters Explained

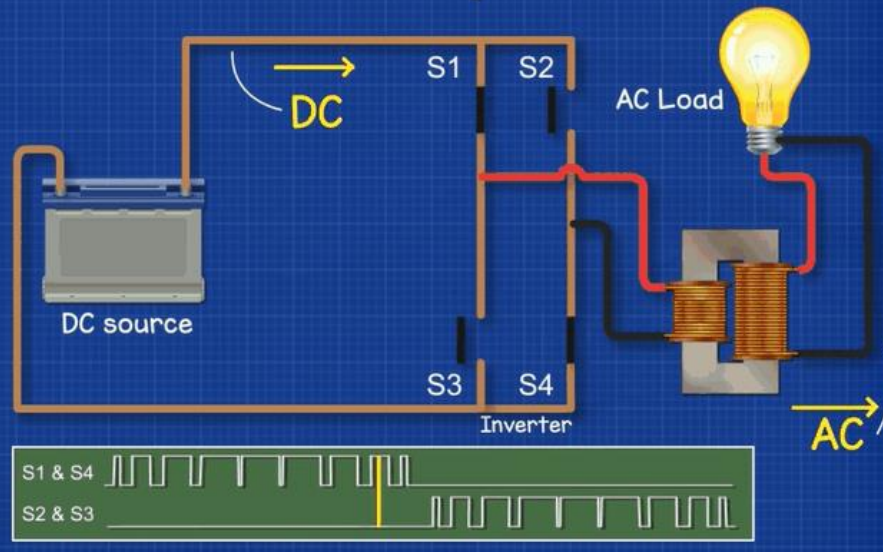

Inverter:
Converting Direct Current
to Alternating Current.
(DC→AC)


(Figures from Internet)

DC/DC Converter

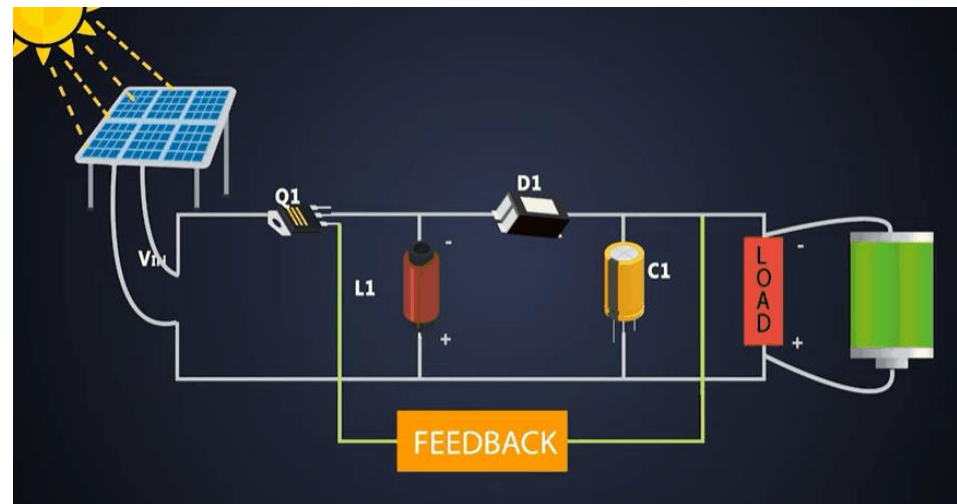

(Figures from Internet)



Power Conversion FOMs

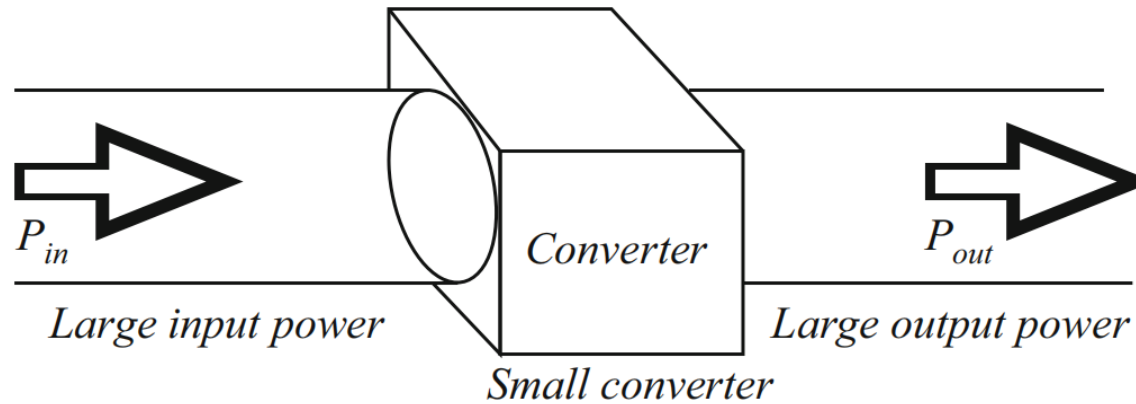

Linear Power Supply



Apple Computer 1

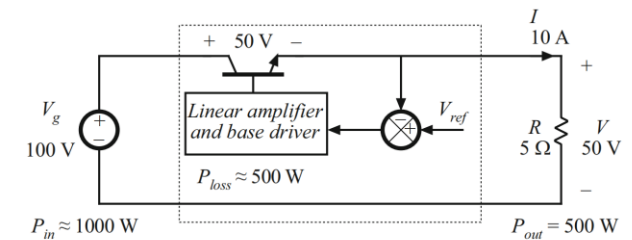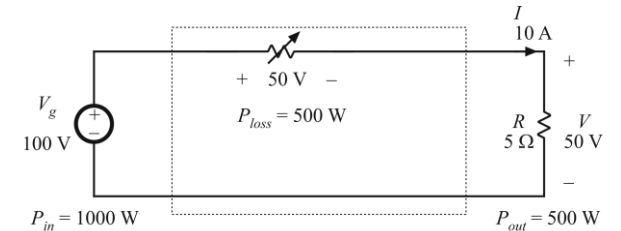


Efficiency: $P_{out}/P_{in} = 50\%$


Switched Mode Power Supply



Apple 140W PD3.1 charger

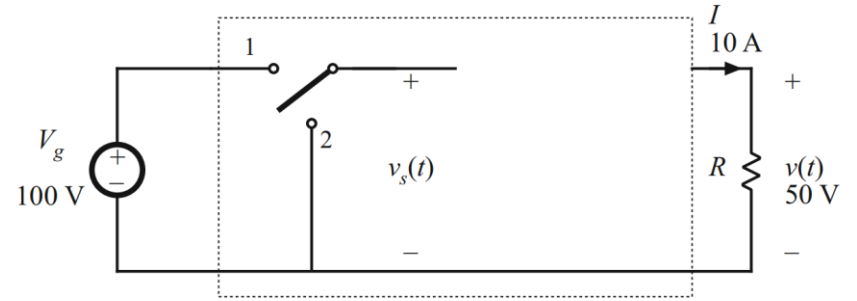


Output voltage $v_s(t)$

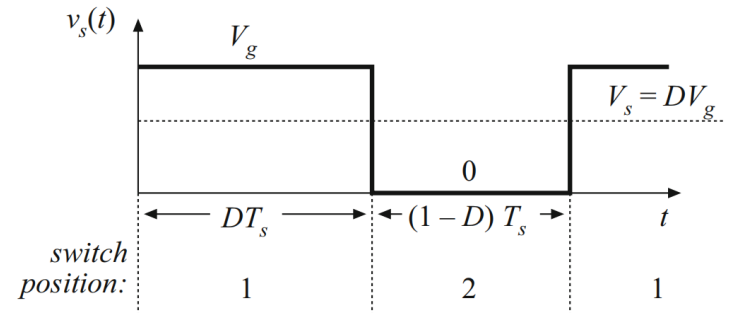


Buck Converter


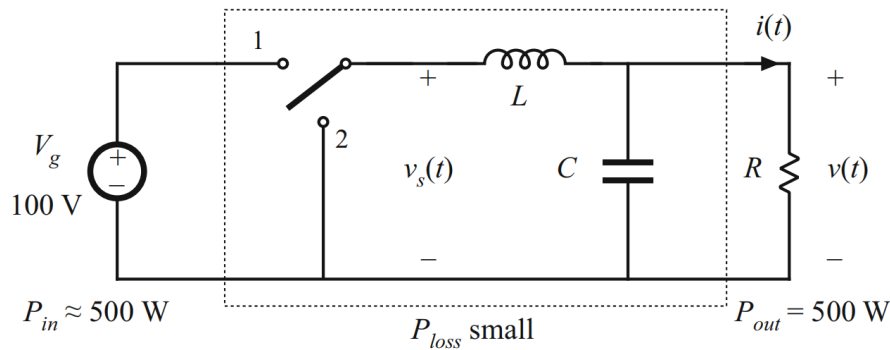
Addition of L-C low-pass filter, for removal of switching harmonics



Realization using **MOSFET** and diode

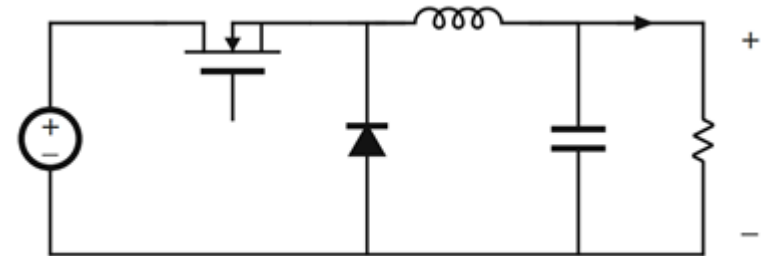


Small-ripple approximation

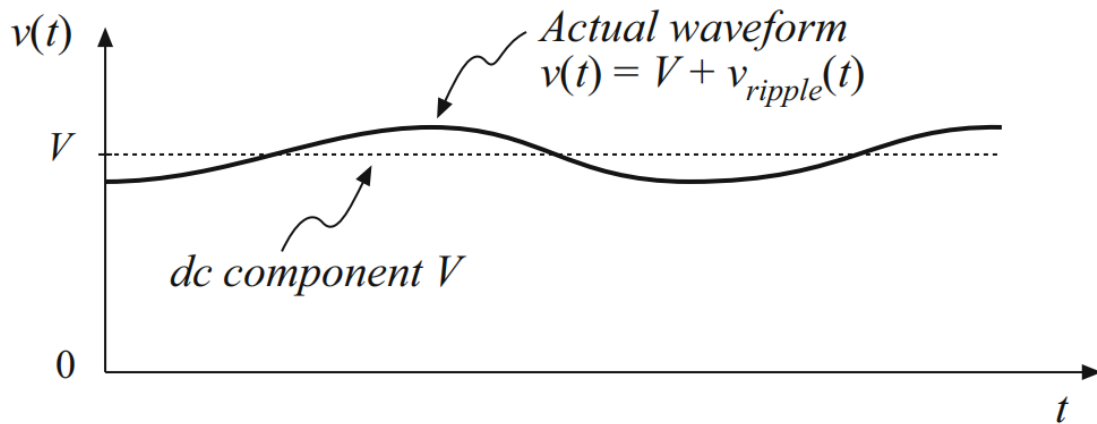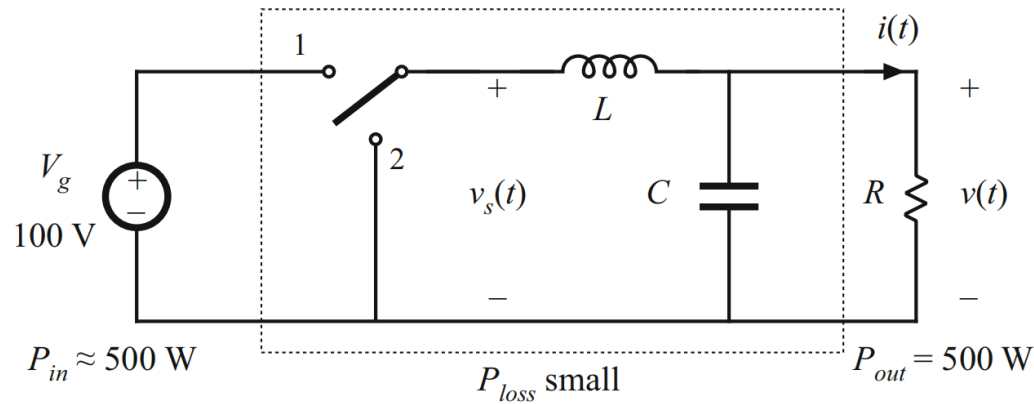

Buck Converter-Mode 1

The devices are assumed to be **ideal**.


Switch in position 1

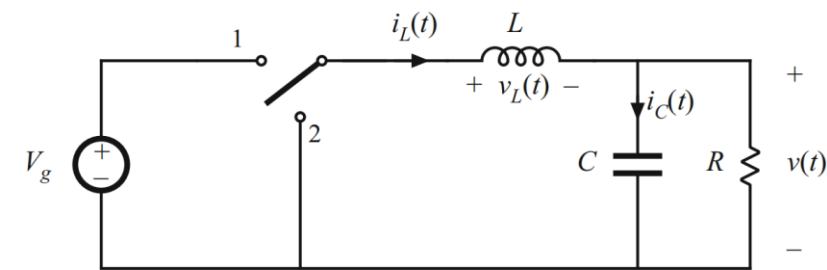


Buck Converter-Mode 2

The devices are assumed to be **ideal**.

Switch in position 2

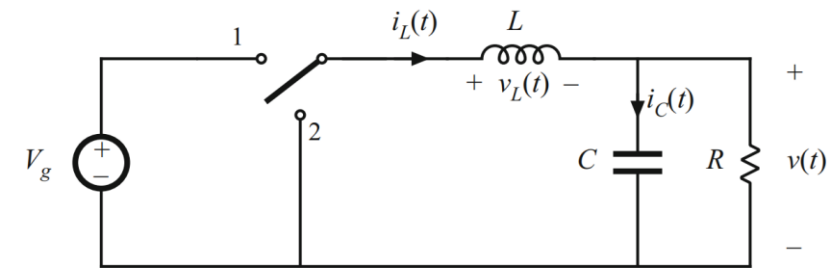


Inductor Voltage and Current

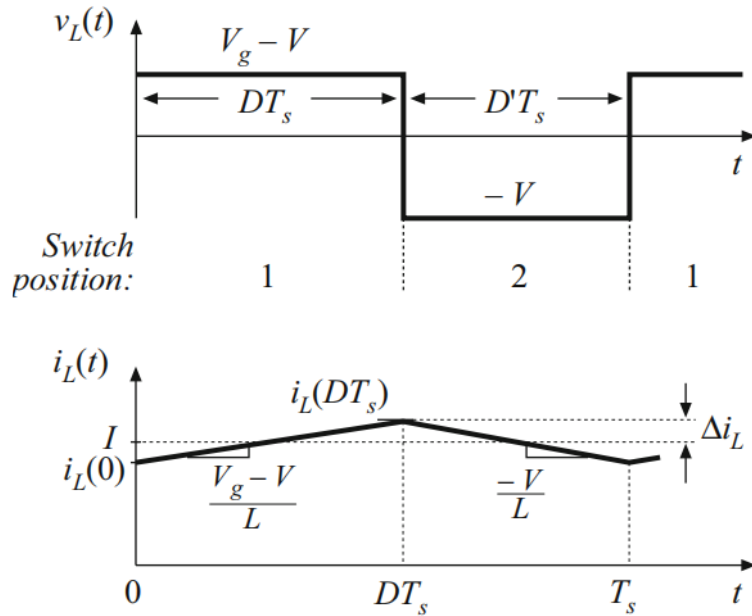

Mode1:

Mode2:


Steady State

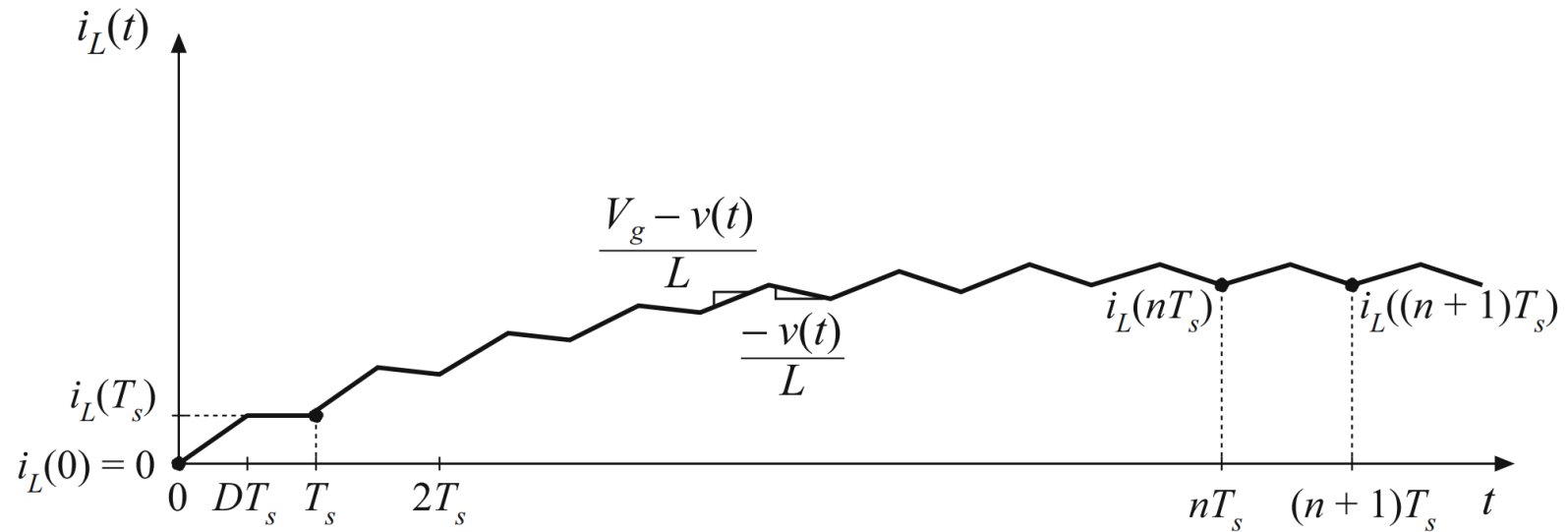

Inductor current waveform during converter turn-on transient



Volt-second balance

inductor volt-second balance.


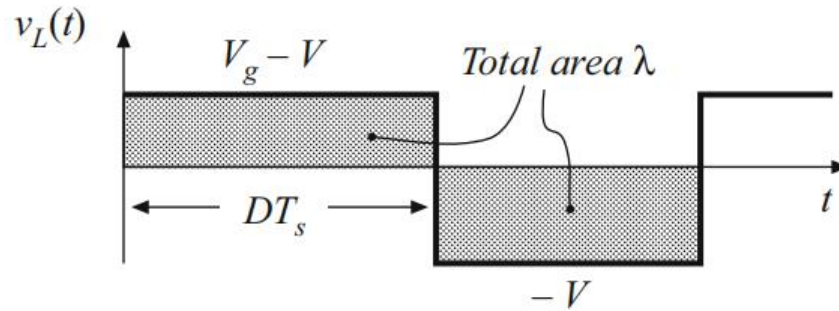


Charge balance

Similarly for capacitors,

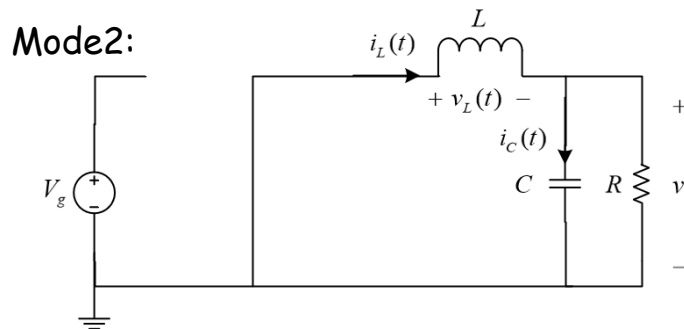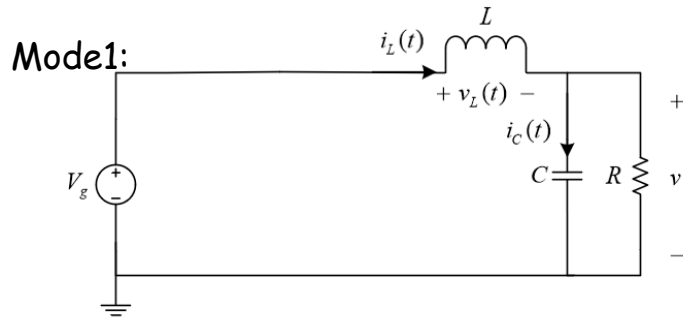


More accurate voltage ripple

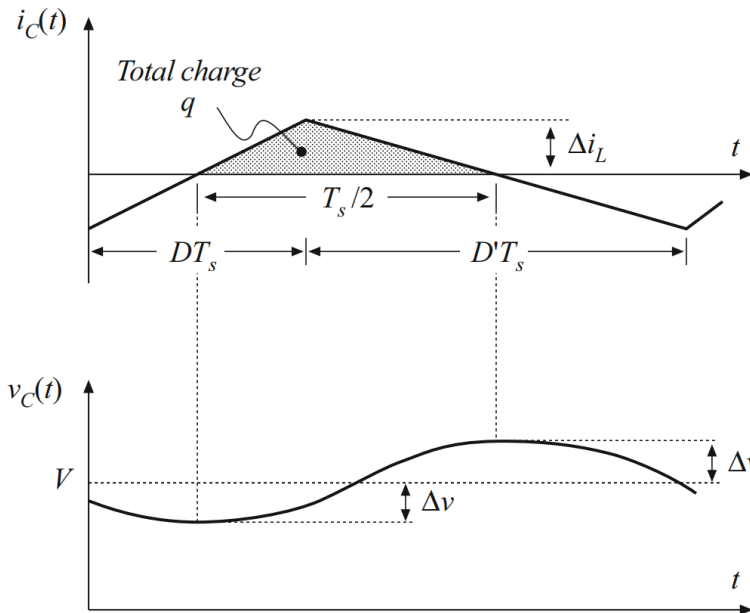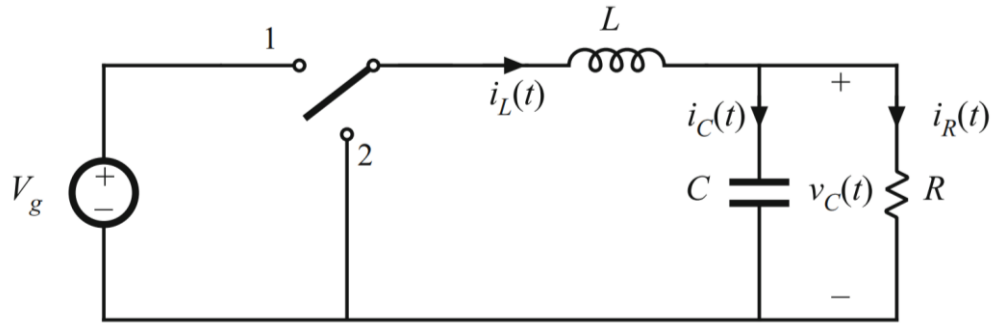


Boost converter

Boost converter(with **ideal switch**):

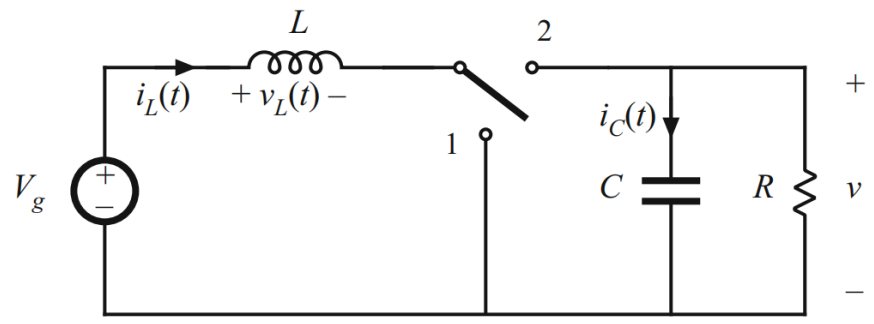


Realization using **MOSFET** and diode

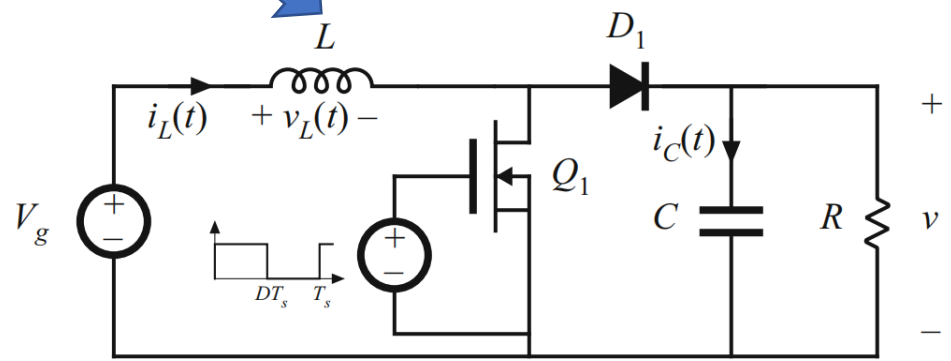


Boost Converter-Model1

The devices are assumed to be **ideal**.

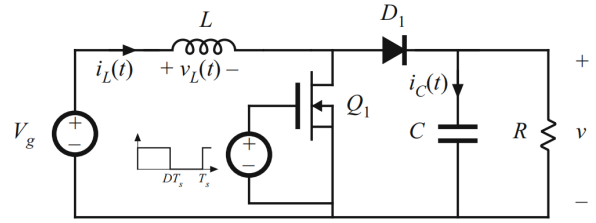


Switch in position 1

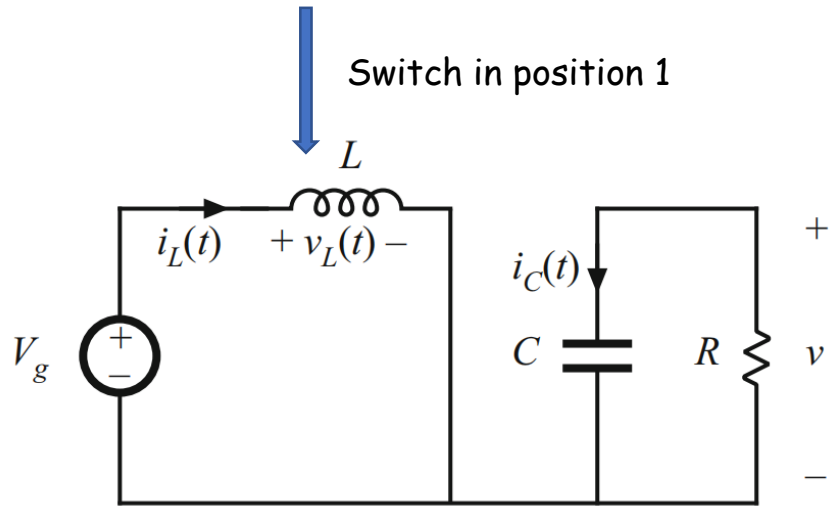


Boost Converter-Mode2


The devices are assumed to be **ideal**.

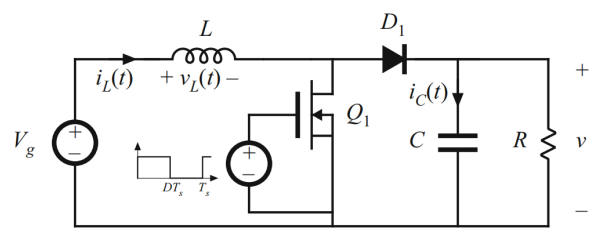


Switch in position 2

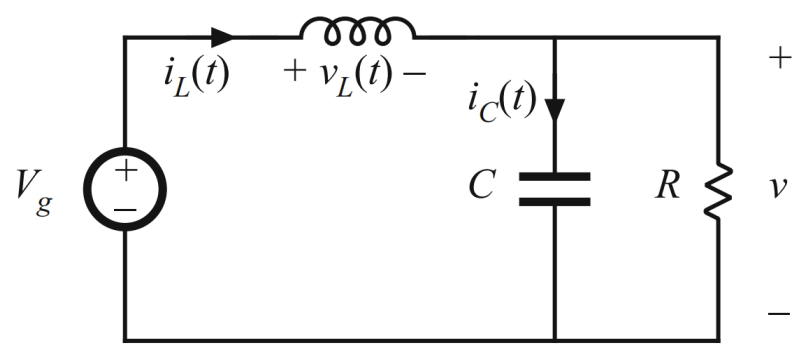


Switching mode analysis-Boost

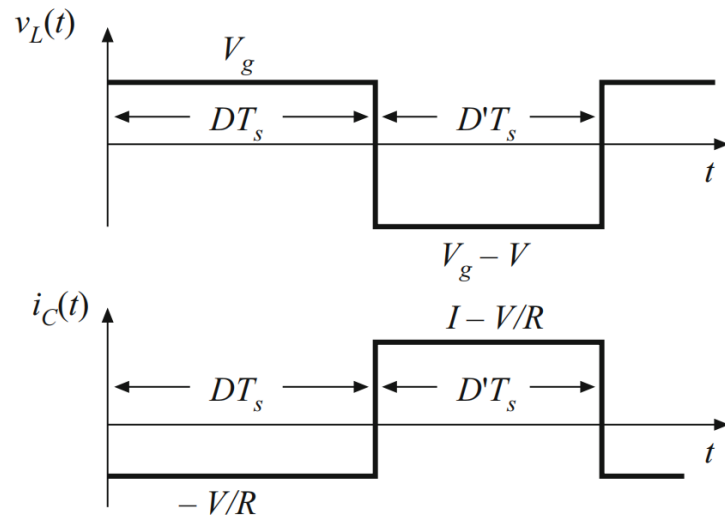


Steady-state analysis

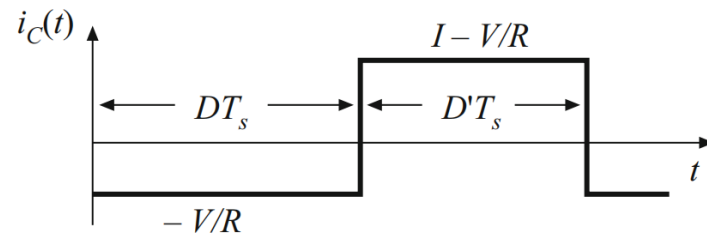

Inductor Current Ripple

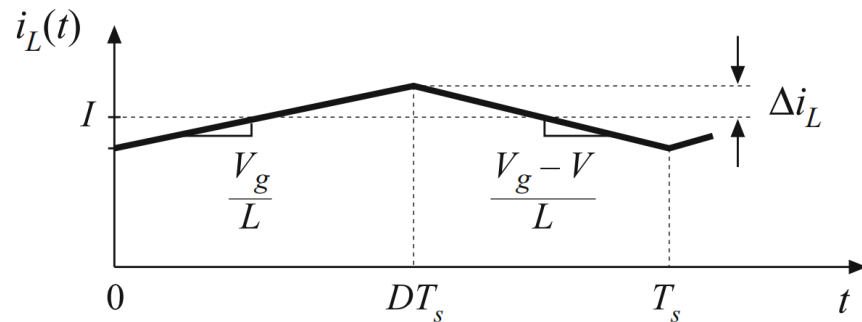

Capacitor Voltage Ripple

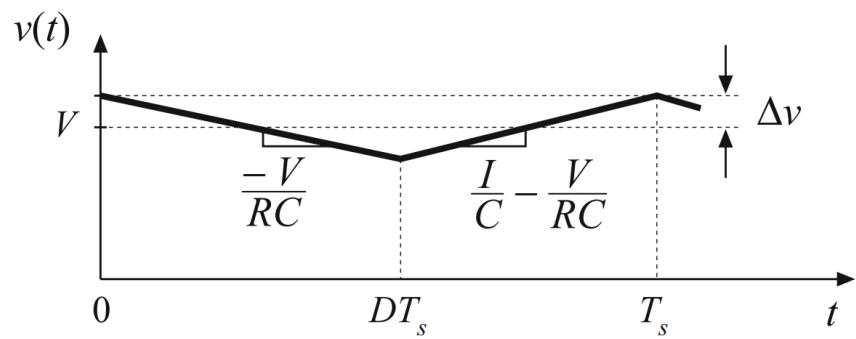

Closed loop control and negative feedback

