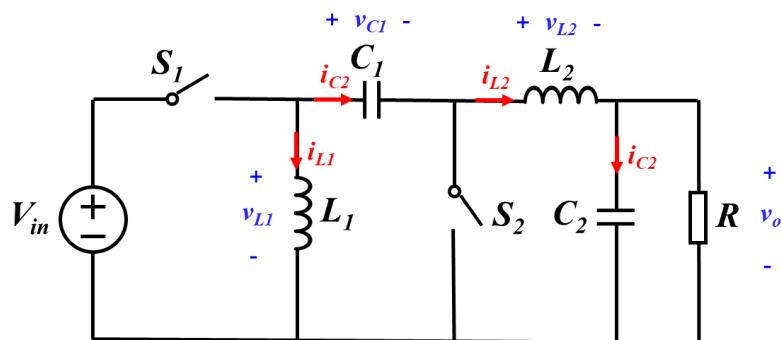


## Homework #1 (2024 Spring, EE 171)

- Deadline: Mar. 25<sup>th</sup> 8:00 a.m.
- Please submit your homework through Gradescope (Course Entry Code: 3PV4VP)
- **Handwriting is not suggested, and a poor format will lose at most 10% of your final score.**
- Giving your solution in English, solution in Chinese is not allowed.
- Plagiarism is not allowed. Those plagiarized solutions will get 0 point.

### Analysis and design of Zeta converter (200 points)



In a period, when  $0 < t < DT_s$ , switch  $S_1$  turns on,  $S_2$  turns off; when  $DT_s < t < T_s$ , switch  $S_1$  turns off,  $S_2$  turns on.

- a) Derive the dc components of each capacitor voltage and inductor current, in terms of the duty cycle  $D$ , the input voltage  $V_{in}$ , and the load resistance  $R$ . **(40 points)**
- b) Derive the current ripple and voltage ripple for all passive components. Express these quantities as functions of the switching period  $T_s$ ; the component values  $L_1$   $L_2$   $C_1$  and  $C_2$ ; the duty cycle  $D$ ; the input voltage  $V_{in}$ ; and the load resistance. Plot the current and voltage for these components. **(40 points)**
- c) Please plot the waveform of the switches. **(20 points)**
- d) In practice, switch  $S_1$  is a MOSFET and has switch-on resistor  $R_{on}$ . Switch  $S_2$  is a diode with switch-on resistor  $R_D$  and forward voltage drop  $V_D$ . Both inductors would have equivalence series resistor  $R_L$ . Derive the equivalent dc model for the converter. **(50 points)**
- e) Using the dc model, derive the efficiency for d). **(10 points)**
- f) Assume the ripples of each component exist, i.e., all the state variables would be time dependent. When the duty cycle is 0.5 and all the ripples are 20% of the corresponding dc components, please calculate the losses of all lossy components, and compare them with the those without considering the ripples. **(40 points)**