

## Homework #2 (2024 Spring, EE 171)

- Deadline: May 6<sup>th</sup> 8:00 a.m.
- Please submit your homework through Gradescope (Course Entry Code: 3PV4VP)
- Handwriting is not suggested, and a poor format will lose at most 10% of your final score.
- Giving your solution in English, solution in Chinese is not allowed.
- Plagiarism is not allowed. Those plagiarized solutions will get 0 point.
- Total: 200 points

### 1. DCM isolated SEPIC converter. (80 points)

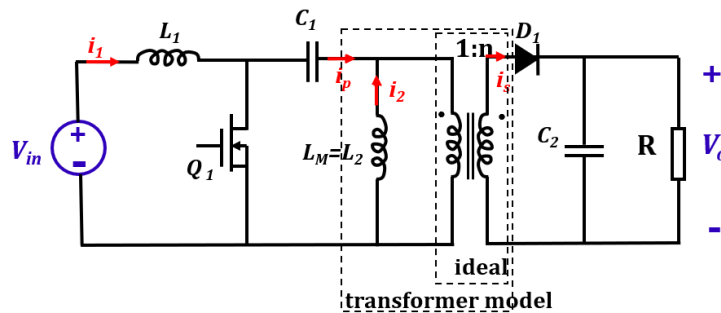


Fig. 1 Isolated SEPIC converter.

- a) Derive the expression for the conditions under which the converter operates in the DCM (for  $i_{D1}$ ). You may assume  $L_1$ ,  $C_1$  and  $C_2$  are sufficiently large. Express the result in the form  $K < K_{crit}(D)$  and derive the expression for  $K$  and  $K_{crit}(D)$ . (30 points)
- b) Derive the conversion ratio  $M(D,K)$  of the converter. (10 points)
- c) Under DCM mode, sketch the voltage and current waveforms of inductor  $L_1$  and  $L_2$ , derive the expressions of their ripple magnitudes and dc components. (20 points)
- d) Based on the current ripples, derive the voltage ripple for  $C_1$ . (20 points)

### 2. All three legs of the magnetic device illustrated in Fig. 2 are of uniform cross-sectional area $A_c$ . Legs 1 and 2 each have magnetic path length $3l$ , while leg 3 has magnetic path length $l$ . Both windings have $n$ turns. The core has permeability $\mu \gg \mu_0$ . (50 points)

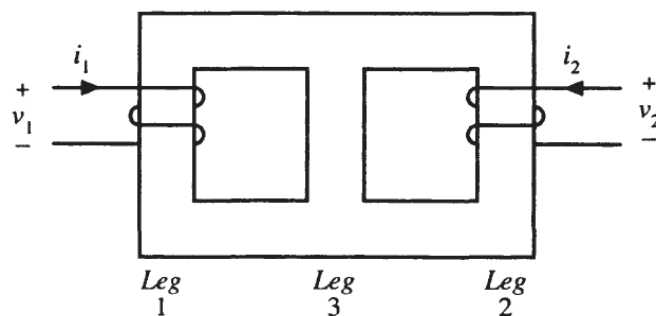


Fig. 2. Magnetic device.

- a) Sketch a magnetic equivalent circuit, and give analytical expressions for all element values. A voltage source is connected to winding 1, such that  $v_1(t)$  is a square wave of peak value  $V_{max}$  and period  $T_s$ . Winding 2 is open-circuited. (30 points)
- b) Sketch  $v_2(t)$  and label its peak value. (20 points)

3. Rotation of switching cells. A network containing switches and reactive elements has terminals a, b, and c, as illustrated in Fig.3(a). You are given that the relationship between the terminal voltages is  $V_{bc}/V_{ac} = \mu(D)$ . (70 points)

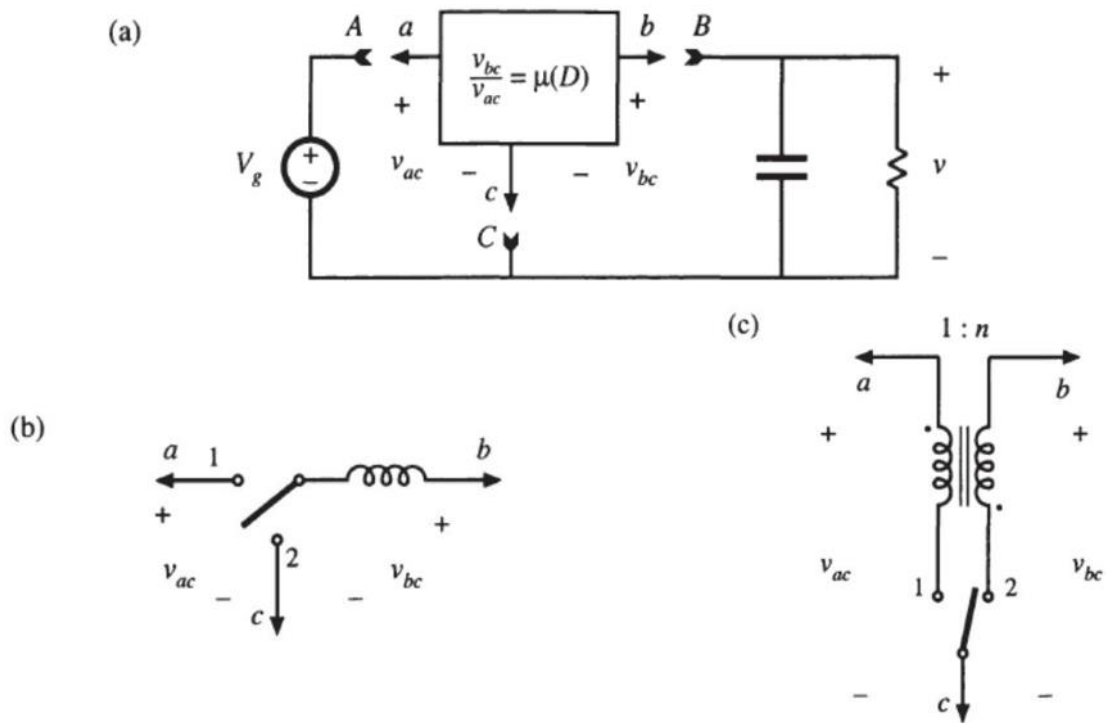


Fig. 3. Rotation of three-terminal switching cells.

- (a) Derive expressions for the source-to-load conversion ratio  $M(D) = V/V_g$ , in terms of  $\mu(D)$ , for the following three connection schemes: (30 points)
- a-A b-B c-C
  - a-B b-C c-A
  - a-C b-A c-B
- (b) Consider the three-terminal network of Fig.3 (b). Determine  $\mu(D)$  for this network. Plug your answer into your results from part (a), to verify that the buck, boost, and buck-boost converters are generated. (20 points)
- (c) Consider the three-terminal network of Fig. 3 (c). Determine  $\mu(D)$  for this network. Plug your answer into your results from part (a). What converters are generated? (20 points)