


 上海科技大学
 ShanghaiTech University

EE115 Analog Circuits Differential Pair

Prof. Haoyu Wang
 Office: SIST Bldg. 1A-225
 wanghy@shanghaitech.edu.cn





 PEARL
 电力电子与再生能源实验室


 上海科技大学
 ShanghaiTech University

Outline

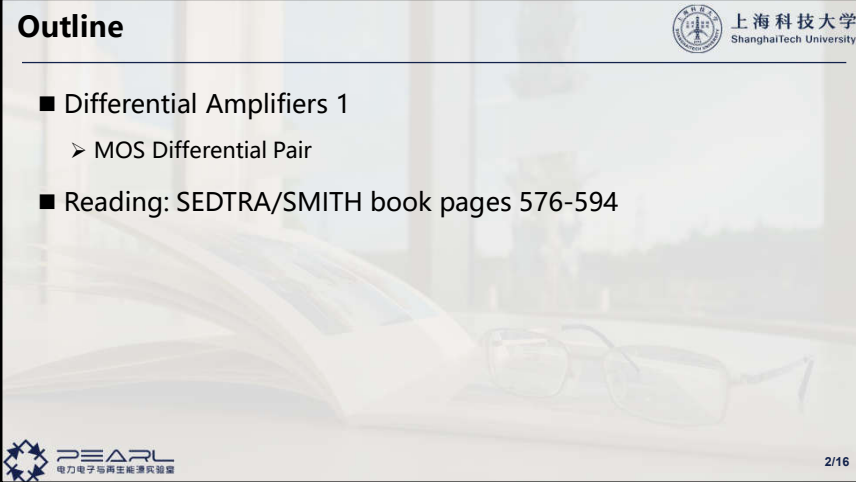- Differential Amplifiers 1
 - MOS Differential Pair
- Reading: SEDTRA/SMITH book pages 576-594





 PEARL
 电力电子与再生能源实验室

2/16

Review: Wilson MOS Mirror


 上海科技大学
 ShanghaiTech University

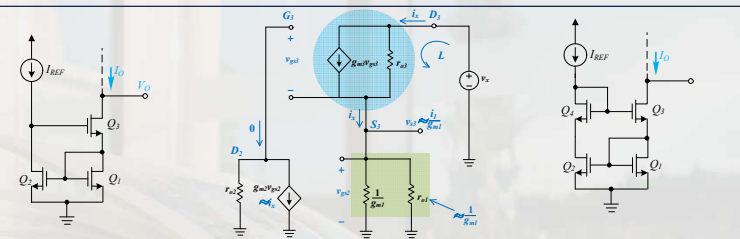

$$R_0 \equiv \frac{v_x}{i_x}$$

$$v_{gs2} \cong i_x / g_{m1}$$

$$g_{m2} v_{gs2} = g_{m2} \frac{i_x}{g_{m1}} = i_x$$

$$v_{g3} = v_{d2} = -i_x r_{o2}$$

$$v_{gs3} = v_{g3} - v_{s3} = v_{d2} - v_{gs2} = -i_x r_{o2} - \frac{i_x}{g_{m1}} \cong -i_x r_{o2}$$

$$g_{m3} v_{gs3} = -(g_{m3} r_{o2}) i_x$$

$$v_x = (i_x + g_{m3} r_{o2} i_x) r_{o3} + \frac{i_x}{g_{m1}}$$


$$R_0 \equiv \frac{v_x}{i_x} = (g_{m3} r_{o3}) r_{o2} + r_{o3} + \frac{1}{g_{m1}} \cong (g_{m3} r_{o3}) r_{o2}$$

3/16

Why Differential?


 上海科技大学
 ShanghaiTech University

- Differential circuits are much **less sensitive** to noises and interferences
- Differential configuration enables us to bias amplifiers and connect multiple stages **without using coupling or bypass capacitors**
- Differential amplifiers are widely used in ICs
 - Excellent **matching** of transistors, which is critical for differential circuits
 - Differential circuits require **more transistors**-not an issue for IC

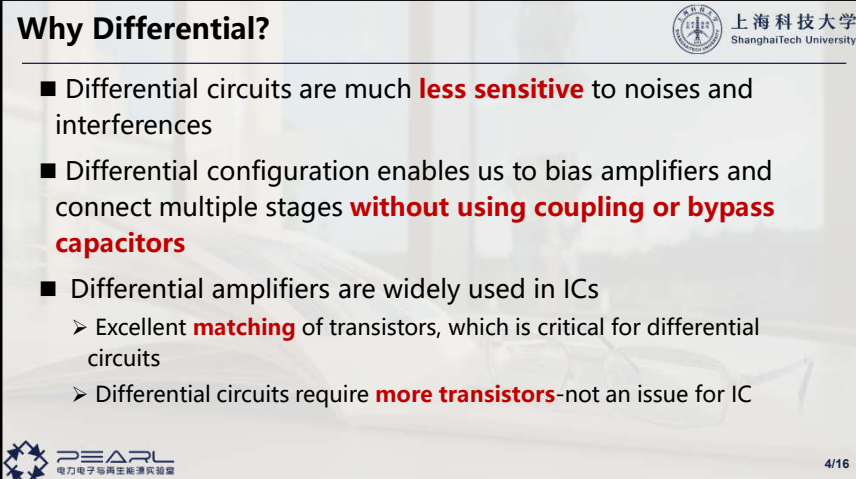


 PEARL
 电力电子与再生能源实验室


4/16

MOS Differential-Pair



- Two **matched** MOS transistors Common current bias.
- Differential signals** applied to v_{G1} and v_{G2} (**equal amplitude but opposite sign**).
- Differential outputs are produced at v_{D1} and v_{D2} .
- Note: in differential configuration with 0 differential input, V_{GS} is fixed for both Q_1 and Q_2 .

Basic Config.

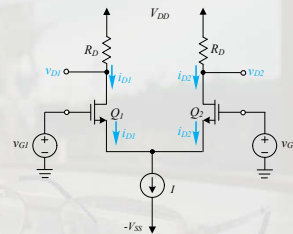

5/16


Continued (Common-Mode Input)



- The common voltages applied to both Q_1 and Q_2 are referred to as V_{CM} .
- Common mode inputs usually come from **noises** or **interferences**.
- Differential pair should **reject** V_{CM} :
 - Since $V_{GS1} = V_{GS2} = V_t + \sqrt{I/k_n}$ is fixed
 - V_{CM} simply changes the voltage at Source, V_S
- The drain currents remain fixed:

$$v_{D1} = v_{D2} = V_{DD} - \frac{I}{2} R_D$$

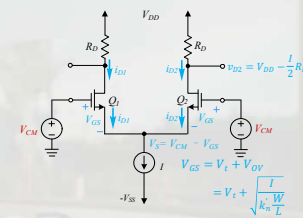Differential Pair Rejects Common-Mode Inputs



$$V_{CMmin} = -V_{SS} + V_{CS} + V_{GS}$$

$$= -V_{SS} + V_{CS} + V_t + V_{OV}$$

$$V_{CMmax} = V_D + V_t$$

$$= V_{DD} - \frac{I}{2} R_D + V_t$$



V_{CS} : Minimum voltage across current source

6/16

Example: diff pair



$V_{DD} = V_{SS} = 1.5V$, $I = 0.4mA$, $R_D = 2.5k\Omega$. Minimum voltage across current source $V_{CS} = 0.4V$. For Q_1 and Q_2 : $k_n = 4 mA/V^2$, $V_{tn} = 0.5V$.

(a) Find V_{OV} and V_{GS} for each transistor

Solution:


$$I_{D1} = I_{D2} = \frac{I}{2}$$

$$\frac{I}{2} = \frac{1}{2} k_n' (W/L) V_{OV}^2$$

$$\frac{0.4}{2} = \frac{1}{2} \times 4 V_{OV}^2$$

$$V_{OV} = 0.316V$$
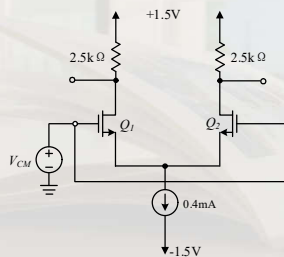
$$V_{GS} = V_t + V_{OV} = 0.5 + 0.316 \approx 0.82V$$




7/16

Continued



(b) Find V_S , I_{D1} , I_{D2} , V_{D1} , V_{D2} for 3 different V_{CM} below:

Solution:

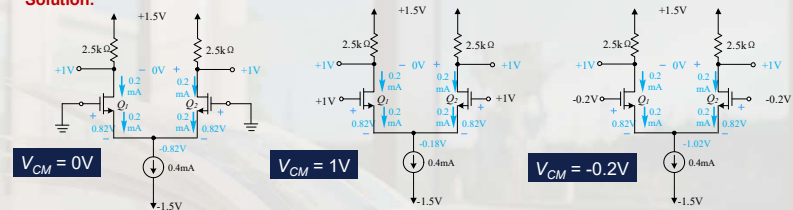

$$V_S = V_G - V_{GS} = 0 - 0.82 = -0.82V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D$$

$$= 1.5 - 0.2 \times 2.5 = +1V$$

$$V_O = V_{D2} - V_{D1} = 0V$$

$$V_S = V_G - V_{GS} = 1 - 0.82 = +0.18V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1.5 - 0.2 \times 2.5 = +1V$$

$$V_O = V_{D2} - V_{D1} = 0V$$

I_{D1} , I_{D2} , V_{D1} , V_{D2} , V_O are unchanged

$$V_S = V_G - V_{GS} = -0.2 - 0.82 = -1.02V$$

$$V_{CS} = -V_G - (-V_{SS}) = -1.02 + 1.5 = +0.48V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = +1V$$


$$V_O = V_{D2} - V_{D1} = 0V$$

8/16

Continued



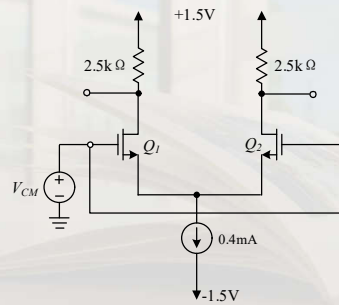(c) What is the highest/lowest permitted values of V_{CM} ?



Solution:

$$V_{CMmax} = V_t + V_D$$

$$= 0.5 + 1 = +1.5V$$


$$V_{CMmin} = -V_{SS} + V_{CS} + V_{GS}$$

$$= -1.5 + 0.4 + 0.82 = -0.28V$$

$$-0.28V \leq V_{CM} \leq +1.5V$$

9/16

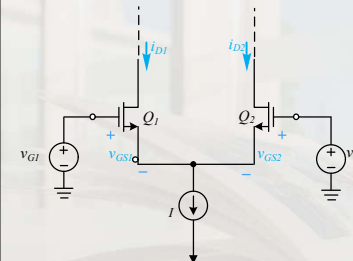Operation with Differential Input Voltage



$$i_{D1} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2$$

$$i_{D2} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS2} - V_t)^2$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{I}{2} k'_n \frac{W}{L}} \cdot v_{id}$$

$$i_{D1} + i_{D2} = I$$


$$i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L} I} \cdot \left(\frac{v_{id}}{2}\right) \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}}$$

$$i_{D2} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L} I} \cdot \left(\frac{v_{id}}{2}\right) \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}}$$



10/16

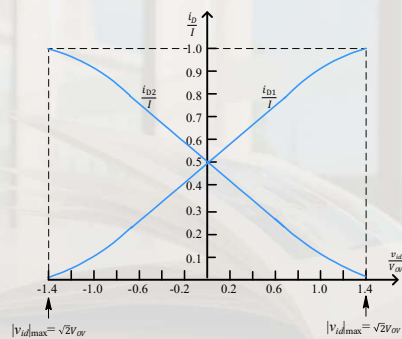Operation with Differential Input Voltage



$$i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L} I} \cdot \left(\frac{v_{id}}{2}\right) \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}}$$

$$i_{D2} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L} I} \cdot \left(\frac{v_{id}}{2}\right) \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}}$$

For small v_{id} , it could be linear:

$$i_{D1} \cong \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right)$$


$$i_{D2} \cong \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right)$$



11/16


Current of Differential Pair for Various V_{OV} 

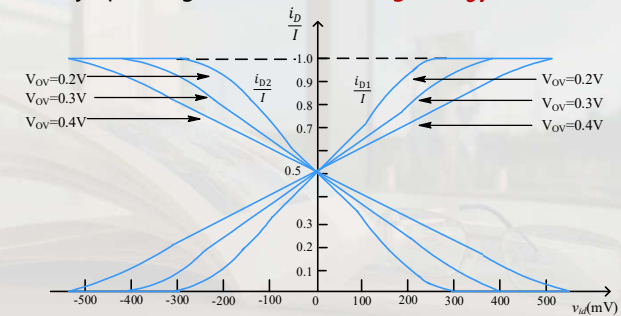- The **linear range** of operation of the MOS differential pair can be **extended** by operating the transistor at **higher V_{OV}**



12/16

Small Signal Operation

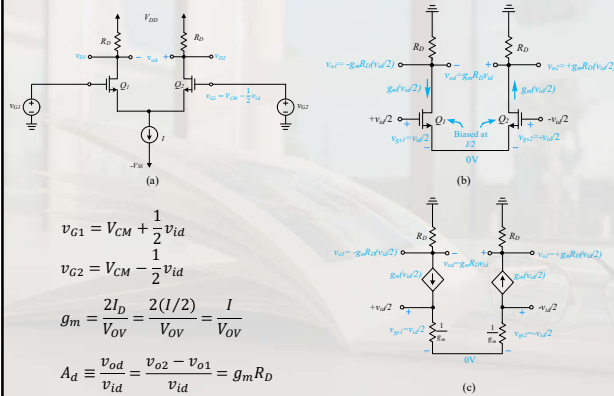

■ For **differential AC small signal**, the differential pair is **anti-symmetric**. The potential at the mid point is zero. This is called **Virtual Ground**


■ This virtual ground is obtained **without bypass capacitor** -> much smaller area and better frequency response

13/16

Differential Half Circuit



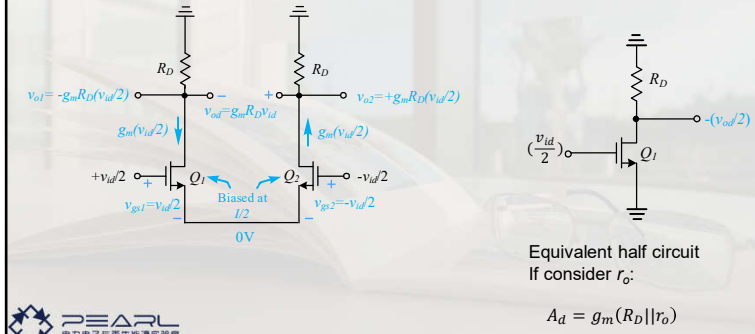■ Because the two halves of the circuits are **anti-symmetric**, and **source** is at **virtual ground**, we can simplify and just analyze the **half circuit**




Equivalent half circuit
If consider r_o :

$$A_d = g_m(R_D || r_o)$$

14/16

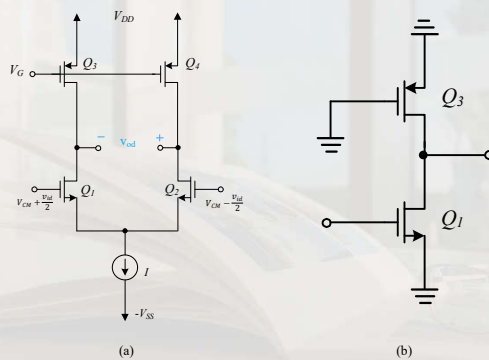Differential Amplifier w/ Current-Source Loads




$$A_d \equiv \frac{v_{od}}{v_{id}} = g_{m1}(r_{o1} || r_{o3})$$

15/16

Cascode Differential Amplifier



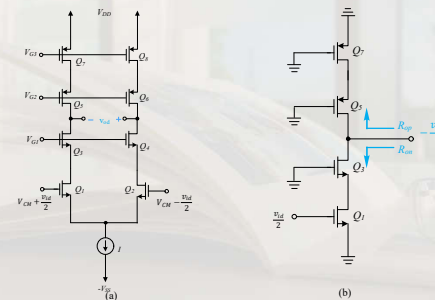■ Cascode configurations for both amplifying transistors and current source loads.



$$A_d \equiv \frac{v_{od}}{v_{id}} = g_{m1}(R_{on} || R_{op})$$

$$R_{on} = (g_{m3}r_{o3})r_{o1}$$

$$R_{op} \equiv (g_{m5}r_{o5})r_{o7}$$

16/16