

EE115A Analog Circuits

Homework 7

Due date: 12/11/2025

Note:

- Please provide enough calculation process to get full marks.
- Please submit your homework to Gradescope (code **J62G3D**) in PDF version.
- It's highly recommended to write every exercise on a single sheet of page.
- Late submissions will have points deducted according to the penalty policy.
- Please use English only to complete the assignment, solutions in Chinese are not allowed.
- Plagiarizer will get zero points.
- The full score of this assignment is 100 points.

Exercise 1. (20pt)

The two-stage CMOS op amp in Fig. P1 is fabricated in a $0.18\text{-}\mu\text{m}$ technology having

$$k'_n = 4k'_p = 400\mu\text{A}/\text{V}^2, \quad V_m = -V_{tp} = 0.4\text{V}.$$

- With A and B grounded, perform a dc design that will result in each of $Q_1, Q_2, Q_3,$ and Q_4 conducting a drain current of $100\ \mu\text{A}$ and each of Q_6 and Q_7 a current of $200\ \mu\text{A}$. Design so that all transistors operate at 0.2-V overdrive voltages. Specify the W/L ratio required for each MOSFET. Present your results in tabular form. What is the dc voltage at the output (ideally)?
- Find the input common-mode range.
- Find the allowable range of the output voltage.
- With $v_A = v_{id}/2$ and $v_B = -v_{id}/2$, find the voltage gain v_o/v_{id} . Assume an Early voltage of 6 V .

 


Fig. P1

Exercise 2. (20pt)

The two-stage op amp in **Figure P1**(show in Exercise 1) is fabricated in a 65-nm technology having $k'_n = 5.4 \times k'_p = 540 \mu\text{A}/\text{V}^2$ and $V_m = -V_{tp} = 0.35 \text{ V}$. The amplifier is operated with $V_{DD} = +1.2 \text{ V}$ and $V_{SS} = 0 \text{ V}$.

- (a) Perform a dc design that will cause each of Q_1 , Q_2 , Q_3 , and Q_4 to conduct a drain current of $200 \mu\text{A}$ and each of Q_6 and Q_7 to conduct a current of $400 \mu\text{A}$. Design so that all transistors operate at 0.15-V overdrive voltages. Specify the W/L ratio required for each MOSFET. Present all results in a table.
- (b) Find the input common-mode range.
- (c) Find the allowable range of the output voltage.
- (d) With $v_A = v_{id}/2$ and $v_B = -v_{id}/2$, find the voltage gain v_o/v_{id} . Assume an Early voltage of 2.4 V .

Exercise 3. (20pt)

Find the intrinsic gain A_0 and the unity-gain frequency f_T of an n -channel transistor fabricated in a $0.13\text{-}\mu\text{m}$ CMOS process for which $L_{\text{ov}} = 0.1L$, $\mu_n = 400\text{ cm}^2/\text{V}\cdot\text{s}$, and $V_A' = 5\text{ V}/\mu\text{m}$. The device is operated at

$$V_{\text{ov}} = 0.2\text{ V}.$$


Find A_0 and f_T for devices with $L = L_{\text{min}}$, $2L_{\text{min}}$, $3L_{\text{min}}$, $4L_{\text{min}}$, and $5L_{\text{min}}$. Present your results in a table. (Hint: For f_T , use the approximate expression

$$f_T \approx \frac{3\mu_n V_{\text{ov}}}{4\pi L^2}.)$$

Exercise 4. (20pt)

For a CS amplifier with $g_m = 5 \text{ mA/V}$, $C_{gs} = 5 \text{ pF}$, $C_{gd} = 1 \text{ pF}$, $C_L = 5 \text{ pF}$, $R_{sig} = 10 \text{ k}\Omega$, and $R'_L = 10 \text{ k}\Omega$, find τ_H and f_H . What is the percentage of τ_H that is caused by the interaction of R_{sig} with the input capacitance? To what value must R_{sig} be lowered in order to double f_H ?

Hint: High-frequency equivalent circuit for the CS amplifier.

 

Exercise 5. (20pt)

Note: This question requires simulation. Please note that you need to use **Multisim** for simulation and provide the simulation circuit and simulation results in your answer.

Ensure that you provide both **theoretical calculation** results and **simulation** results.

(a) Consider a CS amplifier having $C_{gd} = 0.3 \text{ pF}$, $R_{sig} = R_L = 20 \text{ k}\Omega$, $g_m = 4 \text{ mA/V}$, $C_{gs} = 2 \text{ pF}$, C_L (including C_{db}) $= 1 \text{ pF}$, $C_{db} = 0.2 \text{ pF}$, and $r_o = 20 \text{ k}\Omega$. Find the low-frequency gain A_M , and estimate f_H using open-circuit time constants. Hence determine the gain-bandwidth product.

(b) If a CG stage utilizing an identical MOSFET is cascaded with the CS transistor in (a) to create a cascode amplifier, determine the new values of A_M , f_H , and gain-bandwidth product. Assume R_L remains unchanged.

Hint: The common-gate amplifier with the transistor internal capacitances

