



上海科技大学
ShanghaiTech University

EE115 Analog Circuits Bias & Discrete Amp

Prof. Haoyu Wang
Office: SIST Bldg. 3-530
wanghy@shanghaitech.edu.cn




Outline

- Transistor Amplifier 3
 - Biasing
 - Discrete-Circuit Amplifiers
- Reading: SEDTRA/SMITH book pages 448-473




2/13

 
Review: Basic Single-Transistor Amp. Config.



(a) Common source (CS)

 

(b) Common Gate (CG)

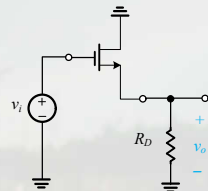

(c) Common Drain (CD)
or Source Follower



3/13

Purposes of Bias Circuit



- Provide a **stable** bias drain current
- Bias **insensitive** to variations in
 - Transistor parameters (V_b , k for MOS)
 - Temperature and other environmental changes
- Keep MOSFET in **flat part** of the I-V curves (**Saturation region**) for desired output swing



4/13

Review: I-V Curves of NMOS


 


Fig. i_D - v_{DS} characteristic for an enhancement-type NMOS transistor.

5/13

 
Example of Non-Ideal Bias

- Fixed v_{GS} from voltage divider
- Large variation in i_D due to **device** variations
- Large **temperature** dependence
 - μ_n and V_t are temperature sensitive



6/13

Adding Source Resistance R_S

 


- R_S provides a **negative feedback**
 - If $I_D \uparrow$, $V_{GS} \downarrow \rightarrow I_D \downarrow$
 - If $I_D \downarrow$, $V_{GS} \uparrow \rightarrow I_D \uparrow$
- Stabilize I_D** w.r.t. device and temperature variations


7/13

Practical Implementations

Single Power Supply

 

Dual Power Supply

 


How to select R_D ?

Rule of thumb: R_D , V_{DS} and R_S each has $1/3 V_{DD}$ voltage drop

8/13

Bias Example

 Given: $I_D = 0.5 \text{ mA}$; $V_t = 1 \text{ V}$, $k_n = 1 \text{ mA/V}^2$, $\lambda = 0$. $V_{DD} = 15 \text{ V}$.
Calculate change in I_D when the MOSFET is replaced with another one with identical k_n but $V_t = 1.5 \text{ V}$



Solution:

Rule of thumb: R_D , V_{DS} and R_S each has

$1/3 V_{DD}$ voltage drop

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{15 - 10}{0.5} = 10 \text{ k}\Omega$$

$$R_S = \frac{V_S}{I_D} = \frac{5}{0.5} = 10 \text{ k}\Omega$$

$$I_D = \frac{1}{2} k_n (W/L) V_{OV}^2$$

$$0.5 = \frac{1}{2} \times 1 \times V_{OV}^2$$

$$V_{GS} = V_t + V_{OV} = 1 + 1 = 2 \text{ V}$$

$$V_G = V_S + V_{GS} = 5 + 2 = 7 \text{ V}$$

Replace

$$I_D = \frac{1}{2} \times 1 \times (V_{GS} - 1.5)^2$$

$$V_G = V_{GS} + I_D R_S$$

$$7 = V_{GS} + 10 I_D$$

$$I_D = 0.455 \text{ mA}$$

$$\Delta I_D = 0.455 - 0.5 = -0.045 \text{ mA}$$

Bias with large drain-to-gate R_G

 


Fig. Biasing the MOSFET using a large drain-to-gate feedback resistance, R_G .

$$V_{GS} = V_{DS} = V_{DD} - R_D I_D$$

$$V_{DD} = V_{GS} + R_D I_D$$

■ R_D provides a negative feedback


➢ $I_D \uparrow$, $V_{GS} \downarrow \rightarrow I_D \downarrow$

➢ $I_D \downarrow$, $V_{GS} \uparrow \rightarrow I_D \uparrow$

■ **Stabilize I_D** w.r.t. device and temperature variations

Coupling. Cap to Separate AC Signal from DC Bias

 - Coupling capacitor is **DC-open** and **AC-short**
- **Prevent** signal source to **change** bias condition
- Coupling capacitor creates a **lower bound** of operating frequency




CS Amplifier with Bias Circuit

- Both coupling and bypass capacitors are DC-open and AC-short

Capacitively Coupled Amplifier:

DC:


AC:

 

$$R_{in} = R_{G1} || R_{G2}$$

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_D || R_L || r_o)$$

 Typical Freq. Response of Capacitively Coupled Amp.



Bandwidth

$$BW = f_H - f_L$$

$$BW \cong f_H$$

Gain-bandwidth product

$$GB \cong |A_M|BW$$