




# EE115 Analog Circuits

## Differential Pair

Prof. Haoyu Wang  
Office: SIST Bldg. 3-530  
wanghy@shanghaitech.edu.cn



## Review: Wilson MOS Mirror

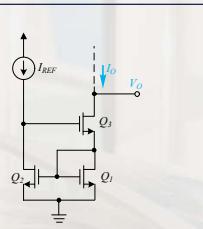


$$R_o \equiv \frac{v_x}{i_x}$$

$$v_{gs2} \cong i_x/g_{m1}$$

$$g_{m2}v_{gs2} = g_{m2} \frac{i_x}{q_{m1}} = i_x$$

$$v_{g3} = v_{d2} = -i_x r_{o2}$$

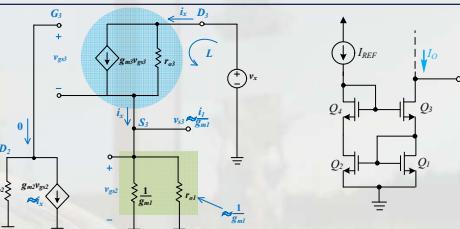

$$v_{gs3} = v_{g3} - v_{s3} = v_{d2} - v_{gs2} = -i_x r_{o2} - \frac{i_x}{g_{m1}} \cong -i_x r_{o2}$$

$$g_{m3}v_{gs3} = -(g_{m3}r_{o2})i_x$$

$$\mathbf{v}_x = (\mathbf{i}_x + g_{m3} r_{o2} \mathbf{i}_x) r_{o3} + \frac{\mathbf{i}_x}{a_{m1}}$$

$$B_x = \frac{v_x}{r} = (a_x - x_{\perp})x_{\parallel} + x_{\perp} + \dots$$

$$R_o \equiv \frac{\dot{x}}{i_x} \equiv (g_{m3}r_{o3})r_{o2} + r_{o3} + \frac{\dot{x}}{g_{m1}} \equiv (g_{m3}r_{o3})r_{o2}$$



- Differential Amplifiers 1
  - MOS Differential Pair
- Reading: SEDTRA/SMITH book pages 576-594



## Why Differential?

- Differential circuits are much **less sensitive** to noises and interferences
- Differential configuration enables us to bias amplifiers and connect multiple stages **without using coupling or bypass capacitors**
- Differential amplifiers are widely used in ICs
  - Excellent **matching** of transistors, which is critical for differential circuits
  - Differential circuits require **more transistors**-not an issue for IC




## MOS Differential-Pair



- Two **matched** MOS transistors Common current bias.
- **Differential signals** applied to  $V_{G1}$  and  $V_{G2}$  (**equal amplitude but opposite sign**).
- Differential outputs are produced at  $V_{D1}$  and  $V_{D2}$ .
- Note: in differential configuration with 0 differential input,  $V_{GS}$  is fixed for both  $Q_1$  and  $Q_2$ .

Basic Config.

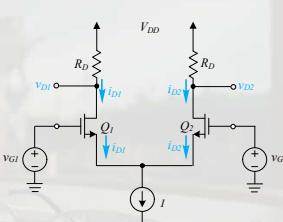

5/16

## Example: diff pair



$V_{DD} = V_{SS} = 1.5V$ ,  $I = 0.4mA$ ,  $R_D = 2.5k\Omega$ . Minimum voltage across current source  $V_{CS} = 0.4V$ . For  $Q_1$  and  $Q_2$ :  $k_n = 4 \text{ mA/V}^2$ ,  $V_{tn} = 0.5V$ .

(a) Find  $V_{OV}$  and  $V_{GS}$  for each transistor

**Solution:**


$$I_{D1} = I_{D2} = \frac{I}{2}$$

$$\frac{I}{2} = \frac{1}{2} k_n (W/L) V_{OV}^2$$

$$\frac{0.4}{2} = \frac{1}{2} \times 4 V_{OV}^2$$

$$V_{OV} = 0.316V$$
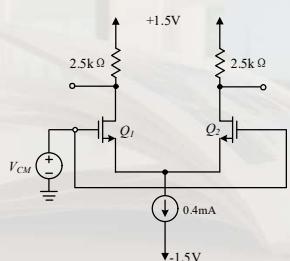
$$V_{GS} = V_t + V_{OV} = 0.5 + 0.316 \approx 0.82V$$



7/16

## Continued (Common-Mode Input)



■ The common voltages applied to both  $Q_1$  and  $Q_2$  are referred to as  $V_{CM}$


■ Common mode inputs usually come from **noises or interferences**.

■ Differential pair should **reject**  $V_{CM}$ :

- Since  $V_{GS1} = V_{GS2} = V_t + \sqrt{I/k_n}$  is fixed
- $V_{CM}$  simply changes the voltage at Source,  $V_S$

■ The drain currents remain fixed:
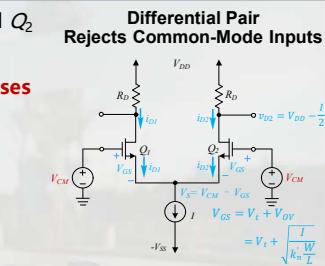
$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D$$



$$V_{CMmin} = -V_{SS} + V_{CS} + V_{GS}$$

$$= -V_{SS} + V_{CS} + V_t + V_{OV}$$

$$V_{CMmax} = V_D + V_t$$

$$= V_{DD} - \frac{I}{2} R_D + V_t$$



$V_{GS}$ : Minimum voltage across current source


6/16

## Continued



(b) Find  $V_S$ ,  $I_{D1}$ ,  $I_{D2}$ ,  $V_{D1}$ ,  $V_{D2}$  for 3 different  $V_{CM}$  below:

**Solution:**

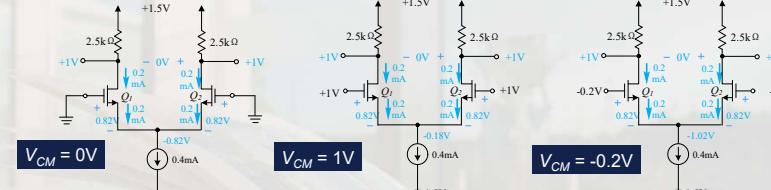

$$V_S = V_G - V_{GS} = 0 - 0.82 = -0.82V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1.5 - 0.2 \times 2.5 = +1V$$

$$= 1.5 - 0.2 \times 2.5 = +1V$$

$$V_O = V_{D2} - V_{D1} = 0V$$

$$V_S = V_G - V_{GS} = 1 - 0.82 = +0.18V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1.5 - 0.2 \times 2.5 = +1V$$

$$= 1.5 - 0.2 \times 2.5 = +1V$$

$$V_O = V_{D2} - V_{D1} = 0V$$

$$V_S = V_G - V_{GS} = -0.2 - 0.82 = -1.02V$$

$$I_{D1} = I_{D2} = \frac{I}{2} = 0.2mA$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1.5 - 0.2 \times 2.5 = +1V$$

$$= 1.5 - 0.2 \times 2.5 = +1V$$


$$V_O = V_{D2} - V_{D1} = 0V$$

$I_{D1}, I_{D2}, V_{D1}, V_{D2}, V_O$  are unchanged

8/16

## Continued

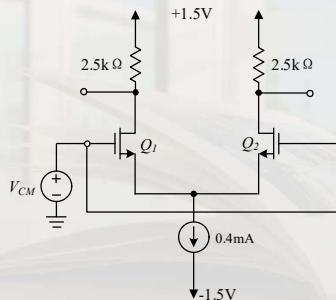(c) What is the highest/lowest permitted values of  $V_{CM}$ ?



**Solution:**


$$V_{CMmax} = V_t + V_D = 0.5 + 1 = +1.5V$$

$$V_{CMmin} = -V_{SS} + V_{CS} + V_{GS} = -1.5 + 0.4 + 0.82 = -0.28V$$

$$-0.28V \leq V_{CM} \leq +1.5V$$

9/16
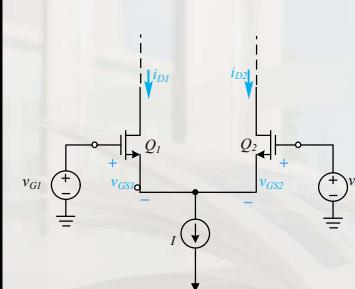
## Operation with Differential Input Voltage



$$i_{D1} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2$$

$$i_{D2} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS2} - V_t)^2$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{1}{2} k'_n \frac{W}{L} \cdot v_{id}}$$

$$i_{D1} + i_{D2} = I$$


$$i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L} I \cdot \left(\frac{v_{id}}{2}\right)} \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n W}}$$

$$i_{D2} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L} I \cdot \left(\frac{v_{id}}{2}\right)} \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n W}}$$



10/16
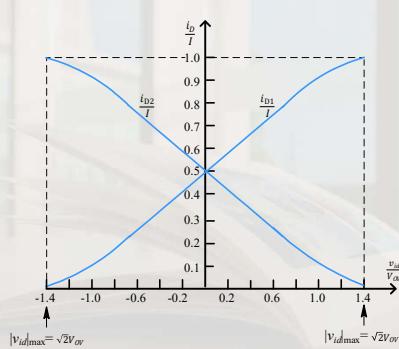
## Operation with Differential Input Voltage



$$i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L} I \cdot \left(\frac{v_{id}}{2}\right)} \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n W}}$$

$$i_{D2} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L} I \cdot \left(\frac{v_{id}}{2}\right)} \cdot \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n W}}$$

For small  $v_{id}$ , it could be linear:


$$i_{D1} \approx \frac{I}{2} + \left(\frac{I}{V_{ov}}\right) \left(\frac{v_{id}}{2}\right)$$

$$i_{D2} \approx \frac{I}{2} - \left(\frac{I}{V_{ov}}\right) \left(\frac{v_{id}}{2}\right)$$

11/16

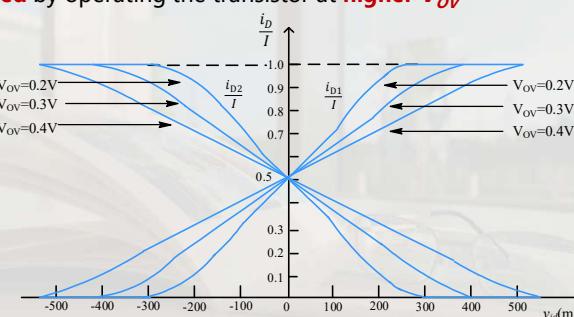
## Current of Differential Pair for Various $V_{ov}$

- The **linear range** of operation of the MOS differential pair can be **extended** by operating the transistor at **higher  $V_{ov}$**



12/16

## Small Signal Operation

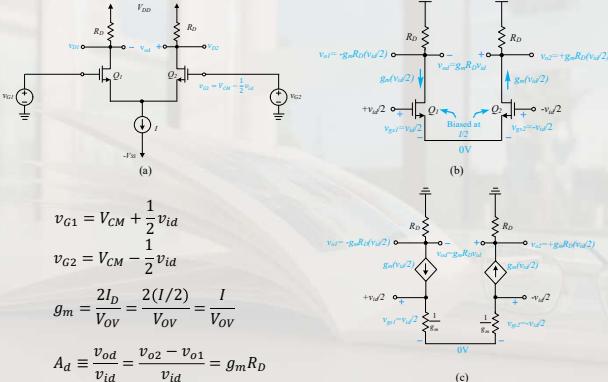


- For **differential AC small signal**, the differential pair is **anti-symmetric**. The potential at the mid point is zero. This is called **Virtual Ground**
- This virtual ground is obtained **without bypass capacitor** -> much smaller area and better frequency response

13/16
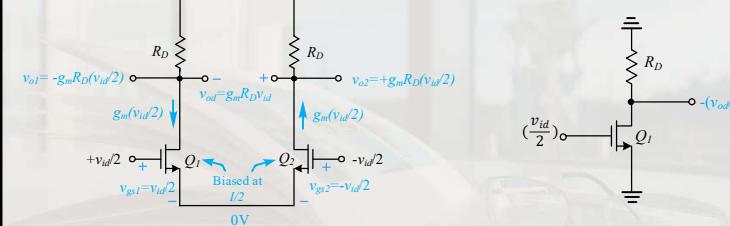
## Differential Half Circuit

- Because the two halves of the circuits are **anti-symmetric**, and **source** is at **virtual ground**, we can simplify and just analyze the **half circuit**




Equivalent half circuit  
If consider  $r_o$ :

$$A_d = g_m (R_D || r_o)$$

14/16

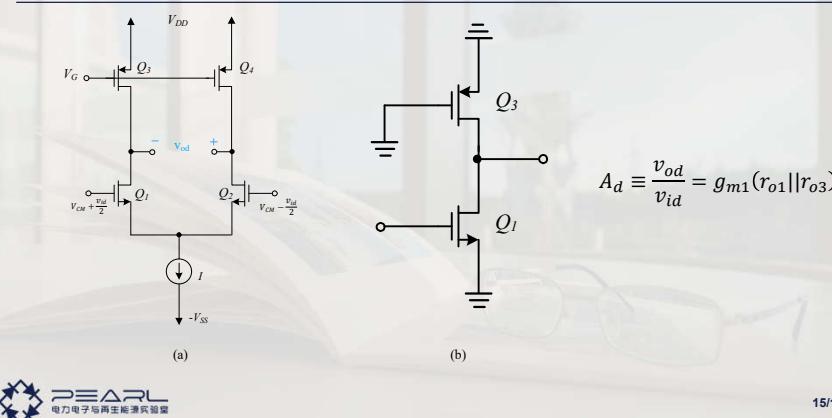
## Differential Amplifier w/ Current-Source Loads



15/16
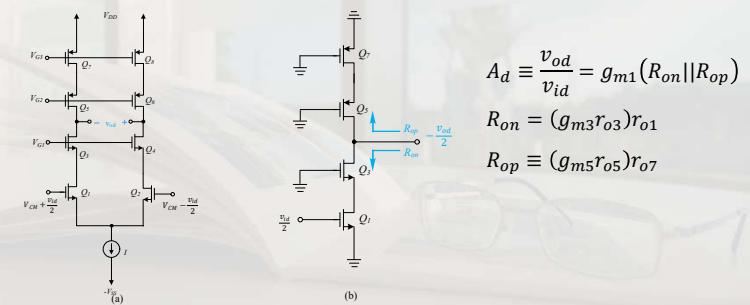
## Cascode Differential Amplifier

- Cascode configurations for both amplifying transistors and current source loads.



16/16