

EE115 Analog Circuits Frequency Response

Prof. Haoyu Wang
Office: SIST Bldg. 3-530
wanghy@shanghaitech.edu.cn



Review: Discrete vs Integrated Circuits

Discrete Circuits

- Resistors and capacitors are frequently used
- AC coupled with **coupling capacitors**
- High DC power supply voltage
- Transistor choice limited to available parts
- Mostly BJT, some MOS

IC

- Use mostly transistors
 - Resistors and capacitors occupy **too much areas**
- Mostly **DC coupled** (without capacitors)
- Low DC power supply voltage (~1V)
- Can vary device size
- Predominantly CMOS
 - BiCMOS provides BJT

Outline


- High Frequency Response 2
 - Frequency Response of Common-Source Amplifiers
 - Open-Circuit Time Constants (OCTC) Method
 - High Frequency Response of Common Gate Amplifiers
- Reading: SEDTRA/SMITH book pages 686-715



Review: CS Amplifier with Bias Circuit

- Both coupling and bypass capacitors are DC-open and AC-short

Capacitively Coupled Amplifier

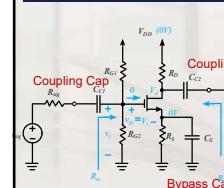


DC



$R_{in} = R_{G1} || R_{G2}$


$v_o = v_{sig} \frac{R_o}{R_{in} + R_{sig}}$

AC

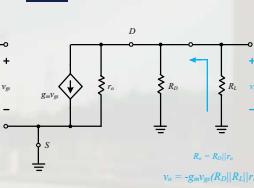

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_D || R_L || r_o)$$

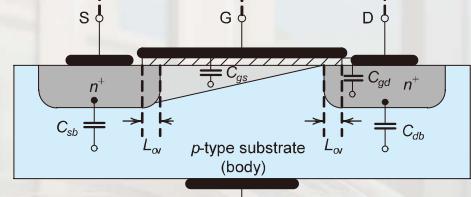Review: Cross Section of MOSFET w/ Internal Cap.



■ Gate/Source capacitance:

$$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov}$$

where

- $C_{ox} = \epsilon_{ox} / t_{ox}$ [F/cm²]
- W: Transistor width
- L: Gate Length
- $C_{ov} = W L_{ox} C_{ox}$
- L_{ox} : overlap between Gate/Source or Gate/Drain, typically 0.05-0.1L

■ Gate/Drain capacitance:

$$C_{gd} = C_{ov}$$


5/17

- MOSFET has several internal capacitances, which take time to charge/discharge, limiting the **transistor speed**.

Review: Unity-Gain Frequency, f_T

- f_T : frequency at which short-circuit current gain = 1

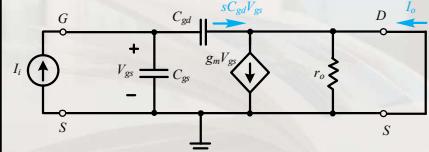- FoM for transistor speed
- Drain is grounded (short-circuit load)



$$I_o = g_m V_{gs} - s C_{gd} V_{gs} = (g_m - s C_{gd}) V_{gs}$$

$$V_{gs} = \frac{I_o}{s(C_{gs} + C_{gd})}$$

$$\text{Combine: } \frac{I_o}{I_i} = \frac{g_m - s C_{gd}}{s(C_{gs} + C_{gd})}$$

$$\left| \frac{I_o}{I_i} \right| (s = j\omega_T) \cong \frac{g_m}{\omega_T (C_{gs} + C_{gd})} = 1$$


$$\text{Unity gain freq.: } \omega_T = \frac{g_m}{(C_{gs} + C_{gd})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

As gate length reduces in advanced technology, C_{gs} reduces and f_T increases

7/17

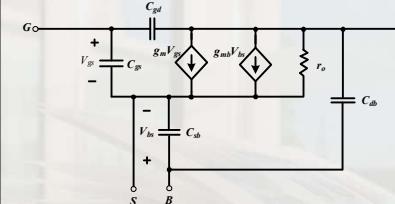Review: MOSFET High-f Equivalent-Circuit Model



■ Source is connected to the body (no **body effect**)

■ Capacitance between drain and body **C_db** neglected

6/17

High Frequency Response of CS Amplifier

$$(a) I_{gd} = s C_{gd} (V_{gs} - V_o)$$

$$(b) I_{gd} = s C_{gd} (V_{gs} - V_o)$$

$$R_L' = R_L || r_o$$

$$I_{gd} = s C_{gd} (V_{gs} - V_o)$$

$$= s C_{gd} [V_{gs} - (-g_m R'_L V_{gs})]$$

$$= s C_{gd} (1 + g_m R'_L) V_{gs}$$

$$V_o = -(g_m V_{gs} - I_{gd}) R'_L$$

$$\frac{V_o}{V_{gs}} = -[g_m - s C_{gd} (1 - g_m R'_L)] R'_L \cong -g_m R'_L$$

Middle band


8/17

Tedious, not intuitive.

Miller Capacitance



Equivalent Circuit

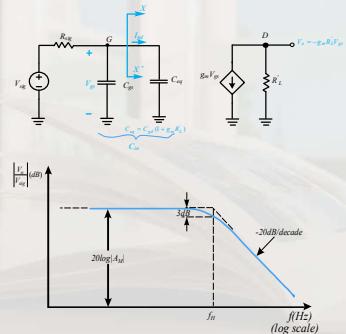

$$I_{gd} = sC_{gd}(1 + g_m R'_L) V_{gs} = sC_{eq} V_{gs}$$

$$C_{eq} = C_{gd}(1 + g_m R'_L)$$

Miller effect, $(1 + g_m R'_L)$ is known as Miller multiplier

$$V_{ds} = \frac{1}{1 + \frac{s}{\omega_p}} V_{sig}$$

Where, ω_p is the pole frequency of the STC circuit

$$\omega_p = 1/(C_{in} R_{sig})$$

$$\frac{V_o}{V_{sig}} = -\frac{g_m R'_L}{1 + \frac{s}{\omega_p}} = \frac{A_M}{1 + \frac{s}{\omega_H}}$$

■ Large input capacitance in CS amplifier due to Miller effect, which greatly reduced the bandwidth of CS amp

9/17



电力电子与再生能源实验室

Open-Circuit Time Constant (OCTC) Method for High Cut-off Frequency



- Replace all **capacitors** by **open circuit**
- Signal source** becomes **zero**
- Consider one capacitor at a time, find resistance R_i **seen** by the i -th capacitor, C_i

$$\omega_H \approx \frac{1}{\sum_i C_i R_i}$$




11/17

Miller's Theorem



Miller Equivalent

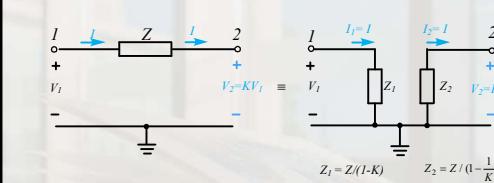

Input side:

$$I_1 = \frac{V_1}{Z_1} = I = \frac{V_1 - KV_1}{Z}$$

$$Z_1 = \frac{Z}{(1 - K)}$$

Output side:

$$I_2 = \frac{0 - V_2}{Z_2} = \frac{0 - KV_1}{Z_2} = I = \frac{V_1 - KV_1}{Z}$$

$$Z_2 = \frac{Z}{(1 - \frac{1}{K})}$$

10/17




电力电子与再生能源实验室

Applying OCTC to CS Amplifier




1. Only consider C_{gs} , find R_{gs}

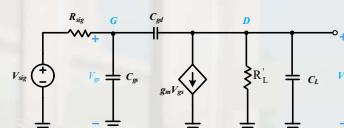

$$R_{gs} = R_{sig} \quad \dots (1)$$

Capacitor = Open Signal source = 0

2. Only consider C_{gd} , find R_{gd}

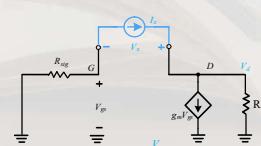

$$V_{gs} = -I_x R_{sig}$$

$$V_d = V_x + V_{gs}$$

$$I_x = g_m V_{gs} + \frac{V_d}{R'_L}$$

$$I_x = g_m V_{gs} + \frac{V_x + V_{gs}}{R'_L}$$


$$R_{gd} \equiv \frac{V_x}{I_x} = R_{sig}(1 + g_m R'_L) + R'_L \quad \dots (2)$$

12/17

Applying OCTC to CS Amplifier

$$R_{gs} = R_{sig} \dots (1)$$
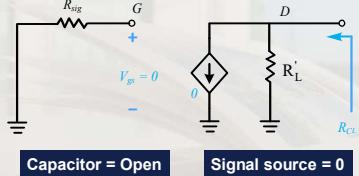
$$R_{gd} = R_{sig}(1 + g_m R'_L) + R'_L \dots (2)$$



3. Only consider C_L , find R_{CL}

$$R_{CL} = R'_L \dots (3)$$

$$\tau_H = C_{gs}R_{gs} + C_{gd}R_{gd} + C_L R_{CL}$$

$$= C_{gs}R_{sig} + C_{gd}[R_{sig}(1 + g_m R'_L) + R'_L] + C_L R'_L$$


$$f_H = \frac{1}{2\pi\tau_H}$$

$$\tau_H = [C_{gs} + C_{gd}(1 + g_m R'_L)]R_{sig} + (C_{gd} + C_L)R'_L$$


- Time constant from **input** port of Miller Equivalent Circuit
- Time constant from **output** port of Miller Equivalent Circuit

13/17

High f Response of Common Gate Amplifier

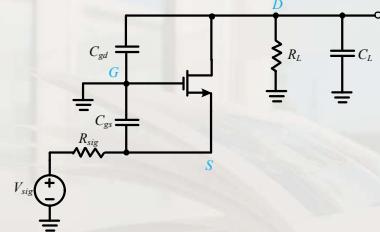

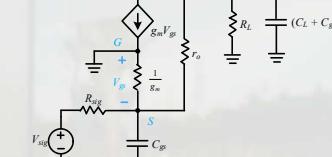
(a) CG amplifier with cap.(ac equivalent)



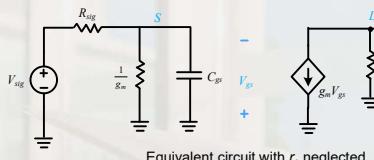(b) Equivalent ac small signal model

14/17

High f Response of Discrete Circuit CG Amplifier



- Discrete circuit CG: early effect can be ignored
- **No Miller effect** since both capacitance are grounded
- The dominant term is likely to be $C_{gs}(R_{sig} \parallel \frac{1}{g_m})$, which is small \rightarrow High f_H
 - Common-Gate is a **broadband** amplifier

$$f_{p1} = \frac{1}{2\pi C_{gs} (R_{sig} \parallel \frac{1}{g_m})}$$

$$\tau_{gs} = C_{gs} \left(R_{sig} \parallel \frac{1}{g_m} \right) = \frac{1}{2\pi f_{p1}}$$

$$f_{p2} = \frac{1}{2\pi (C_{gd} + C_L) R_L}$$

$$\tau_{gd} = (C_L + C_{gd}) R_L = \frac{1}{2\pi f_{p2}}$$

$$\tau_H = C_{gs} \left(R_{sig} \parallel \frac{1}{g_m} \right) + (C_L + C_{gd}) R_L$$


$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{\frac{1}{f_{p1}} + \frac{1}{f_{p2}}}$$

Why early effect can be ignored in discrete circuit?

15/17

High f Response of IC CG Amplifier

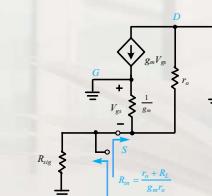- IC CG: early effect must be **considered**.
- Apply **OCTC** method.



$$R_{ds} = R_{sig} \parallel R_{in}$$


$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} \cong \frac{r_o + R_L}{g_m r_o}$$

$$R_{dg} = R_L \parallel R_o$$

$$R_o = r_o + R_{sig} + g_m r_o R_{sig}$$

$$\tau_H = \tau_{gs} + \tau_{gd}$$

$$f_H = \frac{1}{2\pi\tau_H}$$

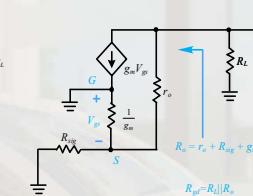

$$R_{ds} = R_{sig} \parallel R_{in}$$

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} \cong \frac{r_o + R_L}{g_m r_o}$$

$$R_{dg} = R_L \parallel R_o$$


$$R_o = r_o + R_{sig} + g_m r_o R_{sig}$$

$$\tau_H = \tau_{gs} + \tau_{gd}$$

16/17

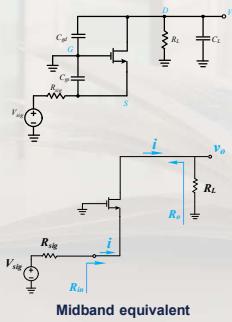Example: frequency response of CG amplifier

Consider a CG amplifier with $g_m = 2mA/V$, $r_o = 20k\Omega$, $C_{gs} = 20fF$, $C_{gd} = 5fF$, $C_L = 25fF$, $R_{sig} = 20k\Omega$, and $R_L = 20k\Omega$. Determine the input resistance, the midband gain, and the upper 3-dB frequency f_H .



Solution:

$$v_o = iR_L$$

$$v_{sig} = i(R_{sig} + R_{in})$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{R_L}{R_{sig} + R_{in}}$$

$$= 20 + 20 + 40 \times 20 = 840k\Omega$$

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o}$$

$$= \frac{20 + 20}{1 + (2 \times 20)} = 0.98k\Omega$$

$$G_v = \frac{20}{20 + 0.98} = \frac{0.95V}{V}$$

$$= 18.6 \times 10^{-12} + 585 \times 10^{-12} = 603.6ps$$

$$R_{gs} = R_{sig} || R_{in}$$

$$= 20 || 0.98 = 0.93k\Omega$$

$$f_H = \frac{1}{2\pi\tau_H}$$

$$= \frac{1}{2\pi \times 603.6 \times 10^{-12}} = 263.7MHz$$

Midband equivalent

17/17