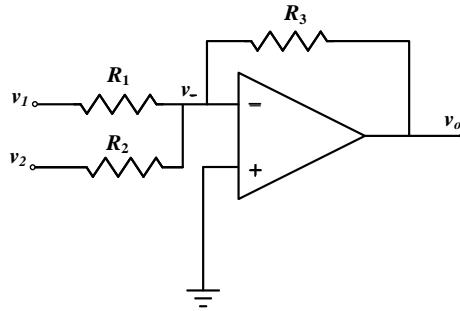


## 1. (24 points) Difference Amplifier

Given an ideal amplifier circuit as illustrated in the figure below.  $R_1 = 2 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $R_3 = 51 \text{ k}\Omega$ ,  $v_1(t) = (0.01\sin 3770t)V$ , and  $v_2(t) = (0.05\sin 10000t)V$ .



- (a) (6 points) Write an expression for the output voltage  $v_o(t)$ .
- (b) (6 points) Write an expression for the voltage appearing at the inverting input  $v_-$ .
- (c) (6 points) What is the input resistance at terminal  $v_1$ ?
- (d) (6 points) What is the output resistance at terminal  $v_o$ ?



## 2. (18 points) DC Imperfections

A particular inverting amplifier with a nominal gain of  $-100 \text{ V/V}$  uses an imperfect op amp in conjunction with  $100 \text{ k}\Omega$  and  $10 \text{ M}\Omega$  resistors. The output voltage is found to be  $+9.31\text{V}$  when measured with the input open; and  $+9.09\text{V}$  with the input grounded.

- (a) (6 points) Plot the circuit configuration. Mark the input port  $v_i$ , the output port  $v_o$ , as well as the values of resistances.
- (b) (6 points) What is the bias current of this amplifier? In what direction does it flow?
- (c) (6 points) Estimate the value of the input offset voltage.
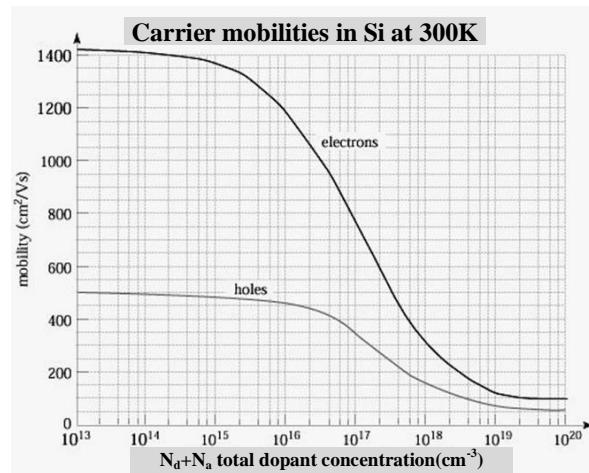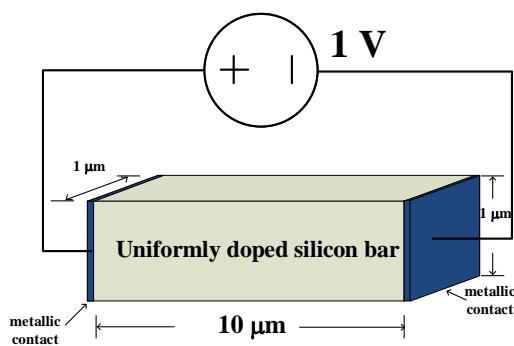
## 3. (18 points) Semiconductor Basics

Consider a Si bar of length  $10\mu\text{m}$  and cross-sectional area  $1\mu\text{m}^2$ , **uniformly doped with  $10^{18}\text{cm}^{-3}$  arsenic**, maintained at  $T = 300\text{K}$ . 1 Volt is applied across its length, as shown below:




(a) (6 points) What are the electron and hole concentrations,  $n$  and  $p$ , in this silicon bar?

(b) (6 points) Estimate the resistance of this silicon bar.

(c) (6 points) Qualitatively (no calculations required), how would the resistance of this silicon bar change if it were to be **additionally doped with  $2 \times 10^{18} \text{cm}^{-3}$  boron**? Explain briefly.

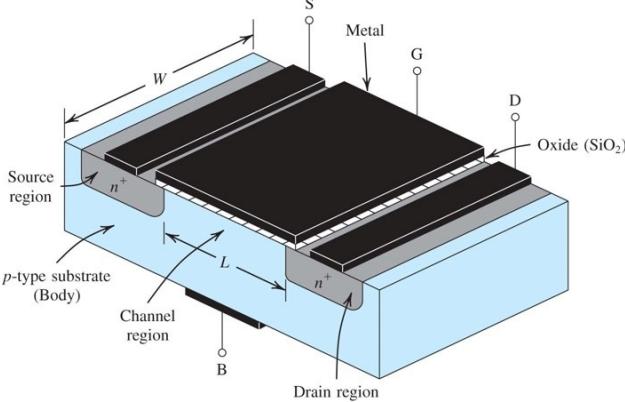4. (18 points) MOSFET

An NMOS transistor is featured with following parameters:  $W = 20\mu\text{m}$ ,  $L = 0.25\mu\text{m}$ ,  $t_{ox} = 6\text{nm}$ ,  $\mu_n = 460\text{cm}^2/(\text{V} \cdot \text{s})$ , and  $V_t = 0.5\text{V}$ .




(a) (6 points) Calculate  $C_{ox}$  and  $k'_n$ .

(b) (6 points) Calculate  $V_{OV}$ ,  $V_{GS}$ , and  $V_{DS,min}$  needed to operate the transistor in the saturation region with a DC  $I_D = 0.5\text{mA}$ .

(c) (6 points) Assume  $v_{DS}$  is very small, find the values of  $V_{OV}$  and  $V_{GS}$  required to cause the device to operate as a  $100\Omega$  resistor.

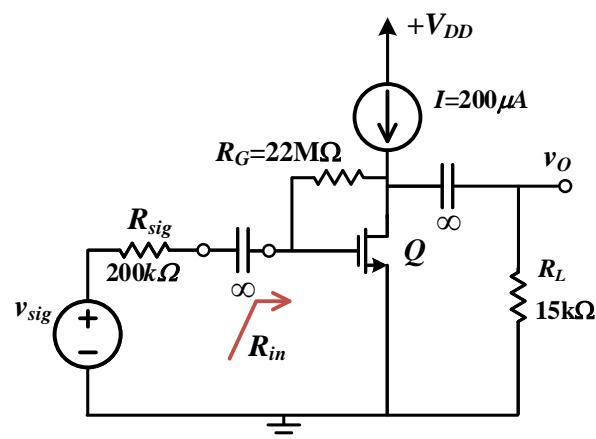5. (22 points) Transistor Amplifier

The figure below shows a discrete circuit amplifier. the NMOS transistor has  $V_t = 0.8\text{V}$ , early voltage  $V_A = 20\text{V}$ , and operate with  $V_D = 1\text{V}$ .



(a) (8 points) Calculate  $g_m$  and  $r_o$ .

(b) (6 points) Calculate  $R_{in}$  and the voltage gain  $v_o/v_{sig}$ .

(c) (6 points) What do  $V_D$  and the voltage gain  $v_o/v_{sig}$  become if  $I$  is increased to  $1\text{mA}$ ?